


Power factor correction

Choose yourself and new technologies






Project co-financed from the EU European Social Fund






Wroclaw University of Technology

Master programmes in English
at Wroclaw University of Technology




References

Advertisement materials and application notes of „ON Semiconductor“






Project co-financed from the EU European Social Fund




Wroclaw University of Technology

Master programmes in English
at Wroclaw University of Technology





Input Characteristics of a Typical Switched-Mode Power Supply without PFC


Top: Input Voltage Bottom: Input Current

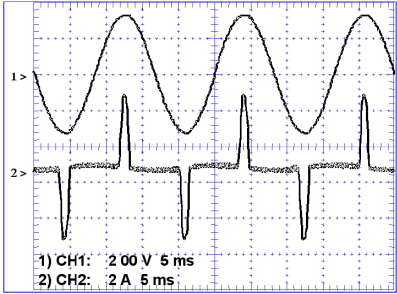

1) CH1: 200 V 5 ms
2) CH2: 2 A 5 ms

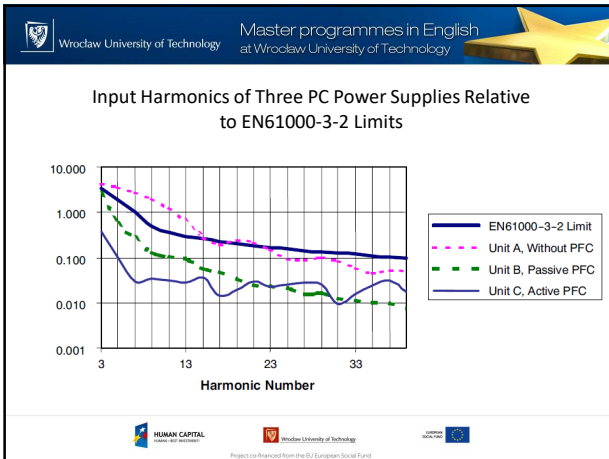

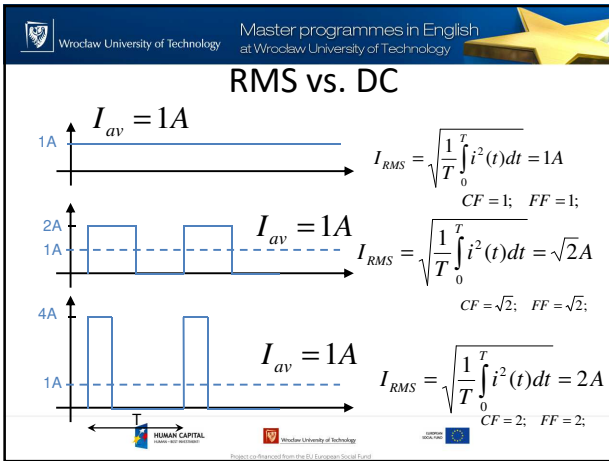

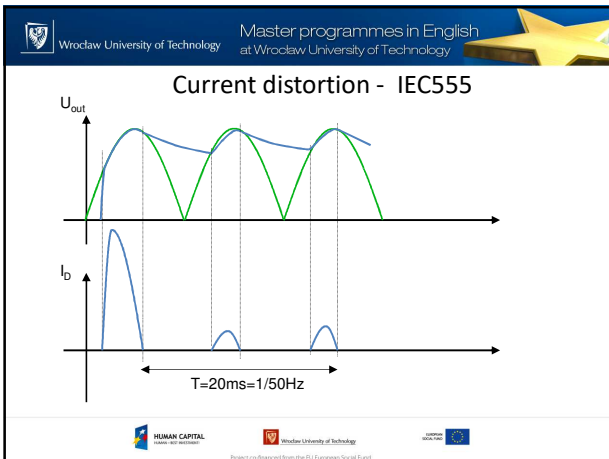

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Supply current distortion - IEC555 EN 61000-3-2

- harmonics (up to 40 harmonic)
- current fluctuations of load
- surge current ???

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Power Factor

$$\eta = \frac{P_{real}}{U_{RMS} \cdot I_{RMS}} \leq 1 \left[\frac{W}{VA} \right]$$

P – real power [w]
Q – reactive power [Var]
S – apparent power [VA]

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Power triangle (no current harmonics case)

$P = V_{RMS} I_{RMS} \cos \varphi$

$S = V_{RMS} I_{RMS}$
total apparent power

$Q = V_{RMS} I_{RMS} \sin \varphi$
reactive or quadrature power

DB5IN224A

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Power Factor $\eta = \cos\theta$

$U_{RMS} = 230V; U_{max} = 325V$

$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{20ms} (5A)^2 (2 + 2ms)} = 2.2A$

$P_{real} = \frac{1}{T} \int_0^T u(t)i(t) dt = 320V \cdot 5A \cdot \frac{4ms}{20ms} = 320W$

$\eta = \frac{P_{real}}{U_{RMS} \cdot I_{RMS}} \approx \frac{320W}{230V \cdot 2.2A} \approx 0.63 \left[\frac{W}{VA} \right]$

For this current $\eta=1$

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Power triangle (no current harmonics case)

$P = \text{Real Power} = V_{RMS} \cdot I_{RMS} \cos \varphi_1$

$Q = \text{Reactive Power} = V_{RMS} \cdot I_{RMS} \sin \varphi_1$

$S = \text{Apparent fundamental power} = V_{RMS} \cdot I_{RMS}$

$D = \text{Distortion Power} = V_{RMS} \sqrt{\sum_{n=2}^{\infty} I_{n,RMS}^2}$

φ_1 is the "conventional" displacement angle (phase lag) between the in-phase fundamental I and V

θ is the distortion angle linked to the harmonic content of the current.

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Total P.F. = $\eta = \cos \varphi_1 \cos \theta$

φ_1 is the "conventional" displacement angle (phase lag) between the in-phase fundamental I and V

θ is the distortion angle linked to the harmonic content of the current.

Both of reactive (Q) and distortion (D) powers produce extra RMS currents, giving extra losses so that then the mains supply network efficiency is decreased.

Improving P.F. means to improve both of factors i.e.:

$\varphi_1 \rightarrow 0 \quad \cos \varphi_1 \rightarrow 1 = \text{reduce phase lag between I and V}$

$\theta \rightarrow 0 \quad \cos \theta \rightarrow 1 = \text{reduce harmonic content of I}$

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

THD(i) vs. P.F. ($\cos \varphi_1 = 1$)

$$PF = \frac{1}{\sqrt{1 + \left(\frac{THD(\%)}{100}\right)^2}}$$

HUMAN CAPITAL Wrocław University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

THD vs. P.F.

$$P.F. = \frac{\cos(\varphi_1)}{\sqrt{1 + \left(\frac{THD(\%)}{100}\right)^2}} = \cos(\theta) \cdot \cos(\varphi_1)$$


HUMAN CAPITAL Wrocław University of Technology


Wrocław University of Technology Master programmes in English at Wrocław University of Technology


Why PF should be 1

$$P_{LOST} = (I_{RMS})^2 R = \left(\frac{1}{\eta}\right)^2 \left(\frac{P}{U_{RMS}}\right)^2 R \quad \left(\frac{1}{\eta}\right)^2 = \left(\frac{1}{0,63}\right)^2 = 2,52$$

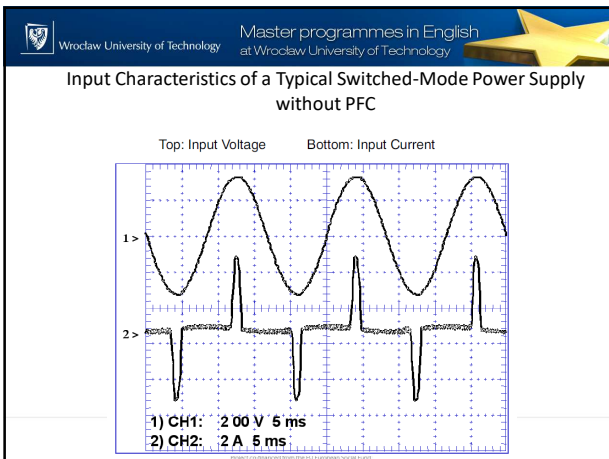HUMAN CAPITAL Wrocław University of Technology



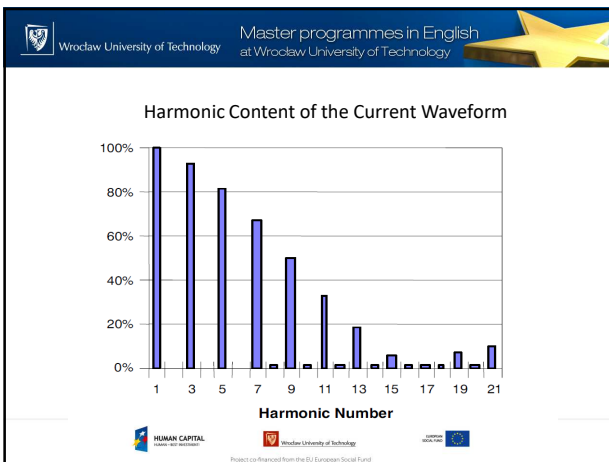

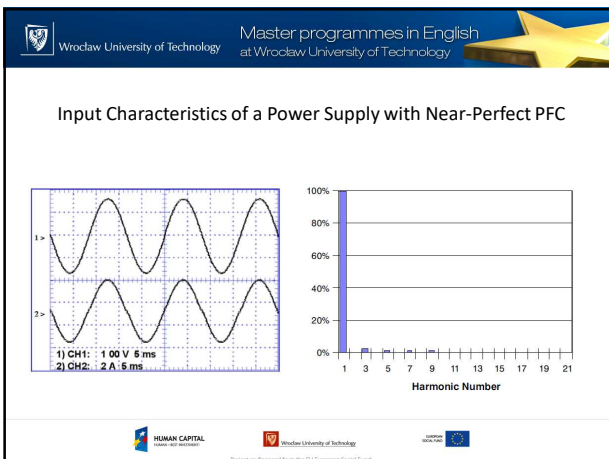

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Input Characteristics of PC Power Supplies with Different PFC Types (None, Passive, and Active)

Waveforms:

1. Input current with no PFC
2. Input current with passive PFC
3. Input current with active PFC
4. Input voltage

CH1: 5 A, 2.5 ms
CH2: 5 A, 2.5 ms
CH3: 5 A, 2.5 ms
CH4: 200 Volt, 2.5 ms

HUMAN CAPITAL
Wroclaw University of Technology
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Input Harmonics of Three PC Power Supplies Relative to EN61000-3-2 Limits

EN61000-3-2 Limit
Unit A, Without PFC
Unit B, Passive PFC
Unit C, Active PFC


HUMAN CAPITAL
Wroclaw University of Technology
Project co-financed from the EU European Social Fund


Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology


Passive PFC in a 250W PC Power Supply

Inrush Current Limiter (Thermistor)
Differential Mode Inductor (L2)
Common Mode Inductor (L3)
PFC Inductor
0.0047
0.022
0.022
0.01
230 Vac
115 Vac
470
325 Vdc to Forward Converter
470

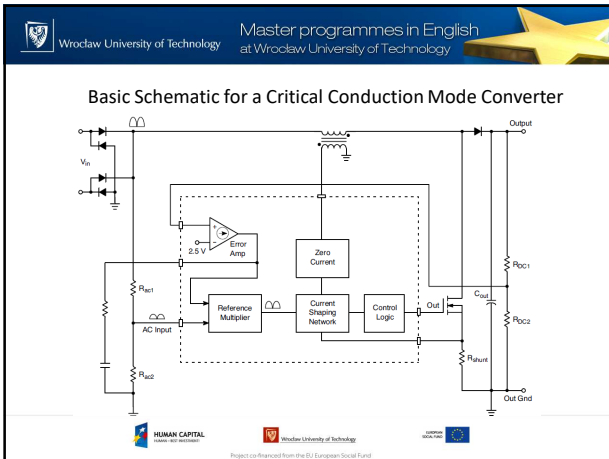HUMAN CAPITAL
Wroclaw University of Technology
Project co-financed from the EU European Social Fund



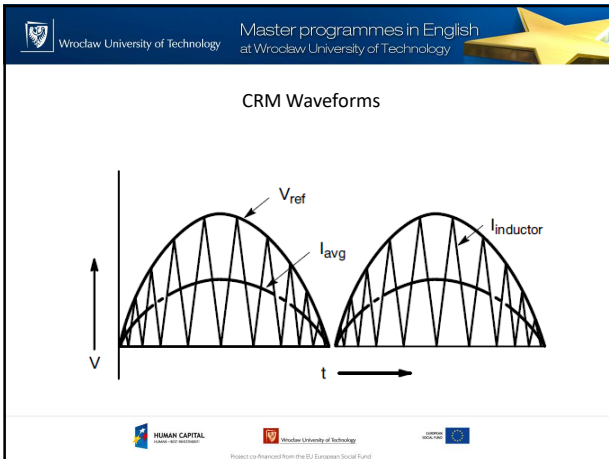

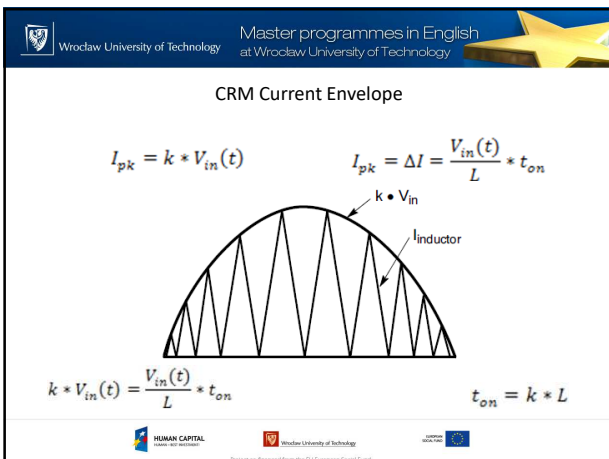

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Simplified Schematic of CRM Controller without Multiplier

HUMAN CAPITAL Wroclaw University of Technology

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Follower Boost


HUMAN CAPITAL Wroclaw University of Technology


Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology


Block Diagram of the Classic PFC Circuit

$$V_i = V_{DIV} \cdot K_M \cdot V_{SIN} = \frac{V_{ERR} \cdot K_M}{K_D \cdot K_S} \cdot V_{SIN} \cdot K_S \cdot K_D^2 \cdot V_{IN}^2$$

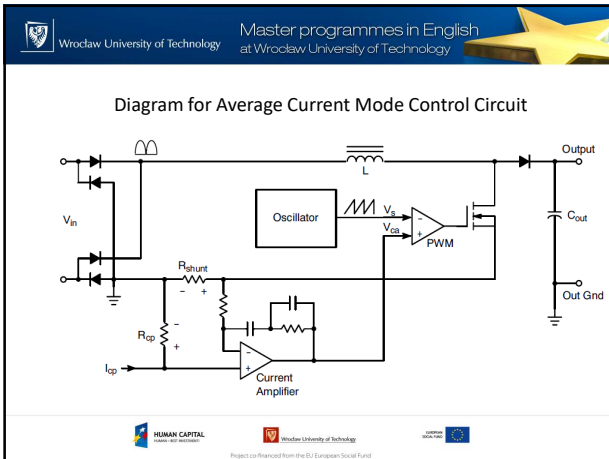HUMAN CAPITAL Wroclaw University of Technology



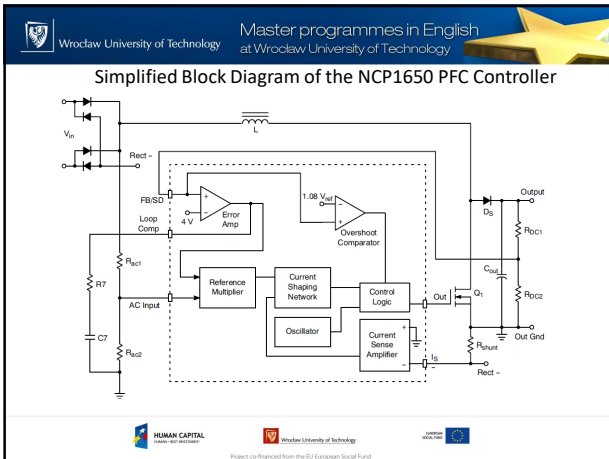

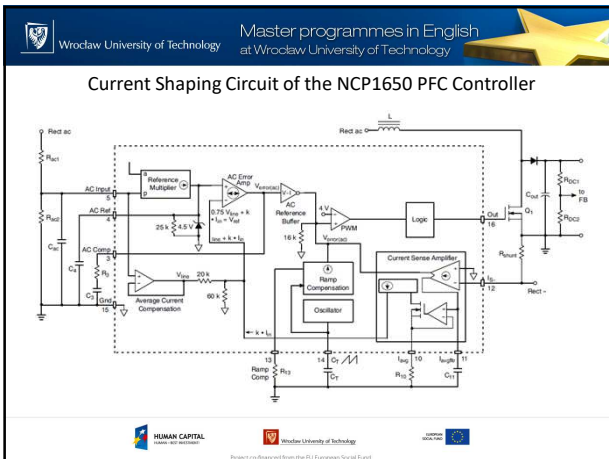

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Summed Waveforms

HUMAN CAPITAL Wroclaw University of Technology

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Waveshaping Circuit Waveforms

HUMAN CAPITAL Wroclaw University of Technology

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Representative Schematic of Voltage Loop Error Amplifier

HUMAN CAPITAL Wroclaw University of Technology

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Switching Multiplier

HUMAN CAPITAL
Wrocław University of Technology
Project co-financed from the EU European Social Fund

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Single Stage PFC Using the NCP1651

HUMAN CAPITAL
Wrocław University of Technology
Project co-financed from the EU European Social Fund

Wrocław University of Technology Master programmes in English at Wrocław University of Technology

Critical Conduction Mode PFC with Fixed Output Voltage

HUMAN CAPITAL
Wrocław University of Technology
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Critical Conduction Mode PFC with Variable Output Voltage

85-265 V
50/60 Hz
AC Input

F2
EMI filter for
var. freq.
ripple

P2
PFC Boost
Front-end using
MC33260

200-400 V
DC out

D2
Step-down Isolated
DC-DC Converter
(200 kHz)

12 V, 10 A
DC out

HUMAN CAPITAL
Wroclaw University of Technology
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Continuos Conduction Mode PFC with Fixed Output Voltage

85-265 V
50/60 Hz
AC Input

F3
EMI filter for
fixed freq.
ripple

P3
PFC Boost
Front-end using
NCP1650 (100 kHz)

400 V
DC out

D3
Step-down Isolated
DC-DC Converter
(200 kHz)

12 V, 10 A
DC out

HUMAN CAPITAL
Wroclaw University of Technology
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Continuos Conduction Mode Isolated Flyback PFC

85-265 V
50/60 Hz
AC Input

F4
EMI filter for
fixed freq.
ripple

P4 (+D4)
Single Stage Flyback PFC &
Isolated DC-DC Converter
using NCP1651 (100 kHz)

12 V, 10 A
DC out

HUMAN CAPITAL
Wroclaw University of Technology
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Mode Select Capacitor Values with respect to Vout vs Vin at Full Load

$$C_T \geq C_{int} + \frac{4 * K_{osc} * L_p * P_{inmax} * I_{resGL}^2}{V_{inmin}^2}$$

HUMAN CAPITAL Wroclaw University of Technology Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Vout vs. Vin with Respect to Ct=560pF at Various Load Conditions

HUMAN CAPITAL Wroclaw University of Technology Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Inductor (Lp)

$$I_{inpk} = \frac{\sqrt{2} \cdot P_{out}}{\eta \cdot V_{inmin}}$$

$$I_{coil_pk} = 2 \cdot I_{inpk}$$

$$L_p = \frac{2 \cdot T_{total} \cdot \left(\frac{V_{out}}{\sqrt{2}} \cdot V_{inmin}\right) \cdot V_{inmin}}{V_{out} \cdot I_{coil_pk}} = 607 \mu H \text{ for the traditional boost}$$

$$L_p = \frac{2 \cdot T_{total} \cdot \left(\frac{V_{out}}{\sqrt{2}} \cdot V_{inmin}\right) \cdot V_{inmin}}{V_{out} \cdot I_{coil_pk}} = 200 \mu H \text{ for the follower boost}$$

HUMAN CAPITAL Wroclaw University of Technology Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Power Switch

$$I_Q = \sqrt{\frac{1}{6} \cdot \frac{4\sqrt{2} \cdot V_{in\ min}}{9 \cdot \pi \cdot V_{out}}} \cdot I_{coil_pk}$$

HUMAN CAPITAL
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Output Capacitor

Energy = Power x Time
where power = 150 W (output power)
and time = 20 ms (hold - up time)

$$\Delta U = U_1 - U_2 = \frac{1}{2} C_{out} (V_{out}^2 - V_{out\ min}^2)$$

$$C_{out} = \frac{2 \cdot \Delta U}{V_{out}^2 - V_{out\ min}^2} = \frac{2 \cdot 3}{400^2 - 280^2} = 74 \mu F \text{ for the Traditional Boost}$$

$$C_{out} = \frac{2 \cdot \Delta U}{V_{out}^2 - V_{out\ min}^2} = \frac{2 \cdot 3}{200^2 - 150^2} = 342 \mu F \text{ for the Follower Boost}$$

HUMAN CAPITAL
Project co-financed from the EU European Social Fund

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Current Sense

Dissipation capability for RCS:


$$P_{CS} = \frac{1}{6} \cdot R_{CS} \cdot I_{coil_pk}^2$$

Overcurrent protection resistor:

$$R_{OCP} = \frac{R_{CS} \cdot I_{coil_pk}}{I_{OCP}}$$

HUMAN CAPITAL
Project co-financed from the EU European Social Fund

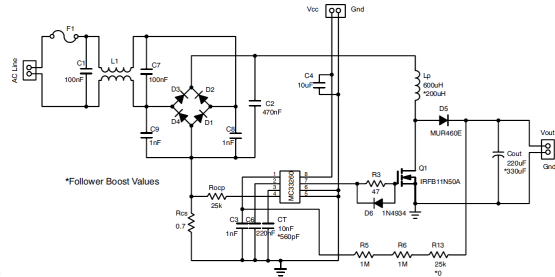MC33260 Traditional and Follower Boost Schematic



Design Table – Traditional and Follower Boost


Mode Select	Traditional Boost	Follower Boost
P _O (W)	150	150
L _p (μH)	607	200
C _D (μF)	220	330
R _{CS} (Ω)	0.7	0.7
R _{OCF} (kΩ)	20	20
C _T (pF)	10000	560


Measurement Results for the Traditional Boost

150 W PFC Front End – MC33260 Traditional Boost				
V _{in} (Vac)	85	115	175	265
Efficiency (%)	87.8	91.6	94.3	96.2
THD (%)	8.87	11.04	14.8	17.6
PF (%)	99.49	99.32	98.83	97.61
V _{out} (V)	401.5	408.3	414.6	418

Measurement Results for the Follower Boost

150 W PFC Front End – MC33260 Follower Boost				
V _{in} (Vac)	85	115	175	265
Efficiency (%)	89.5	92.5	93.7	95.9
THD (%)	5.95	6.21	10.67	21
PF (%)	99.76	99.75	99.25	97.37
V _{out} (V)	203	276	391	400.7

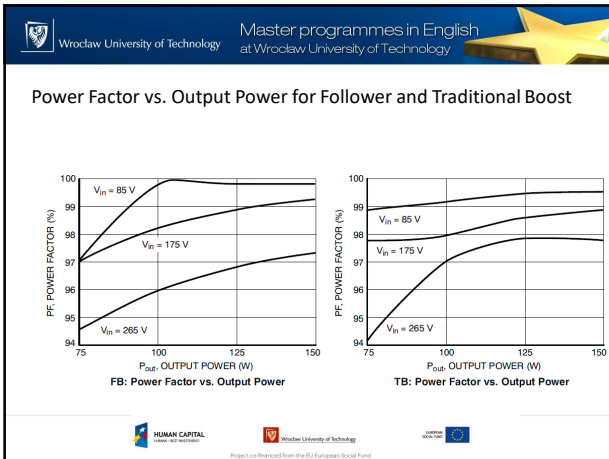

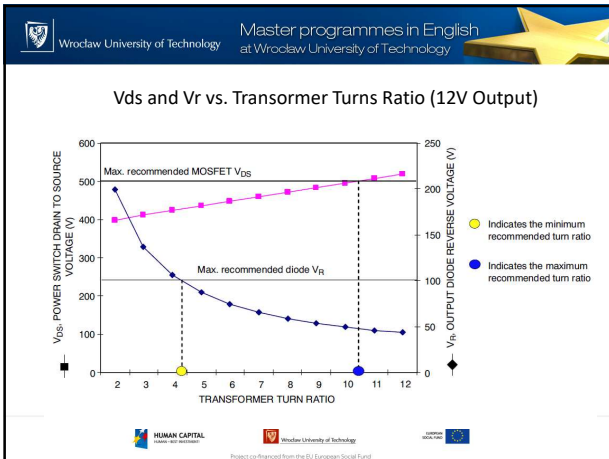

Wroclaw University of Technology Master programmes in English at Wroclaw University of Technology

Power Switch


$$V_{DS} = \sqrt{2} \cdot V_{in\ max} + \frac{N_p}{N_s} \cdot V_{out} + I_p \cdot \sqrt{\frac{L_p(\text{leakage})}{C_p + C_{oss}}}$$

$$I_{pk} = \frac{\sqrt{2} \cdot P_{in} \cdot T}{V_{in\ min} \cdot t_{on}} + \frac{2 \cdot \sqrt{2} \cdot V_{in\ min} \cdot t_{on}}{L_p}$$

HUMAN CAPITAL Wroclaw University of Technology



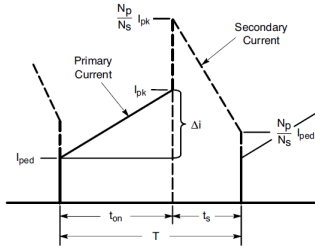Primary and Secondary Currents of the Flyback Transformer





Output Rectifier


$$V_R \geq V_{out} + \sqrt{2} \cdot V_{in \max} \cdot \frac{N_s}{N_p}$$

$$P_d = V_F \cdot I_F \cdot (1-D) \text{ with } I_F = \frac{(I_{pk} + I_{ped})}{2} \cdot \frac{N_p}{N_s}$$





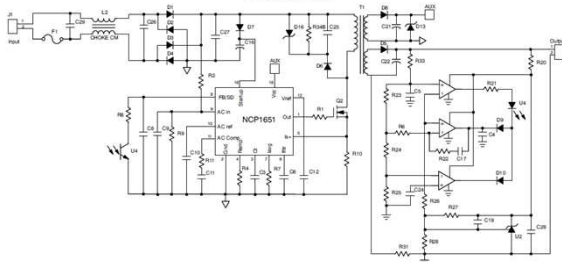
Simplified NCP1651 One Stage Flyback Power Factor Converter Schematic




NCP1651 PFC Circuit Results

V _{in} (Vac)	85	115	230	265
P _{in} (W)	153.8	146	140.1	140.3
I _{line(rms)}	1.80	1.27	0.63	0.56
V _{out} (V)	11.72	11.78	11.77	11.78
I _{out} (A)	10	10	10	10
Efficiency (%)	76.2	80.7	84.0	84.0
PF (%)	99.79	99.86	96.70	93.87
THD (%)	4.76	4.29	6.4	7.9

Efficiency vs. Output Power

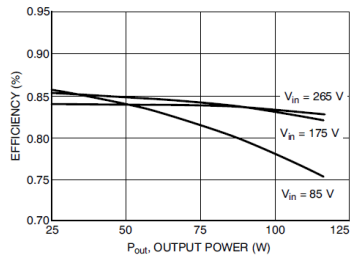


Power Factor vs. Output Power

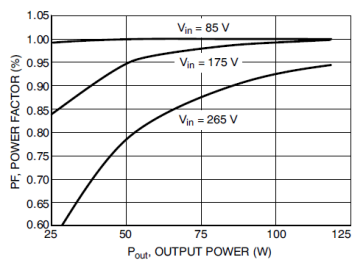



THD vs. Output Power

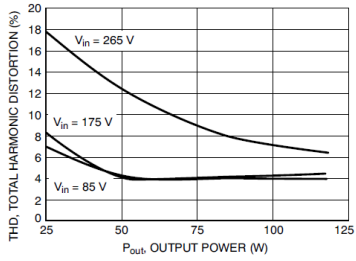



Summary

- PF definition
- PF vs. THD
- PFC methods