



Wrocław University of Technology


Amplifiers principles, frequency effects & some other parameters

Jerzy S. Witkowski



Wrocław University of Technology

Response of an AC amp

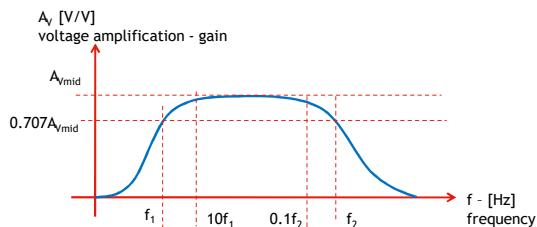


2




Wrocław University of Technology

Low/Mid/High frequency

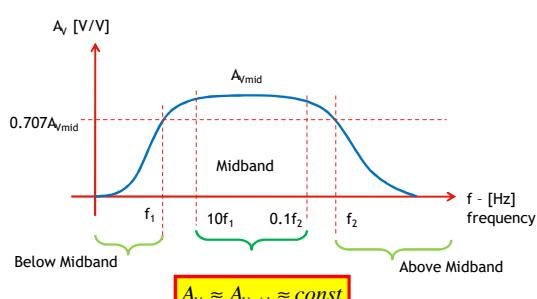




Low/Mid/High frequency

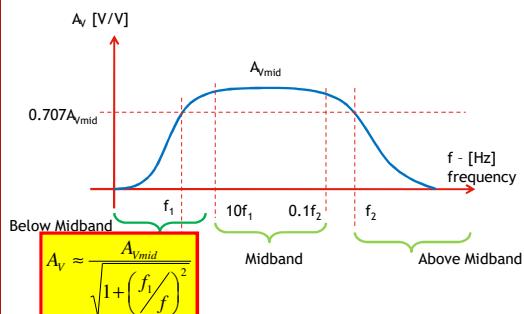

Low/Mid/High frequency

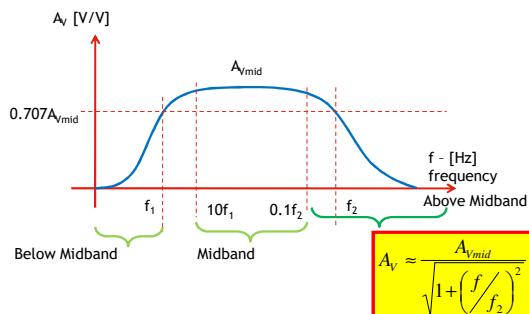

Low/Mid/High frequency

$$A_V \approx \frac{A_{\text{mid}}}{\sqrt{1 + \left(\frac{f}{f}\right)^2} \sqrt{1 + \left(\frac{f}{f_2}\right)^2}}$$

$$\Leftrightarrow \frac{A_{\text{mid}}}{\left(1 + \frac{1}{R_1 C_1 s}\right) \left(1 + R_2 C_2 s\right)}$$


Assumption:

One dominant capacitor is producing lower cutoff frequency
One dominant capacitor is producing high cutoff frequency

- "first order poles"



DC amplifier

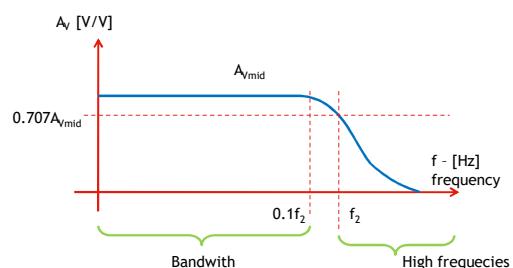

DC amplifier

$$A_V \approx \frac{A_{Vmid}}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}} \Leftrightarrow \frac{A_{Vmid}}{(1 + R_2 C_2 s)}$$

Assumption:
One dominant capacitor determines the upper cutoff frequency



Decibel power gain review of logarithms

$$x = 10^y \Leftrightarrow y = \log_{10}(x) = \log(x)$$

$$\log(1) = \log(10^0) = 0$$

$$\log(1) = 0$$

$$\log(10) = 1$$

$$\log(0.1) = -1$$

$$\log(100) = 2$$

$$\log(0.01) = -2$$

$$\log(1000) = 3$$

$$\log(0.001) = -3$$

$$\log(ab) = \log(a) + \log(b)$$

$$\log\left(\frac{a}{b}\right) = \log(a) - \log(b)$$



Decibel power gain - $A_{P(dB)}$

power gain:

$$A_P = \frac{P_{out}}{P_{in}}$$

power gain in dB:

$$A_{P(dB)} = 10 \log\left(\frac{P_{out}}{P_{in}}\right) = 10 \log(A_P)$$



Decibel power gain - important numbers

A_p (factor)		$A_{P(dB)}$
=10*10	100	20
=10*2*2	40	+16
=10^2	20	+13
10	10	+10
=2*2	4	+6
2	2	+3
1/2	0.5	-3
=1/2 * (1/2)	0.25	-6
=(1/10)	0.1	-10
=(1/2)*(1/10)	0.05	-13
=(1/2)*(1/2)*(1/10)	0.025	-16
=(1/10)*(1/10)	0.01	-20





Decibel power gain - important numbers

amplification

A_p (factor)		$A_{P(dB)}$
10	10	+10
2	2	+3

attenuation

A_p (factor)		$A_{P(dB)}$
1/2	0.5	-3
1/10	0.1	-10



Decibel voltage gain

voltage gain:

$$A_V = \frac{U_{out}}{U_{in}}$$

voltage gain in dB:

$$A_{P(dB)} = 20 \log\left(\frac{U_{out}}{U_{in}}\right) = 20 \log(A_V)$$



Decibel voltage gain - important numbers

A _V (factor)		A _{V(dB)}
=10*10	100	40
10	10	+20
=2*2	4	+12
2	2	+6
=1.41	$\sqrt{2}$	+3
=0.707	$1/\sqrt{2}$	-3
1/2	0.5	-6
= $(1/2) * (1/2)$	0.25	-6
= $(1/10)$	0.1	-20
= $(1/10)*(1/10)$	0.01	-40




Decibel voltage gain - important numbers

A _V (factor)		A _{V(dB)}
10	10	+20
2	2	+6
=1.41	$\sqrt{2}$	+3
=0.707	$1/\sqrt{2}$	-3
1/2	0.5	-6
1/10	0.1	-20




Response of an AC amp

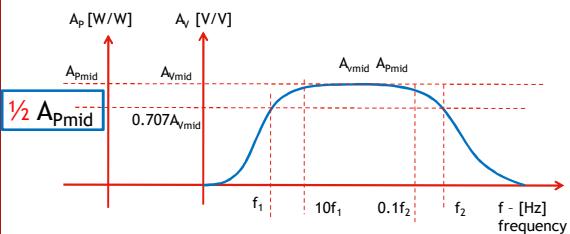



Response of an AC amp

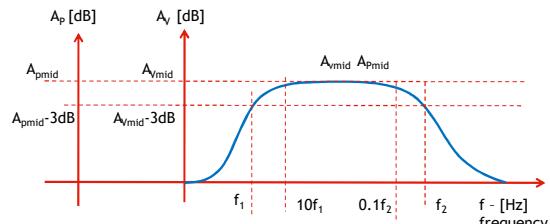

TIP :!!!!!!

-3dB= power decreases twice and voltage $\sqrt{2}$ times



Cutoff frequencies

Cutoff frequencies


Cutoff frequencies

TIP :!!!!!!

-3dB= power decreases twice
and voltage decreases $\sqrt{2} \approx 0.707$ times



[dB] vs.[V/V]

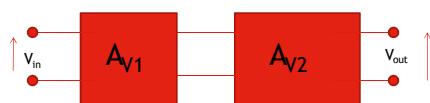


$$A_V = \frac{U_{out}}{U_{in}} = A_{V1} \cdot A_{V2}$$

$$A_{V(dB)} = A_{V1(dB)} + A_{V2(dB)}$$



[dB] vs.[V/V] an example

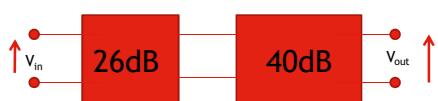

$$A_{V(dB)} = A_{V1(dB)} + A_{V2(dB)} = 26 + 40 = 66dB$$

$$66dB = 6dB + 20dB + 40dB$$

$$66dB \rightarrow \times 2 \times 10 \times 100 = 2000[V/V]$$



Decibels above a REFERENCE dBm, dBμ, dBV.....

$$P[dBm] = 10 \log \left(\frac{P[W]}{1mW} \right)$$

$$U[dB\mu] = 20 \log \left(\frac{U[V]}{1\mu V} \right)$$

$$U[dBV] = 20 \log \left(\frac{U[V]}{1V} \right)$$



Some more dB

- dB_i (isotropic antenna)
- dB_c (carrier)
- dBA



dBm an example

$$\cancel{10\text{dBm} \oplus 23\text{dBm} =} \\ \cancel{= 10\text{mW} + 200\text{mW} = 210\text{mW} = 23.2\text{dBm}}$$

$P_{in} = 10\text{dBm}$
(10 mW)

13dB
(x20W/W)
(x4.47V/V)

$P_{out} = 23\text{dBm} = 10\text{dBm} + 13\text{dB}$
(200mW)



Summary


- cutoff frequencies ?
- dB for voltage and power gains
- dB vs. factors (3,6,10,20 dB)
- dBm, dBu, dBV ?




Bode plots



Bode plots -logarithmic scales

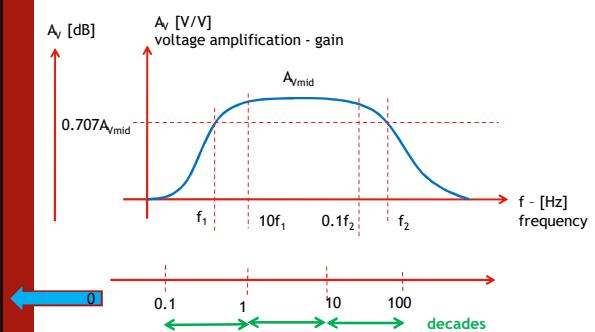


Bode plot

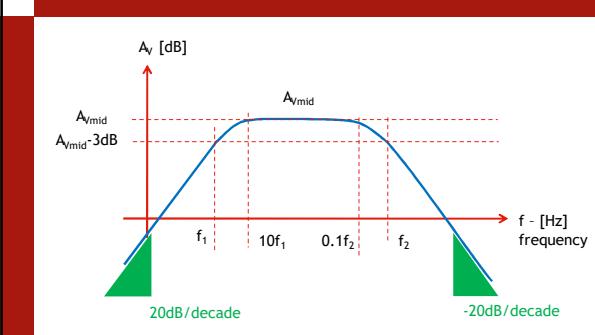



Bode plot - low f

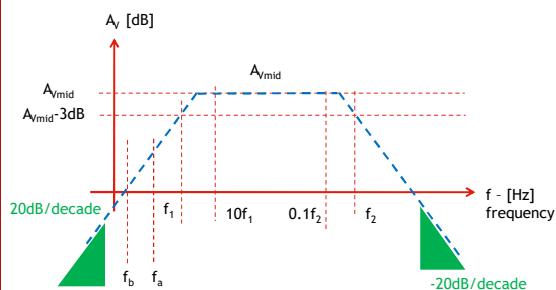

Bode plot - 20dB/decade ???

$$A_V \approx \frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$A_{V(mid)}/\text{decade} = 20 \log \frac{A_V(f_a)}{A_V(f_b)} = 20 \log \sqrt{\frac{1 + \left(\frac{f_a}{f_c}\right)^2}{1 + \left(\frac{f_b}{f_c}\right)^2}} = 20 \log \sqrt{\frac{f_a^2 + f_c^2}{f_b^2 + f_c^2}}$$


$$1 \text{ decade} = \frac{f_b}{f_a} = 10$$

$f_a, f_b \ll f_c$

$$A_{V(dB)}/\text{decade} = 20 \log \sqrt{\frac{f_a^2 + f_1^2}{f_b^2 + f_1^2}} \sqrt{\frac{f_b^2}{f_a^2}} \approx 20 \log \frac{f_b}{f_a} = 20 \log(0.1) = +20[\text{dB / dec}]$$



Bode plot - high f

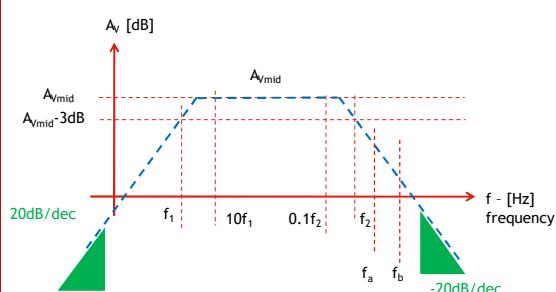



Bode plot - 20dB/decade ???

$$A_V \approx \frac{A_{Vmid}}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}}$$


$$A_{V(dB)}/\text{decade} = 20 \log \frac{A_V(f_a)}{A_V(f_b)} = 20 \log \frac{\sqrt{1 + \left(\frac{f_a}{f_2}\right)^2}}{\sqrt{1 + \left(\frac{f_b}{f_2}\right)^2}} = 20 \log \sqrt{\frac{f_a^2 + f_2^2}{f_b^2 + f_2^2}}$$

1 decade = $\frac{f_a}{f_b} = 0.1$
 $f_a, f_b \gg f_2$

$$A_{V(dB)}/\text{decade} = 20 \log \sqrt{\frac{f_a^2 + f_2^2}{f_b^2 + f_2^2}} \approx 20 \log \frac{f_a}{f_b} = 20 \log(0.1) = -20[\text{dB}/\text{dec}]$$





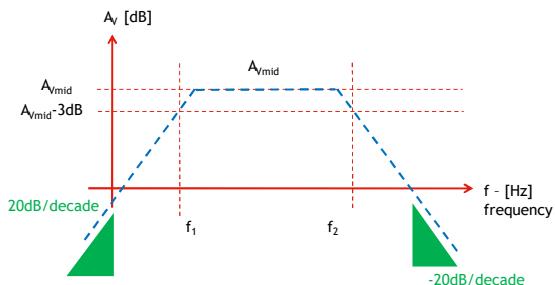
Bode plot + simplified frequency response



20dB/dec = 6dB/oct

$$A_{V(dB)}/\text{decade} = 20 \log \sqrt{\frac{f_a^2 + f_2^2}{f_b^2 + f_2^2}} \approx 20 \log \frac{f_a}{f_b} = 20 \log(0.1) = -20[\text{dB}/\text{dec}]$$

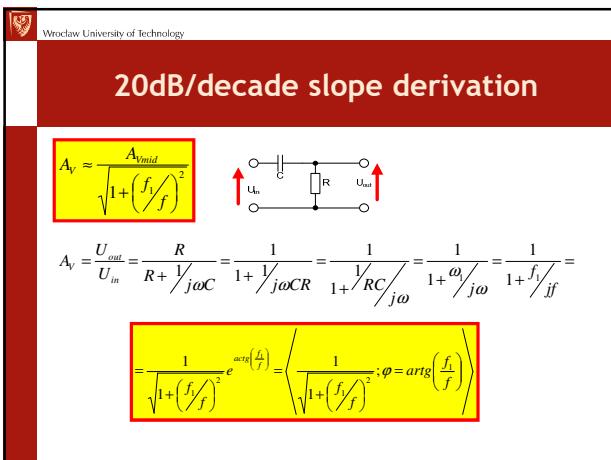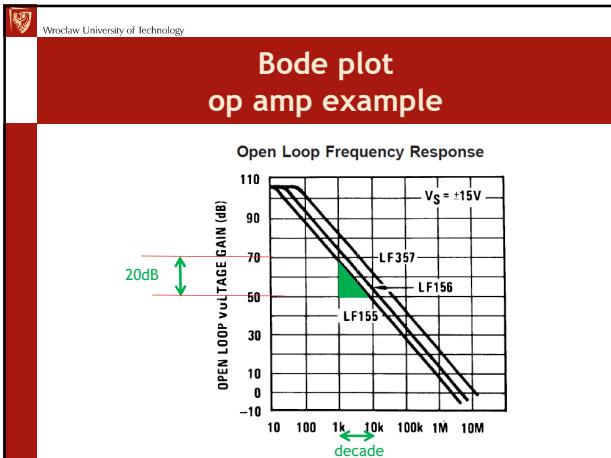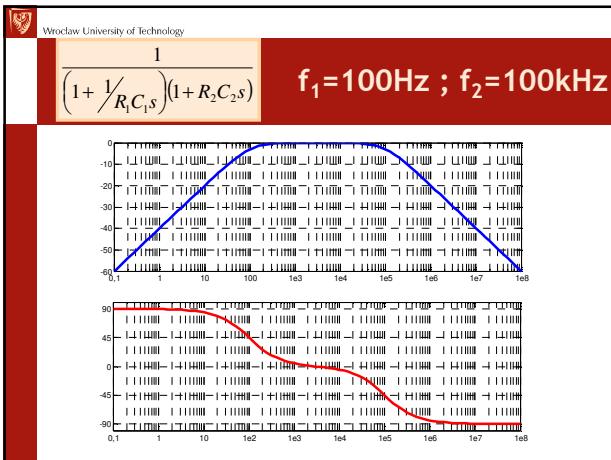
$$A_{V(dB)}/\text{oct} = 20 \log \sqrt{\frac{f_a^2 + f_2^2}{f_b^2 + f_2^2}} \approx 20 \log \frac{f_a}{f_b} = 20 \log \left(\frac{1}{2}\right) \approx -6[\text{dB}/\text{oct}]$$





20dB/decade slope derivation
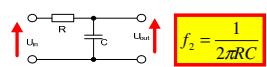
$$A_v = \frac{A_{v,0}}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}}$$




$$f_2 = \frac{1}{2\pi RC}$$

$$A_v = \frac{U_{out}}{U_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega CR} = \frac{1}{1 + j\omega \frac{1}{\omega_2}} = \frac{1}{1 + j\frac{\omega}{\omega_2}} = \frac{1}{1 + j\frac{f}{f_2}} =$$


$$= \frac{1}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}} e^{-j\text{arg}\left(\frac{f}{f_2}\right)} = \sqrt{\frac{1}{1 + \left(\frac{f}{f_2}\right)^2}}; \varphi = -\text{arg}\left(\frac{f}{f_2}\right)$$



Bode plots - phase simplified plot

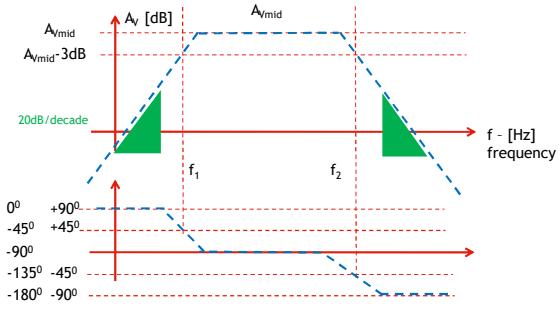


Bode plot -phase - real plot

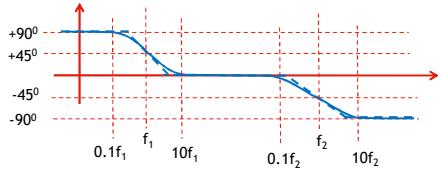



Higher order Bode plots simplified plot

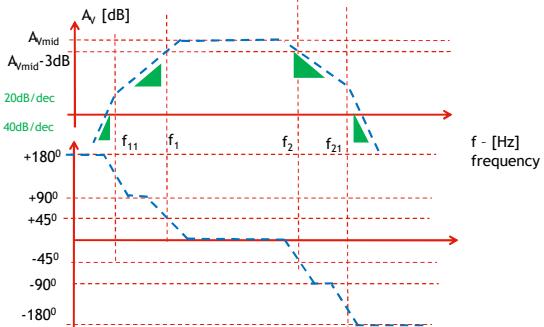


Slope vs. phase

	frequency						
Slope [dB/dec]	+60	+40	+20	0	-20	-40	-60
Phase [deg]	+270	+180	+90	0	-90	-180	-270
Transfer function	$-s^3$	$-s^2$	$-s$	const	$-1/s$	$-1/s^2$	$-1/s^3$



rise time vs. bandwidth

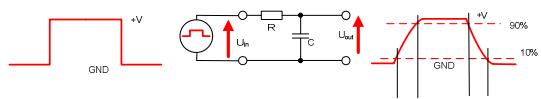

$$\frac{U_{out}}{+V} = \left(1 - e^{-\frac{t}{RC}}\right)$$



rise time vs. bandwidth

$$0.9 = \left(1 - e^{-\frac{t_2}{RC}}\right) \Rightarrow -\frac{t_2}{RC} = \ln(0.1)$$

$$0.9 = \left(1 - e^{-\frac{t_1}{RC}}\right) \Rightarrow -\frac{t_1}{RC} = \ln(0.9)$$

$$f_2 = \frac{1}{2\pi RC}$$


$$T_R = \frac{0.35}{f_2} = T_F$$

$0.35 = \frac{2\pi}{\ln(90\%)/10\%}$

Assumption:
One dominant capacitor is producing high cutoff frequency



Simulink analysis - low pass filter

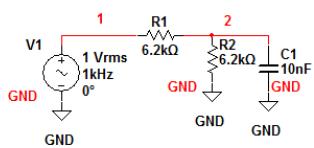


$$A(0\text{Hz}) = -6\text{dB}$$

$$f_2 = 5.134\text{Hz}$$




Simulink analysis - l.p. result

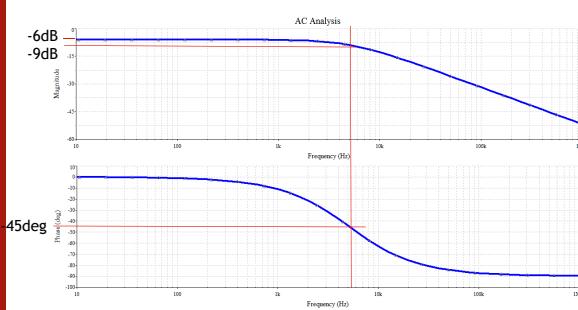




Fall & Rise time - example

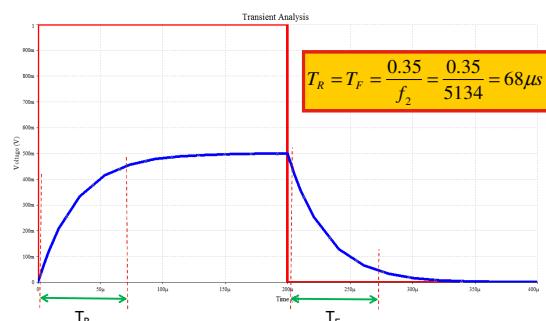

Simulink analysis - high pass filter

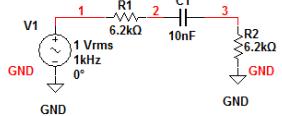


$$A(\infty \text{Hz}) = -6 \text{dB}$$

$$f_1 = 1.283 \text{Hz}$$




Simulink analysis - h.p. result

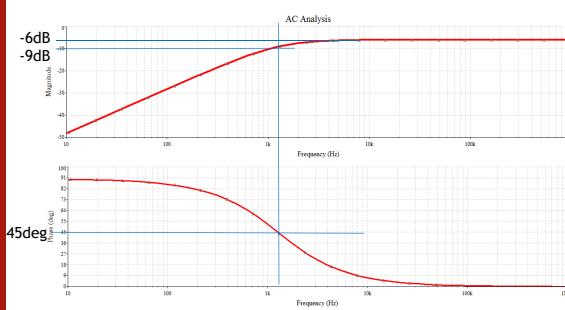




A few examples

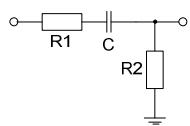

R1	C	R2	f1	Av(f=∞)
5k1	100n	10k	105Hz	-3.6dB
10k	100n	5k1	105Hz	-9.5dB
10k	220n	5k1	50Hz	-9.5dB
10k	100n	51k	26Hz	-1.6dB





A few examples

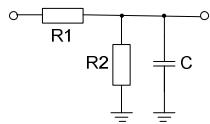

R1	R2	C	f2	Av(f=0)
10k	5k1	1n	105Hz	-9.5dB
5k1	10k	1n	105Hz	-3.6dB
5k1	10k	2n2	53Hz	-3.6dB
k51	10k	1n	26Hz	-0.4dB



Compensated divider

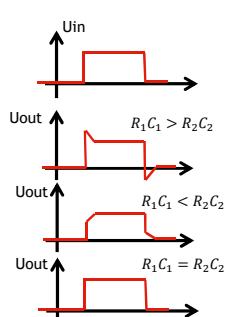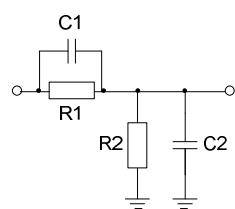



Bode plot - conclusions

- the absolute value and the phase of transfer function are correlated (exceptions exists)
- for circuits with one dominant capacitor (first order t. function) the gain rise/fall (low/high frequency) $20\text{dB/dec} = 6\text{dB/oct}$
- for cutoff frequencies ($-/+3\text{dB}$ below maximum gain) the pase is $+/- 45\text{deg}$
- when the gain rise/fall 20dB/dec the phase is $+/- 90\text{deg}$
- compensated divider- perfect pulse response- flat frequency response



Problems (Amplifiers principles, Bode plots)


- What is dB ?
- dB ($\pm 3, \pm 6, \pm 10, \pm 20$) vs. $[V/V]$ and $[W/W]$
- What is dB_μ , dB_m , dB_V ?
- What is idea of Bode plots ?
- Draw Bode plot for low-/high- pass first order filter.
- What is the idea of compensated divider ?



Power amplification




Voltage amplification unloaded amp

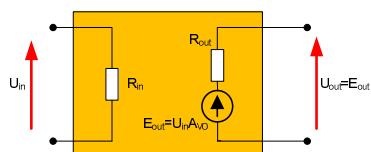

$$A_V = A_{V0}$$



Voltage amplification loaded amp

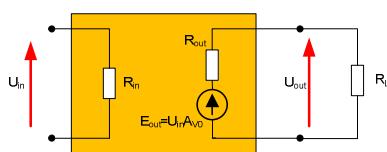


$$A_V = \frac{U_{out}}{U_{in}} = \frac{E_{out}}{U_{in}} \frac{U_{out}}{E_{out}} = A_{V0} \frac{R_L}{R_L + R_{out}}$$

TIP:
This A_V usually announced in advertisements



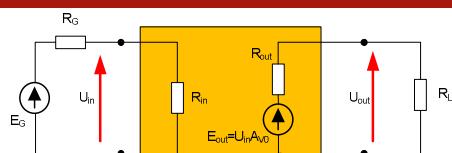Effective voltage amplification -unmatched circuit




$$A_V = \frac{U_{out}}{U_{in}} = \frac{E_{out}}{U_{in}} \frac{U_{out}}{E_{out}} = A_{V0} \frac{R_L}{R_L + R_{out}}$$

$$A_{V_{eff}} \stackrel{\text{def}}{=} \frac{U_{out}}{E_G} = \frac{U_{in}}{E_G} \frac{E_{out}}{U_{in}} \frac{U_{out}}{E_{out}} = \underbrace{\frac{R_{in}}{R_G + R_{in}}}_{\gamma} A_{V0} \underbrace{\frac{R_L}{R_L + R_{out}}}_{\frac{A_V}{A_V}} = \gamma A_V$$



Power amplification

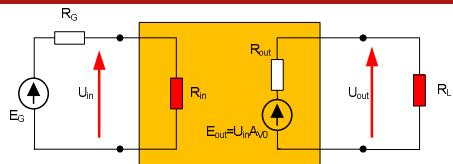


$$P_{in} = \frac{U_{in}^2}{R_{in}}$$

$$P_{out} = \frac{U_{out}^2}{R_L}$$

$$A_p = \frac{P_{out}}{P_{in}} = \left(\frac{U_{out}}{U_{in}} \right)^2 \frac{R_{in}}{R_L} = (A_v)^2 \frac{R_{in}}{R_L}$$



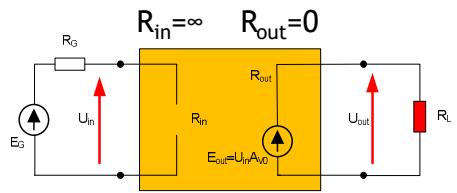Voltage vs. power amplification in dB case $R_{out}=0$; $R_{in}=\infty$




$$A_p = \frac{P_{out}}{P_{in}} = \left(\frac{U_{out}}{U_{in}} \right)^2 \frac{R_{in}}{R_L} = (A_v)^2 \frac{R_{in}}{R_L} = \infty$$

TIP:
Operational amplifier has infinite power gain
-input power is zero !!!!



Power amplification

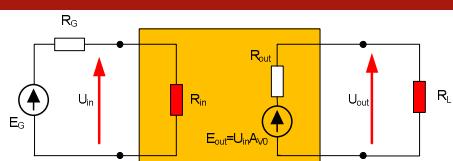

$$P_{in} = \frac{U_{in}^2}{R_{in}}$$

$$P_{out} = \frac{U_{out}^2}{R_L}$$

$$A_p = \frac{P_{out}}{P_{in}} = \left(\frac{U_{out}}{U_{in}} \right)^2 \frac{R_{in}}{R_L} = (A_v)^2 \frac{R_{in}}{R_L}$$

$$A_p = \frac{P_{out}}{P_{in}} = \left(\frac{U_{out}}{U_{in}} \right)^2 \frac{R_{in}}{R_L} = (A_v)^2 \frac{R_{in}}{R_L}$$

$$A_{P(dB)} = 10 \log \left(\frac{P_{out}}{P_{in}} \right) = 10 \log \left(\left(\frac{U_{out}}{U_{in}} \right)^2 \frac{R_{in}}{R_L} \right) = 20 \log \left(\frac{U_{out}}{U_{in}} \right) + 10 \log \left(\frac{R_{in}}{R_L} \right) = A_{V(dB)} + 10 \log \left(\frac{R_{in}}{R_L} \right)$$

$$A_{P(dB)} = A_{V(dB)} + 10 \log \left(\frac{R_m}{R_L} \right)$$

The diagram illustrates a circuit model for a power source E_G connected to a load R_L through a transmission line. The transmission line consists of two parallel branches: one with resistance R_{in} and another with a dependent voltage source $E_{out} = U_{in}A_{v0}$. The total output voltage is U_{out} , and the total output resistance is R_{out} .

Available input power:

$$P_{in \ max} = \frac{E_G^2}{4R_G}$$

Available output power:

$$P_{out \ max} = \frac{U_{out}^2}{4R_{out}}$$

Maximum available power gain:

$$A_{P-available} = \frac{P_{out \ max}}{P_{in \ max}} = \left(\frac{U_{out}}{E_G} \right)^2 \frac{R_G}{R_{out}} = \left(A_{Veff} \right)^2 \frac{R_G}{R_{out}} = \left(\frac{R_m}{R_G + R_m} A_{v0} \frac{R_L}{R_{out} + R_L} \right)^2 \frac{R_L}{R_{out}}$$

Wrocław University of Technology

---- for matched circuits

$$R_G = R_{in} \quad \& \quad R_{out} = R_L$$

Available power gain = Available output power / Available input power

$$P_{in\ max} = \frac{E_G^2}{4R_G} = \frac{U_{in}^2}{R_{in}}$$

$$P_{out\ max} = \frac{E_{out}^2}{4R_{out}} = \frac{E_{out}^2}{4R_L} = \frac{U_{out}^2}{R_L}$$

$$A_{P-available} = \frac{P_{out\ max}}{P_{in\ max}} = \left(\frac{E_{out}}{E_G} \right)^2 \frac{R_G}{R_{out}} = \left(\frac{U_{out}}{U_{in}} \right)^2 \frac{R_{in}}{R_L}$$

$$A_{P-available} = A_{P(dB)} = A_{V(dB)} + 10 \log \left(\frac{R_G}{R_L} \right) = A_{V(dB)} + 10 \log \left(\frac{R_G}{R_L} \right)$$


$$R_G = R_{in}$$

$$R_{out} = R_L$$



---- for matched circuits

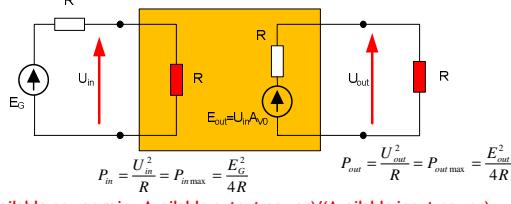- the most often case $R_G=R_L=R_{in}=R_{out}=R$



Available power gain = Available output power/(Available input power)


$$A_{P-available} = \frac{P_{out\max}}{P_{in\max}} = \left(\frac{E_{out}}{E_G} \right)^2 = \frac{P_{out}}{P_{in}} = \left(\frac{U_{out}}{U_{in}} \right)^2 = \left(A_{v0} \frac{1}{2} \right)^2 = A_v = 4 \left(\frac{U_{out}}{E_G} \right)^2 = 4(A_{Veff})^2$$

$$A_P(dB) = A_{P(dB)-available} = A_{V(dB)} = A_{Veff(dB)} + 6dB$$




---- for matched circuits another approach

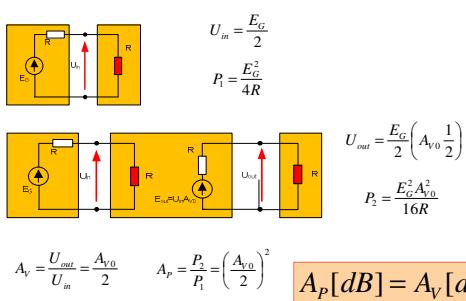- the most often case $R_G=R_L=R_{in}=R_{out}=R$



50Ω system
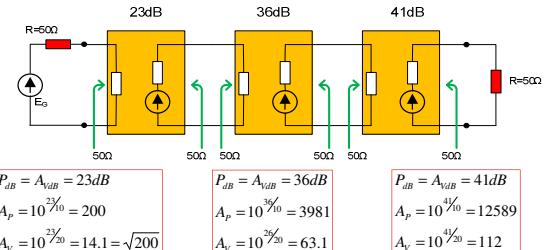
$$P_{dB} = A_{VdB} = 100dB; \quad A_p = 10^{\frac{100}{20}} = 10^{10}; \quad A_v = 10^{\frac{100}{20}} = 100000$$





dBm vs. dB μ

$$P_{dBm} = 10 \log \frac{P_w}{1mW}$$

$$P_w = ImW \cdot 10^{\frac{P_{dBm}}{10}} = \frac{U^2}{R}$$

$$U = \sqrt{ImW \cdot R \cdot 10^{\frac{P_{dBm}}{10}}}$$

$$U_{dB\mu} = 20 \log \frac{\sqrt{ImW \cdot R \cdot 10^{\frac{P_{dBm}}{10}}}}{1\mu V} = 20 \log \frac{\sqrt{ImW \cdot R}}{1\mu V} + 20 \log \sqrt{10^{\frac{P_{dBm}}{10}}}$$

$$U_{dB\mu} = 10 \log(10^9 R) + P_{dBm} = 80 + 10 \log(10R) + P_{dBm}$$

$$U_{dB\mu} = 107 + P_{dBm}$$

for $R=50\Omega$



Problems (power amplification)

- voltage gain vs. effective voltage gain
- Voltage vs. power amplification in dB
- available power gain ?
- available power gain for matched systems ?