




Wrocław University of Technology

Operational Amplifier Op-Amp



Wrocław University of Technology


Op-Amp block diagram

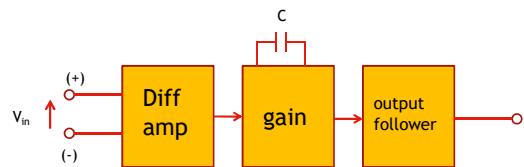



Wrocław University of Technology

Op-Amp model

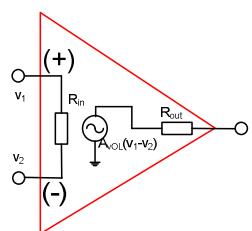



uA741 - inside


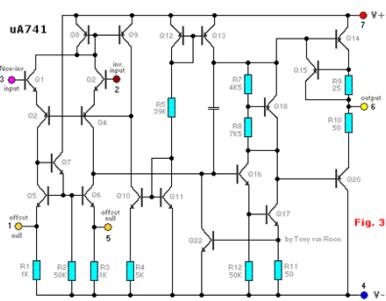


Fig. 3

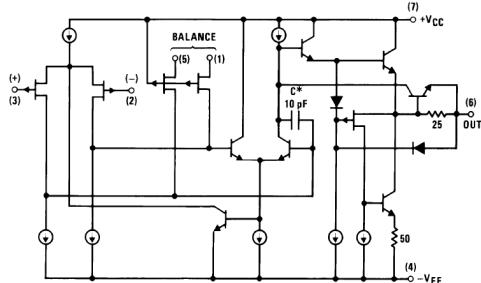

LF155/157



Typical Op-Amp parameters

Parameter	Symbol	Perfect op-amp	uA741	LF157
OL gain	A_{VOL}	infinite	100000	200000
Unity gain frequency	f_T	infinite	1MHz	20MHz
Input resistance	R_{in}	infinite	2MΩ	$10^{12}\Omega$
Output resistance	R_{out}	zero	75Ω	100Ω
Input bias	$I_{in(bias)}$	zero	80nA	30pA
Input offset current	$I_{in(off)}$	zero	20nA	3pA
Input offset voltage	$V_{in(off)}$	zero	2mV	1mV
CMRR	CMRR	infinite	90dB	100dB





More Op-Amp parameters

Type	Manufacturer	Offset-voltage	Bias current	Gain-bandwidth product	Slew rate	Operating voltage min/max	OPs per case	Special feature
VN-OPamps: Low cost universal types								
...74	Many	1 mV	80 nA	1.5 MHz	0.6 V/μs	6/36 V	1	high voltage
...324	Many	2 mV	45 nA	1 MHz	0.6 V/μs	3/32 V	4	single supply
AD8034	Analog D.	1 mV	1 pA	80 MHz	80 V/μs	5/24 V	2	fast
AD8038	Analog D.	1 mV	0.5 pA	520 MHz	100 V/μs	3/12 V	2	enhanced fast
AD8040	Analog D.	1 mV	0.2 pA	8 MHz	5 V/μs	3/ 6 V	4	RRIO
AD8049	Analog D.	0.5 mV	0.2 pA	0.4 MHz	0.1 V/μs	2/ 5 V	4	RRIO
AD8074	Analog D.	20 μV	5 nA	10 MHz	4 V/μs	8/36 V	4	$V_{ad} = 3nV/\sqrt{Hz}$
ADA4851	Analog D.	0.6 mV	2.1 pA	130 MHz	375 V/μs	3/10 V	4	
OP17	Analog D.	20 μV	1 nA	0.5 MHz	10 V/μs	6/36 V	1	Low offset
LTC1424	Linear	50 μV	1 pA	18 MHz	10 V/μs	3/ 6 V	4	$V_{ad} = nV/\sqrt{Hz}$
MAX4094	Maxim	30 μV	20 nA	0.5 MHz	0.2 V/μs	3/ 6 V	4	RRIO
MAX4351	Maxim	1 mV	8 μA	200 MHz	490 V/μs	9/11 V	2	RRIO, fast
MAX4495	Maxim	0.3 mV	0.2 pA	5 MHz	50 V/μs	5/10 V	4	RRIO
MAX4496	Maxim	0.2 mV	1 pA	1 MHz	0.5 V/μs	2/ 6 V	2	RRIO
LF356	National	1 mV	30 pA	5 MHz	12 V/μs	8/36 V	1	robust
LMC6034	National	1 mV	40 fA	1.4 MHz	1 V/μs	5/15 V	4	low bias
LMC6484	National	0.1 mV	20 pA	1.5 MHz	1 V/μs	3/10 V	4	RRIO
LMH6642	National	1 mV	0.4 pA	55 MHz	22 V/μs	3/12 V	2	RRIO
OPA2244	Texas I.	1 mV	10 nA	0.3 MHz	0.1 V/μs	2/36 V	2	$I_o = 40 \mu A$
OPA4134	Texas I.	0.5 mV	5 pA	8 MHz	20 V/μs	5/36 V	4	low distortion
OPA4343	Texas I.	2 mV	0.2 pA	8 MHz	0.6 V/μs	3/16 V	4	TO
TLC084	Texas I.	0.4 mV	3 pA	10 MHz	16 V/μs	5/16 V	4	single supply
TLC274	Texas I.	1 mV	0.1 pA	2 MHz	3 V/μs	3/16 V	4	single supply




Bandwith Gain bandwith

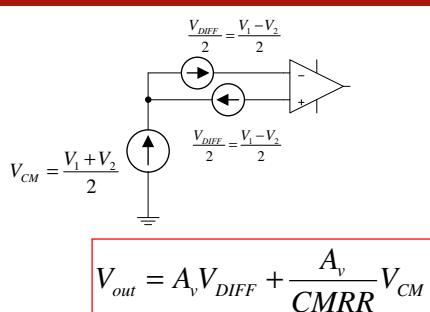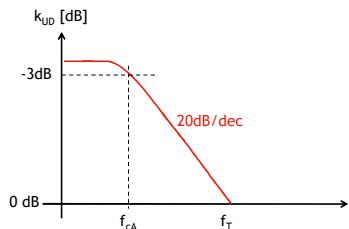



Common Mode Rejection Ratio
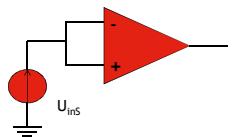
$$V_{out} = A_v V_{DIFF} + \frac{A_v}{CMRR} V_{CM}$$



$$V_{OUT} = \frac{A_v}{CMRR[V/V]} V_{inS}$$




Input offset voltage






Voltage offset vs. input bias current

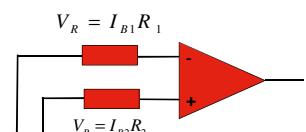


$$V_{out(off)} = (I_B(R + \Delta R) - (I_B + \Delta I_B)R) A_v = \\ = (\Delta I_B R + I_B \Delta R) A_v \underset{\Delta R=0}{\approx} \Delta I_B R A_v$$



Input and output voltage swing

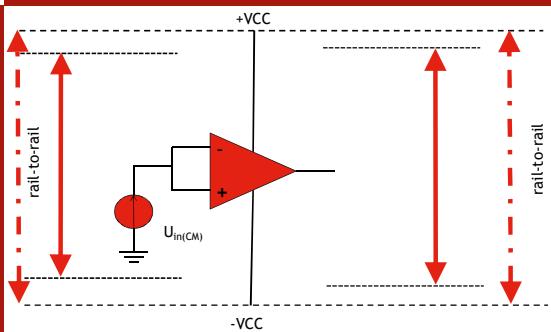

Slew-Rate Szerokość pasma mocy

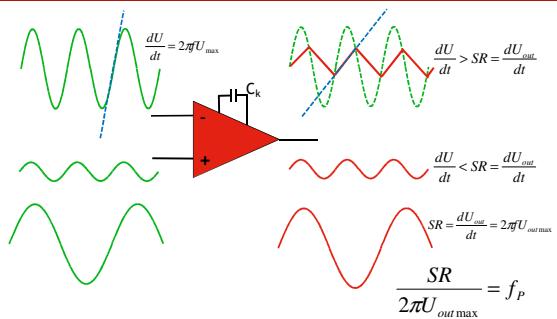

Op-Amp - power supply

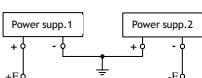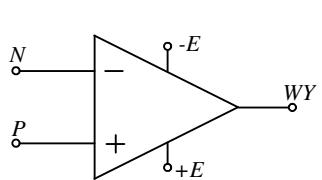




Op-Amp common applications

- inverting amp,
- Non-inverting amp
- summing amp
- substracting amp
- integrator
- differentiator



Inverting Amp virtual ground

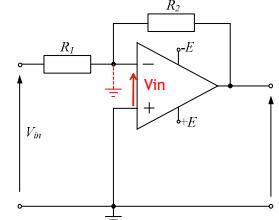

For a perfekt OA:

$$A_{vOL} = \infty$$

$$r_{in} = \infty$$


so:

$$V_{in} = \frac{V_{out}}{A_{vOL}} = \frac{V_{out}}{\infty} = 0$$

$$I_{in} = \frac{V_{in}}{r_{in}} = \frac{V_{in}}{\infty} = 0$$



Inverting Amp

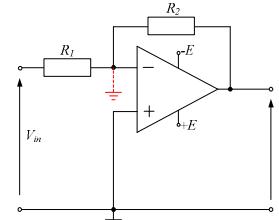

$$I_{in} = \frac{V_{in}}{R_1} \quad I_{out} = \frac{V_{out}}{R_2}$$


$$I_{in} = -I_{out}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$



inverting amp (in detail)

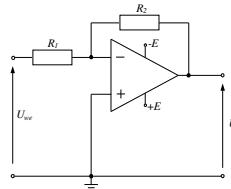

$$A_v = -\frac{R_2}{R_1} \frac{1}{1 + \frac{R_1 + R_2}{A_{v,OL} R_1}} \approx -\frac{R_2}{R_1}$$


$$R_{in} = R_1 \frac{1}{1 + \left| \frac{A_v}{A_{v,OL}} \right|} \approx R_1$$

$$R_{out} = R_{out0} \frac{R_1 + R_2}{R_1 (1 + A_{v,OL}) + R_2} \approx R_{out0} \left| \frac{A_v}{A_{v,OL}} \right|$$

$$f_2 \approx \frac{f_T}{A_v}$$




Bias current compensation

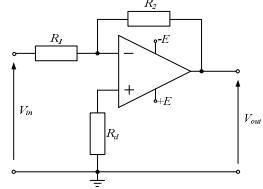

$$R_d = \frac{R_1 R_2}{R_1 + R_2}$$



non-inverting amp

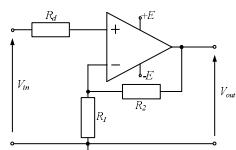

$$A_v = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{R_1 + R_2}{A_{v,OL} R_1}} = 1 + \frac{R_2}{R_1}$$


$$R_{in} = R_{in0}$$

$$R_{out} = \frac{R_{out0}}{A_{v,OL}}$$


$$f_2 \approx \frac{f_T}{A_v}$$




Follower

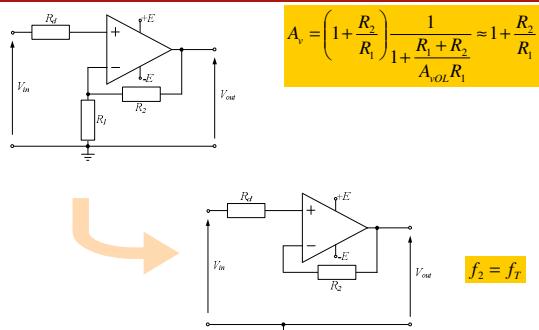

Frequency characteristic

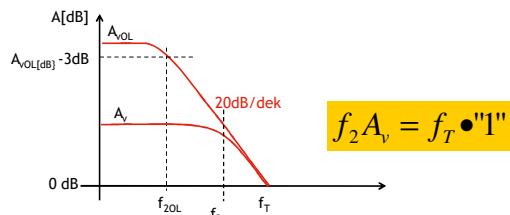

Summing amp

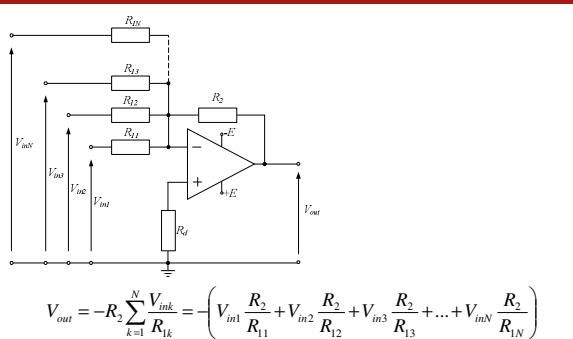



Sumator odwracający

$$V_{out} = -R_2 \sum_{k=1}^N \frac{V_{in_k}}{R_{1k}} = -\left(V_{in1} \frac{R_2}{R_{11}} + V_{in2} \frac{R_2}{R_{12}} + V_{in3} \frac{R_2}{R_{13}} + \dots + V_{inN} \frac{R_2}{R_{1N}} \right)$$


when: $R_{11} = R_{12} = R_{13} = \dots = R_{1N} = R_1$

$$V_{out} = -\frac{R_2}{R_1} (V_{in1} + V_{in2} + V_{in3} + \dots + V_{inN})$$

$$R_d = R_2 \| R_{11} \| R_{12} \| R_{13} \| \dots \| R_{1N}$$



Substraktor (DIFFERENCE AMPLIFIER)

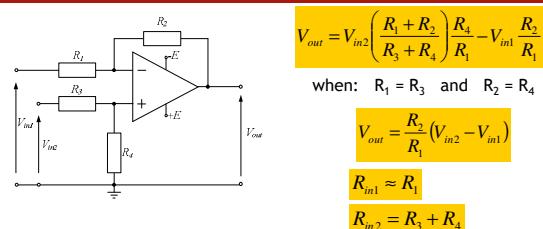

$$V_{out} = V_{in2} \left(\frac{R_1 + R_2}{R_3 + R_4} \right) R_4 - V_{in1} \frac{R_2}{R_1}$$

when: $R_1 = R_3$ and $R_2 = R_4$


$$V_{out} = \frac{R_2}{R_1} (V_{in2} - V_{in1})$$

$$R_{in1} \approx R_1$$

$$R_{in2} = R_3 + R_4$$



Instrumentation Amp

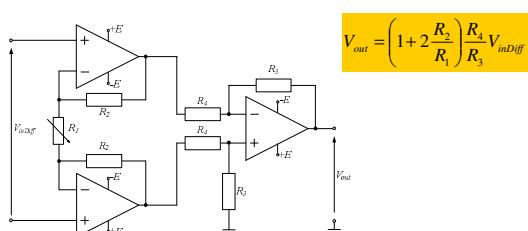


$$V_{out} = \left(1 + 2 \frac{R_2}{R_1} \right) R_4 V_{inDiff}$$



Instrumentation Amp


offset voltage can be applied

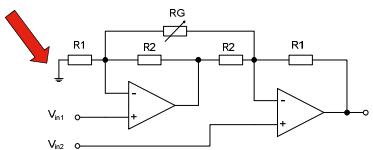

$$V_{out} = (V_{in2} - V_{in1}) \left(1 + \frac{R_3}{R_2} + \frac{2R_1}{R_G} \right)$$



Integrator

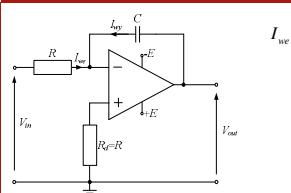

$$I_{we} = \frac{U_{we}(t)}{R} \quad I_{in} = I_C = C \frac{dV_{out}(t)}{dt}$$


$$I_{in} = -I_{out}$$

$$V_{out}(t) = -\frac{1}{RC} \int V_{in}(t) dt + U_0$$

$$V_{out} = -\frac{V_{in}}{R_i C} t + U_0$$



Differentiator

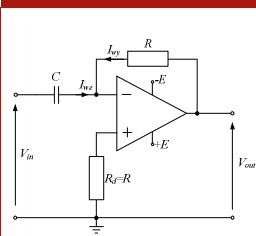


$$I_{in} = C \frac{dV_{in}(t)}{dt} \quad I_{out} = \frac{V_{in}(t)}{R}$$

$$I_{in} = -I_{out}$$

$$V_{out}(t) = -RC \frac{dV_{in}(t)}{dt}$$



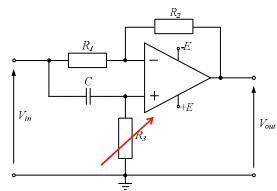
phase shifter (all pass filter of 1st order)



$$\frac{V_{out}}{V_{in}} = -\frac{1-sCR_3}{1+sCR_3}$$




current - voltage transducer

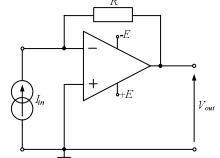

$$V_{out} = -I_{in}R$$




Voltage - current transducer

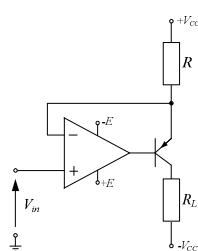

$$I_L = \frac{V_{cc} - V_{in}}{R}$$



Voltage - current transducer (2)

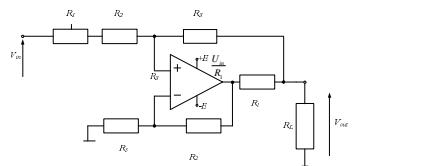


$$I_L = \frac{V_{in}}{R_1} + \frac{R_2 - R_3}{R_1 R_3} V_{out} \Big|_{R_2=R_3} = \frac{V_{in}}{R_1}$$



INIC

(Current Negative Impedance Converter)


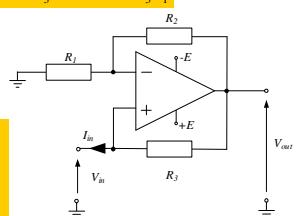
$$I_{in} = \frac{V_{out} - V_{in}}{R_3} = \frac{V_{in} \left(\frac{R_2}{R_1} + 1 \right) - V_{in}}{R_3} = \frac{R_2}{R_1 R_3}$$



$$R_{in} = -R_3 \frac{R_2}{R_1}$$




Gyrator

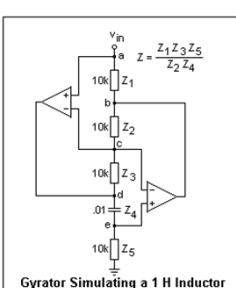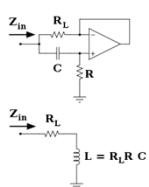


Gyrator Simulating a 1 H Inductor



Girator

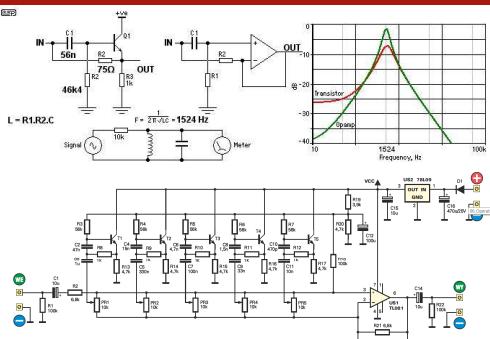

Auto-zero Amp ???

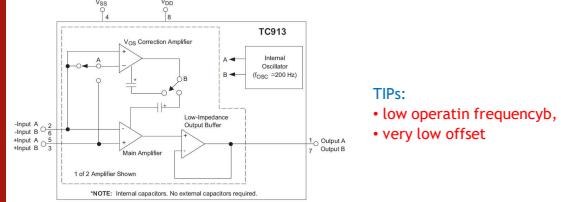

TIPS:
• low operatin frequency,
• very low offset



Summing up

- real and perfect Op-Amp parameters,
- applications:
 - inverting and non-inverting amp,
 - summing amp and subtracting amp,
 - instrumentation amp,
 - integrator and differentiator,
 - idea of an auto zero amp ??