




Wrocław University of Technology



BJT amplifier -basics


Wrocław University of Technology

BJT model

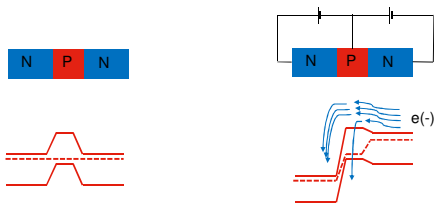

Wrocław University of Technology

Currents in BJT

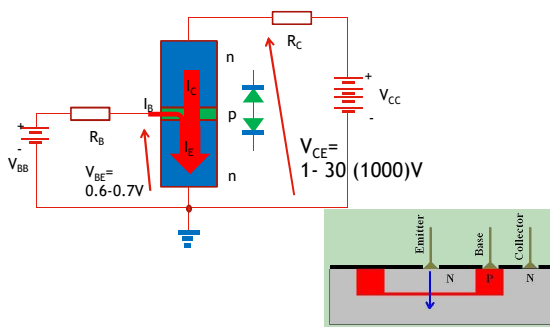

Wrocław University of Technology

CE conection - Base bias

Wrocław University of Technology

Input characteristic

$$I_B = I_s \left(e^{\frac{U_{BE}}{\phi_T}} - 1 \right)$$

Wrocław University of Technology

Output characteristic

$$I_E = I_C + I_B$$

$$I_E \approx I_C$$

$$I_B \ll I_C$$

Wrocław University of Technology

BJT - the simplest model (Ebers - Mollé)

$I_C = \beta_{DC} I_B$

Wrocław University of Technology

Bias calculation - simple example

$$V_{BE} = 0.65V$$


$$V_{BB} = I_B R_B + V_{BE} \quad I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{12 - 0.65}{220k} = 51.6\mu A$$


$$I_C = I_B \cdot \beta_{DC} = 51.6\mu A \cdot 150 = 7.74mA$$


$$V_{CE} = V_{CC} - R_C I_C = 12 - 1k \cdot 7.74mA = 4.26V$$

Wrocław University of Technology

DC load line

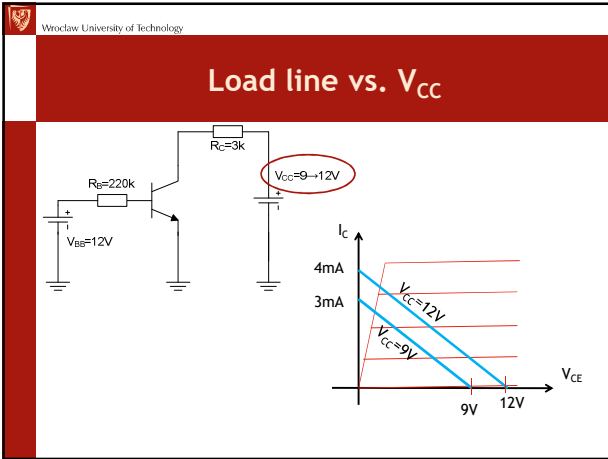

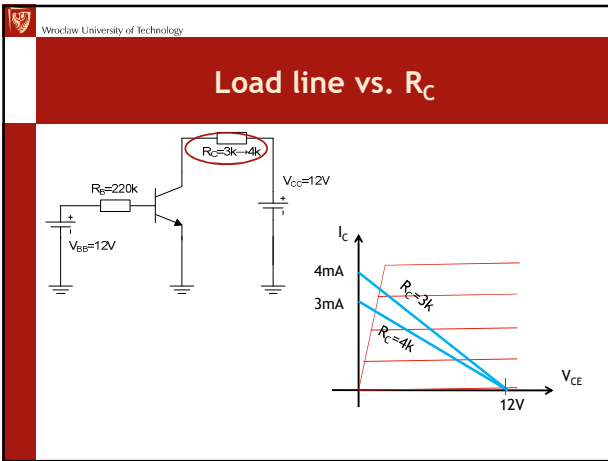

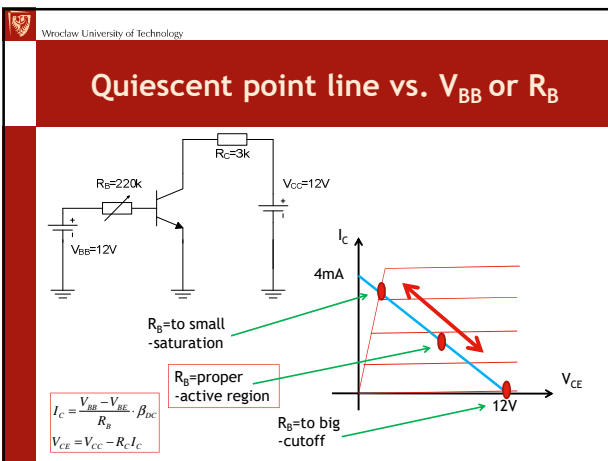

Wrocław University of Technology

Small changes effect

	I_B	I_C	V_{CE}
$\uparrow V_{BB}$	\uparrow	\uparrow	\downarrow
$\uparrow V_{CC}$	-	-	\uparrow
$\uparrow R_C$	-	-	\downarrow
$\uparrow R_B$	\downarrow	\downarrow	\uparrow
$\uparrow T (\downarrow V_{BE})$	\uparrow	\uparrow	\downarrow
$\uparrow \beta$	-	\uparrow	\downarrow

$\leftarrow \rightarrow \downarrow$

Wrocław University of Technology

Small changes effect

	I_B	I_C	V_E	V_C	V_{CE}
$\uparrow V_{BB}$	\uparrow	\uparrow	\uparrow	\downarrow	\downarrow
$\uparrow V_{CC}$	-	-	-	\uparrow	\uparrow
$\uparrow R_C$	-	-	-	\downarrow	\downarrow
$\uparrow R_E$	\downarrow	\downarrow	-	\uparrow	\uparrow
$\uparrow T (\downarrow V_{BE})$	\uparrow	\uparrow	\uparrow	\downarrow	\downarrow
$\uparrow \beta$	-	-	-	-	-

$\leftarrow \rightarrow \downarrow$

Wrocław University of Technology

VDB - Voltage Divider Bias mixed (potentiometric) biasing

Thevenin theorem >>>>>>>>>

$$V_{BB} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}}$$

$$R_B = R_{B1} \parallel R_{B2}$$

Wrocław University of Technology

Potentiometric biasing

$$V_{BB} = I_B R_B + I_E R_E + V_{BE}$$

$$V_{CC} = V_{CE} + R_C I_C + R_E I_E$$

$$V_{BE} = 0.65V; \quad I_C \approx I_E; \quad I_C = \beta_{DC} I_B$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B / \beta_{DC}} \approx I_C$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E \approx V_{CC} - (R_C + R_E) I_C$$

Wrocław University of Technology

Potentiometric biasing - an example

$$V_{BB} = V_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}} = 4V$$

$$R_B = R_{B1} \parallel R_{B2} = 6.66k$$

$$V_{BE} = 0.65V; \quad I_C \approx I_E; \quad I_C = \beta_{DC} I_B$$

$$I_E \approx I_C = \frac{V_{BB} - V_{BE}}{R_E + R_B / \beta_{DC}} = 1.62mA$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E \approx V_{CC} - (R_C + R_E) I_C = 5.5V$$

Wrocław University of Technology

Small changes effect

	I_B	I_C	V_B	V_E	V_C	V_{CE}
$\uparrow V_{CC}$	\uparrow	\uparrow	\uparrow	\uparrow	$\uparrow \downarrow$	$\uparrow \downarrow$
$\uparrow R_C$	-	-	-	-	\downarrow	\downarrow
$\uparrow R_E$	\downarrow	\downarrow	-	-	\uparrow	\uparrow
$\uparrow R_{B1}$	\downarrow	\downarrow	\downarrow	\downarrow	\uparrow	\uparrow
$\uparrow R_{B2}$	\uparrow	\uparrow	\uparrow	\uparrow	\downarrow	\downarrow
$\uparrow T (\downarrow V_{BE})$	\uparrow	\uparrow	\downarrow	\uparrow	\downarrow	\downarrow
$\uparrow \beta$	$\sim \downarrow$	\uparrow	\uparrow	\uparrow	\downarrow	\downarrow

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B / \beta_{DC}} \approx I_C$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E \approx V_{CC} - (R_C + R_E) I_C$$

Wrocław University of Technology

Stiff/Firm voltage divider

$$I_E \approx I_C = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta_{DC}}}$$

Emitter bias:
 β_{DC} independent
 $I_E \approx I_C = \frac{V_{BB} - V_{BE}}{R_E}$

Base bias:
 $I_E \approx I_C = \frac{V_{BB} - V_{BE}}{\frac{R_B}{\beta_{DC}}}$

Stiff divider: $R_E > 100 \frac{R_B}{\beta_{DC}}$

Firm divider: $R_E > 10 \frac{R_B}{\beta_{DC}}$

Wrocław University of Technology

Two supply emitter bias

$$V_{EE} = I_B R_B + I_E R_E + V_{BE}$$

$$V_{CC} - V_{EE} = V_{CE} + R_C I_C + R_E I_E$$

$$V_{BE} = 0.65V; \quad I_C \approx I_E; \quad I_C = \beta_{DC} I_B$$

$$I_E \approx I_C = \frac{-V_{EE} - V_{BE}}{R_E + \frac{R_B}{\beta_{DC}}}$$

$$V_{CE} \approx (V_{CC} - V_{EE}) - (R_C + R_E) I_C$$

Wrocław University of Technology

Collector feedback bias

$$V_{CC} = V_{BE} + I_B R_B + I_C R_C$$

$$V_{CC} \approx V_{CE} + R_C I_C$$


$$V_{BE} = 0.65V; \quad I_C \approx I_E; \quad I_C = \beta_{DC} I_B$$

$$I_E \approx I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta_{DC}}}$$

$$V_{CE} \approx V_{CC} - R_C I_C$$

Wrocław University of Technology

Collector- Emitter feedback bias

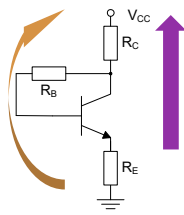

$$V_{CC} = I_B R_B + I_C R_C + I_E R_E + V_{BE}$$

$$V_{CC} \approx V_{CE} + R_C I_C + R_E I_E$$

$$V_{BE} = 0.65V; \quad I_C \approx I_E; \quad I_C = \beta_{DC} I_B$$

$$I_E \approx I_C = \frac{V_{CC} - V_{BE}}{R_E + R_C + \frac{R_B}{\beta_{DC}}}$$

$$V_{CE} \approx V_{CC} - (R_C + R_E) I_C$$


Wrocław University of Technology


Q - point stabilization


Higher – better temp stabilization


$$I_E \approx I_C = \frac{(V) - V_{BE}}{R + \left(\frac{R_B}{\beta_{DC}} \right)}$$

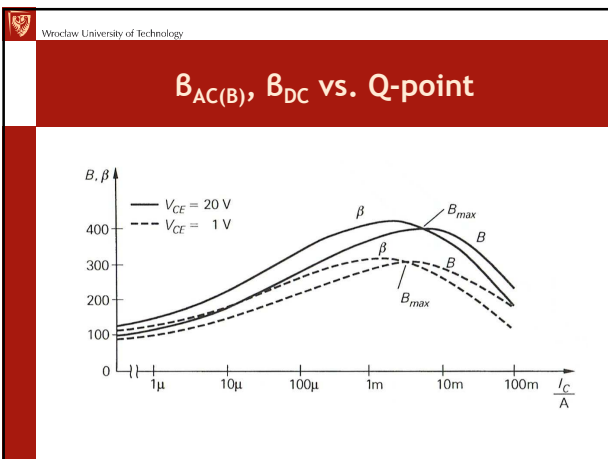
Smaller (in comp. with R) – better β stabilization




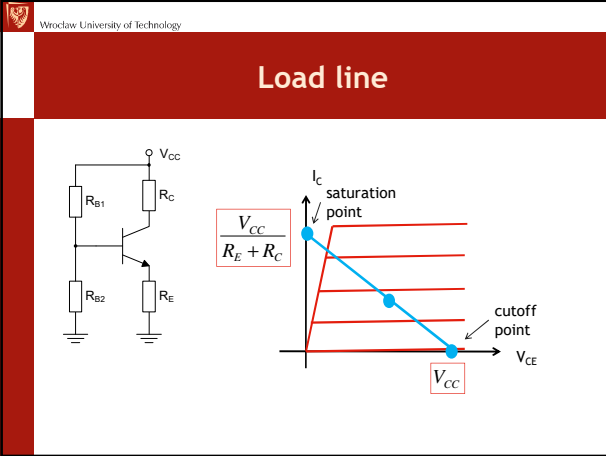


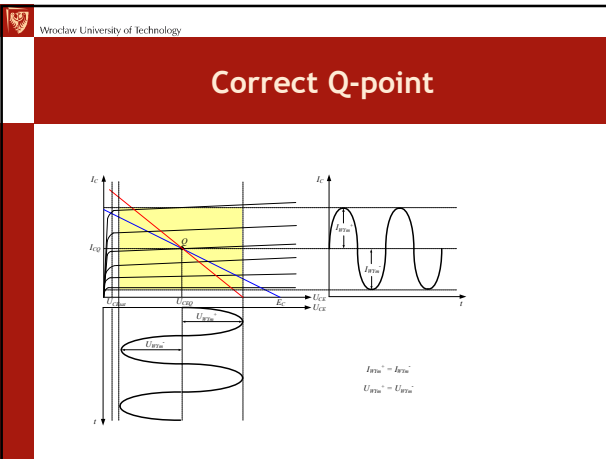

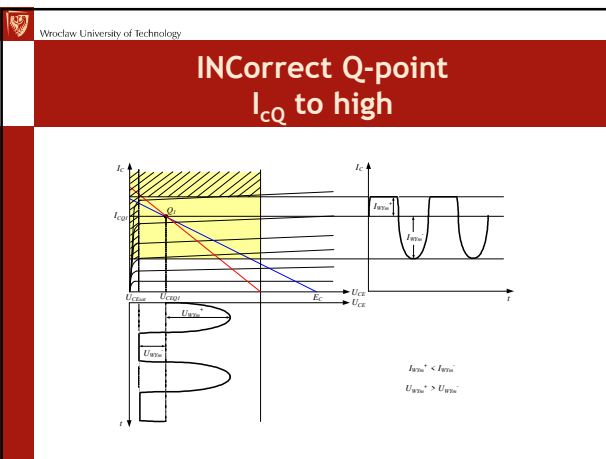

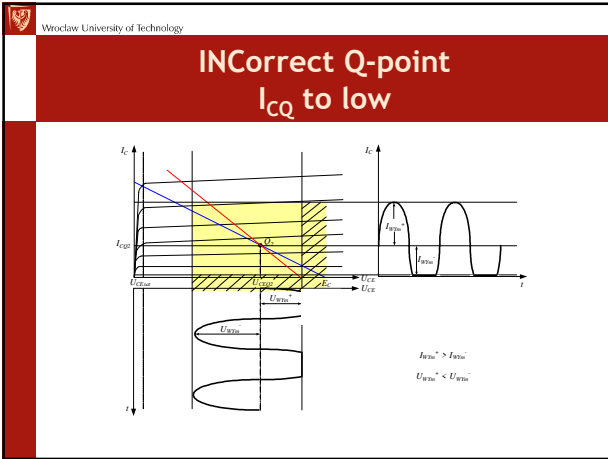

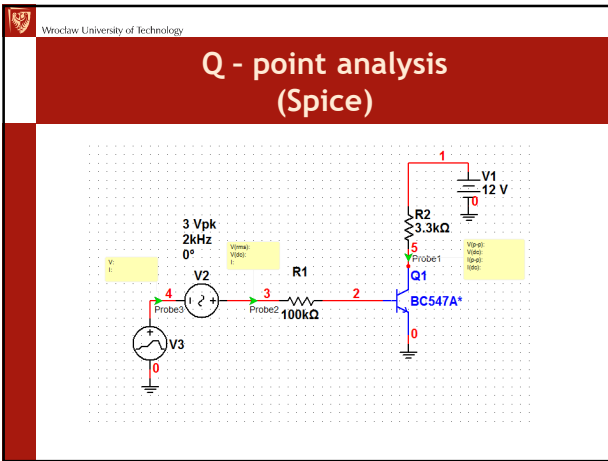

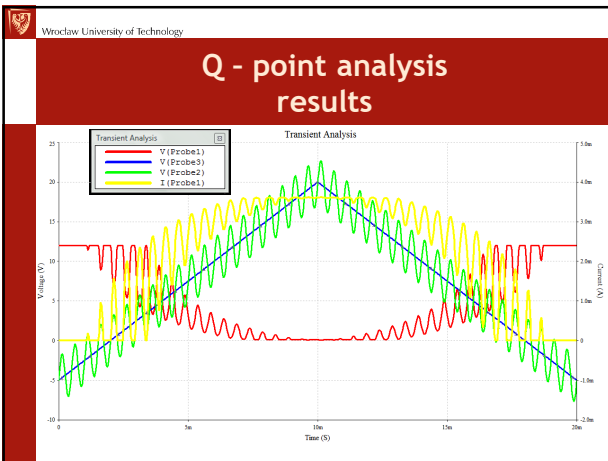

Wrocław University of Technology

Q - point vs. application

Application	$I_C(Q)$	$V_{CE}(Q)$ [V]
Low noise l.f. amps	20-200 [μ A]	1-5
Small to medium signal l.f. & h.f. amps	0.2-2 [mA]	3-10
High input impedance amps (op amps)	0.1-10 [μ A]	0.7-5
Broadband h.f. amps; low noise h.f.	5-50 [mA]	5-10
Medium power l.f. amps	0.1 -10 [A]	5-15
High power l.f. amps (class A is not popular)	2-10 [A]	20-200
high power h.f. & special amps (not common - class C is most popular)	2-10 [A]	20-1200

- Wrocław University of Technology
- ## Summary
- Ebers- Moll simplified model
 - Bias calculation
 - base current
 - emitter current
 - voltage divider
 - collector feedback
 - Load line calculation
 - Q-point vs. application

- Wrocław University of Technology
- ## Problems
- Draw and describe simplified BJT model.
 - What is the DC load line ?
 - Estimate saturation point and cut-off for given circuit (known parameters: R_C , R_E , V_{CC}).
 - Estimate Q-point for given schematic diagram (known parameters: R_{B1} , R_{B2} , R_C , R_E , U_{BEQ} , V_{CC} , β).
