



Wrocław University of Technology

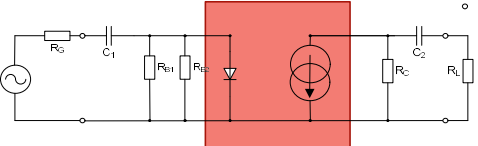

BJT amplifier -cutoff frequencies






Wrocław University of Technology


Basic -cutoff frequencies




Wrocław University of Technology

Basic - low/high cutoff frequencies

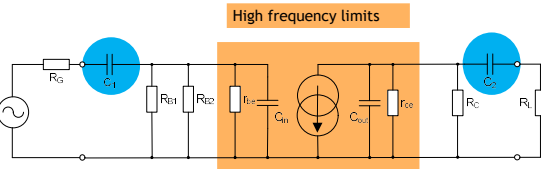


High frequency limits

Low frequency limits




Wrocław University of Technology

RC high pass filter low cuoff frequency

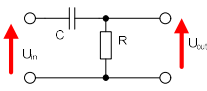

$$f_i = \frac{1}{2\pi RC}$$

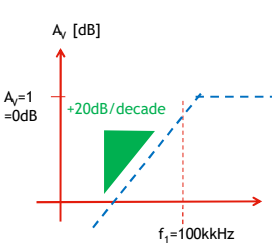



$A_v = 1 = 0\text{dB}$

$+20\text{dB/decade}$

$f_i = 100\text{kHz}$



Wrocław University of Technology

Low input cutoff frequencies

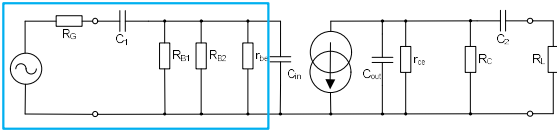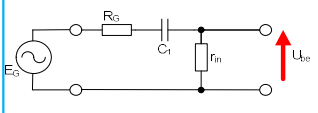Wrocław University of Technology

Input BJT low frequencies

$$U_{be} = U \frac{r_{\pi}}{R_G + r_{\pi}}$$
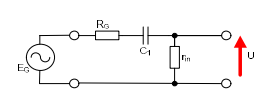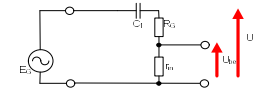
$$f_{in} = \frac{1}{2\pi(R_G + r_{in})C_1}$$

$$f_i = \frac{1}{2\pi RC}$$

Wrocław University of Technology

Low input cutoff frequencies

$$f_{in} = \frac{1}{2\pi(R_G + R_{B1} \parallel R_{B2} \parallel r_{be})C_1}$$

Wrocław University of Technology

Low input cutoff frequencies

$$f_{out} = \frac{1}{2\pi(R_C \parallel r_{ce} + R_L)C_2} = \frac{1}{2\pi(r_{outCE} + R_L)C_2}$$

Wrocław University of Technology

CE amp BJT low frequencies

$$f_{inE} = \frac{1}{2\pi r_{inE} C_E}$$

$$r_{inE} = R_E \parallel \left(\frac{r_{be} + R_{B1} \parallel R_{B2} \parallel R_G}{\beta} \right) \approx R_E \parallel \frac{1}{g_m}$$

$$f_{inE} = \frac{1}{2\pi \left(R_E \parallel \frac{r_{be} + R_{B1} \parallel R_{B2} \parallel R_G}{\beta} \right) C_E} \approx \frac{1}{2\pi \left(R_E \parallel \frac{1}{g_m} \right) C_E}$$

Wrocław University of Technology

Low frequencies of CE - sum up

$$f_{1in} = \frac{1}{2\pi(R_G + R_{B1} \parallel R_{B2} \parallel r_{be})C_1}$$

$$f_{1out} = \frac{1}{2\pi(R_C \parallel r_{ce} + R_L)C_2}$$

$$f_{1E} = \frac{1}{2\pi(R_E \parallel \frac{r_{be} + R_{B1} \parallel R_{B2} \parallel R_G}{\beta})C_E}$$

$$f_1 \approx \sqrt{(f_{1in})^2 + (f_{1out})^2 + (f_{1E})^2}$$

Wrocław University of Technology

Low frequencies of CC - sum up

$$f_{1in} = \frac{1}{2\pi \left[R_G + R_{B1} \parallel R_{B2} \parallel \underbrace{(r_{be} + \beta(R_E \parallel R_L))}_{r_{out}} \right] C_1}$$

$$f_{1out} = \frac{1}{2\pi \left[R_E \parallel \underbrace{\frac{r_{be} + R_{B1} \parallel R_{B2} \parallel R_G}{\beta}}_{r_{in,cc}} + R_L \right] C_2}$$

$$f_1 \approx \sqrt{(f_{1in})^2 + (f_{1out})^2}$$

Wrocław University of Technology

Low frequencies of CB - sum up

$$f_{1in} = \frac{1}{2\pi(R_G + R_E \parallel \frac{r_{be} + R_{B1} \parallel R_{B2}}{\beta})C_1}$$

$$f_{1out} = \frac{1}{2\pi(R_C \parallel r_{ce} + R_L)C_2}$$

$$f_{1B} = \frac{1}{2\pi(R_{B1} \parallel R_{B2} \parallel (r_{be} + \beta(R_E \parallel R_G)))C_B}$$

$$f_1 \approx \sqrt{(f_{1in})^2 + (f_{1out})^2 + (f_{1B})^2}$$

Wrocław University of Technology

Low frequencies - sum up

f	CE	CC	CB
f_{in}	$\mathcal{X} \frac{1}{2\pi(R_G + R_{B1} \parallel R_{B2} \parallel r_{be})C_1}$	$\mathcal{X} \frac{1}{2\pi(R_G + R_{B1} \parallel R_{B2} \parallel (r_{be} + \beta(R_E \parallel R_L)))C_1}$	$\frac{1}{2\pi(R_G + R_E \parallel \frac{R_L}{\beta})C_1}$
f_{out}	$\frac{1}{2\pi(R_C \parallel r_{ce} + R_L)C_2}$	$\frac{1}{2\pi(R_E \parallel \frac{r_{be} + R_{B1} \parallel R_{B2} \parallel R_L}{\beta} + R_L)C_2}$	$\mathcal{X} \frac{1}{2\pi(R_C \parallel r_{ce} + R_L)C_2}$
$f_{1E(B)}$	$\frac{1}{2\pi(R_E \parallel \frac{r_{be} + R_{B1} \parallel R_{B2} \parallel R_L}{\beta})C_E}$	NA	$\frac{1}{2\pi(R_{B1} \parallel R_{B2} \parallel (r_{be} + \beta R_E \parallel R_L))C_B}$
f_1	$f_1 \approx \sqrt{(f_{1in})^2 + (f_{1out})^2 + (f_{1E(B)})^2}$		

Wrocław University of Technology

Low frequencies - sum up

f	CE	CC	CB
f_{in}	$\mathcal{X} \frac{1}{2\pi(R_G + r_{inCE})C_1}$	$\mathcal{X} \frac{1}{2\pi(R_G + r_{inCC})C_1}$	$\mathcal{X} \frac{1}{2\pi(R_G + r_{inCB})C_1}$
f_{out}	$\frac{1}{2\pi(r_{outCE} + R_L)C_2}$	$\frac{1}{2\pi(r_{outCC} + R_L)C_2}$	$\frac{1}{2\pi(r_{outCB} + R_L)C_2}$
$f_{1E(B)}$	$\frac{1}{2\pi(R_E \parallel r_{outCC})C_E}$	$\frac{1}{2\pi(r_{inCC}(R_E \rightarrow R_L))C_B}$
f_1	$f_1 \approx \sqrt{(f_{1in})^2 + (f_{1out})^2 + (f_{1E(B)})^2}$		

Wrocław University of Technology

Input BJT low frequencies

$U_o = U \frac{R_2}{R_1 + R_2}$

$f_i = \frac{1}{2\pi RC}$

$f_{in} = \frac{1}{2\pi(R_1 + R_2)C_1}$

Wrocław University of Technology

Basic - low/high cutoff frequencies

Low frequency limits

High frequency limits

Wrocław University of Technology

RC low pass filter

$$f_2 = \frac{1}{2\pi RC}$$

$A_v = 1 = 0\text{dB}$

-20dB/decade

$f_2 = 10\text{Hz}$

Wrocław University of Technology

High input cutoff frequencies

Wrocław University of Technology

Input BJT high frequencies

$$U = U_{in} \frac{r_{in}}{R_G + r_{in}}$$

$$f_{2in} = \frac{1}{2\pi(R_G \parallel r_{in})C_{in}}$$

Wrocław University of Technology

High input cutoff frequencies

Wrocław University of Technology

Output BJT high frequencies

$$U_{in} = \frac{R_L}{R_L + r_{ce} \parallel R_C}$$

$$f_{2out} = \frac{1}{2\pi(r_{ce} \parallel R_C \parallel R_L)C_{out}} = \frac{1}{2\pi(r_{out} \parallel R_L)C_{out}}$$

Wrocław University of Technology

Output & Input cutoff frequencies

$$f_{2in} = \frac{1}{2\pi(R_G \parallel r_{in})C_{in}}$$

$$f_{2out} = \frac{1}{2\pi(r_{out} \parallel R_L)C_{out}}$$

Wrocław University of Technology

The Miller effect

$$I_{in} = I_C = \frac{V_C}{\frac{1}{s}C} = \frac{V_{in} + V_{out} |A_v|}{\frac{1}{s}C}$$

$$= \frac{V_{in}}{\frac{1}{s}C(1 + |A_v|)} = \frac{V_{in}}{\frac{1}{s}C_{in}}$$

$$C_{in} = C(1 + |A_v|)$$

Wrocław University of Technology

The Miller effect (inverting amp !!!!!)

$$C_{in} = C(|A_v| + 1)$$

$$C_{out} = C \left(\frac{|A_v| + 1}{|A_v|} \right)$$

Wrocław University of Technology

The Miller effect - an example

A_v [dB]

$A_v = 100\text{dB} = 100000\text{V/V}$

$f_2 = 10\text{Hz}$

-20dB/decade

f - [Hz]
frequency

Wrocław University of Technology

Miller effect in MOSFET

$\Delta U_{Cgd} = E + V_{CC}$

$\Delta Q = C_{gs} \cdot V_{cc} + C_{gd} (E + V_{cc}) = V_{cc} \left(C_{gs} + C_{gd} \left(1 + \frac{E}{V_{cc}} \right) \right)$

$C_{in} = C_{cb} + C_{bc} (1 + |A_v|)$

Wrocław University of Technology

Miller effect for power MOSFET switching transistors

$I_D = 17\text{ A}$

V_{GS} Gate-to-Source Voltage (V)

Q_G Total Gate Charge (nC)

$V_{DS} = 80\text{ V}$

$V_{DS} = 50\text{ V}$

$V_{DS} = 20\text{ V}$

For test circuit see figure 13

91021_08

Wrocław University of Technology

Summary of CE amp BJT medium frequencies

$\phi_V \approx 26 \text{ mV}$
 $V_T \approx 50 \div 300 \text{ V}$
 $U_{CEQ}, I_{CQ} - Q - \text{po int}$
 $\beta_{ac} \approx \beta_{dc}$

$r_{in} = R_{B1} \parallel R_{B2} \parallel r_{in}$
 $r_{out} = r_{ce} \parallel R_C \approx R_C$ (if $r_{ce} \gg R_C$)

$g_m = \frac{I_{CQ}}{\phi_T}$
 $r_{be} = \frac{\beta}{g_m}$
 $r_{ce} = \frac{V_T + U_{CEQ}}{I_{CQ}}$

$k_{veff} = -g_m \cdot \frac{R_{LOAD}}{R_L \parallel R_{out}} \cdot \frac{Y_V}{k_V} \cdot \frac{Y_{in}}{r_{inCE}}$

Wrocław University of Technology

Summary of CE BJT amp input characteristic

$C_{inCE} = C_{be} + C_{bc}(1 + |A_v|)$

$r_{in} = \underbrace{R_{B1} \parallel R_{B2}}_{R_B} \parallel r_{be}$

Wrocław University of Technology

Summary of CE amp BJT upper cutoff frequency

$C_{inCE} = C_{be} + C_{bc}(1 + |A_v|)$

$r_{inCE} = \underbrace{R_{B1} \parallel R_{B2}}_{R_B} \parallel r_{be}$

$f_{2in} = \frac{1}{2\pi(R_G \parallel r_{inCE})C_{inCE}}$


Wrocław University of Technology

Summary of CE amp BJT high frequencies

$$C_{bc} + C_{bc} = \frac{g_m}{2 \cdot \pi \cdot f_T}$$

$$g_m = \frac{I_{CQ}}{\phi_T}$$

$$C_{inCE} = C_{be} + C_{bc}(1 + |A_v|) \approx \frac{g_m}{2 \cdot \pi \cdot f_T} + C_{bc} |A_v|$$

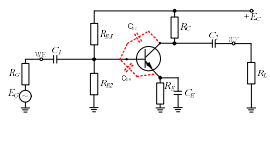


$$r_{in} = \underbrace{R_{B1} \parallel R_{B2}}_{R_B} \parallel r_{be}$$

$$f_{2in} = \frac{1}{2\pi(R_G \parallel r_{in})C_{in}}$$

Wrocław University of Technology

...taking $r_{bb'}$ into account

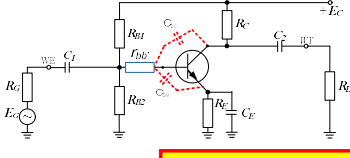


$$f_{2in} = \frac{1}{2\pi((R_G \parallel R_B + r_{bb'}) \parallel r_{be})C_{in}}$$

....very important for v.h.f.
when R_G is small and commensurate with $r_{bb'}$.

Wrocław University of Technology

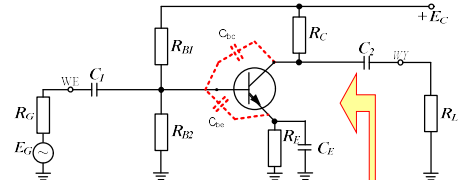Summary of CE BJT amp output characteristic



$$f_{2out} = \frac{1}{2\pi(R_L \parallel R_C \parallel r_{ce})(C_{bc} + C_{para})}$$

$$C_{outCE} = C_{bc} + C_{parasitic}$$

$$r_{outCE} = r_{ce} \parallel R_C$$

Wrocław University of Technology

Summary of CC amp BJT high frequencies

$\phi_T \approx 26mV$
 $U_{T1} \approx 50 \div 300V$
 $U_{T1}, U_{T2} - \text{pkt.pracy}$
 β
 f_T z katalogu
 C_w
dla m.cz. = 0

$$g_m = \frac{I_{CQ}}{\phi_T}$$

$$r_{ce} = \frac{U_{T1} + U_{T2}}{I_{CQ}}$$

$$C_w = \frac{g_m}{2 \cdot \pi \cdot f_T} - C_w$$

$$f_{2in} = \frac{1}{2 \cdot \pi \cdot R_G \parallel R_{B1} \cdot \left(C_{bc} + \frac{C_{be}}{g_m \cdot r_{ce} \parallel R_E \parallel R_L} \right)}$$

$f_{2out} \gg f_{2in}$

Wrocław University of Technology

Summary of CB amp BJT high frequencies

$$f_{2in} = \frac{1}{2\pi \left(R_G \parallel R_E \parallel \frac{r_{be}}{\beta} \right) C_{be}}$$

$$f_{2out} = \frac{1}{2\pi (R_C \parallel R_L \parallel r_{ce}) (C_{bc} + C_{para})}$$

Wrocław University of Technology

High frequencies - sum up

f	CE	CC	CB
f_{2in}	\mathcal{X} $f_{2in} = \frac{1}{2\pi (R_G \parallel (R_E \parallel r_e)) C_w}$ $C_w = C_w + C_w (1 + A_v)$	\mathcal{X} $f_{2in} = \frac{1}{2 \cdot \pi \cdot R_G \parallel r_{ce} \left(C_w + \frac{C_{be}}{g_m \cdot r_{ce} \parallel R_E \parallel R_L} \right)}$	$f_{2in} = \frac{1}{2\pi \left(R_G \parallel \left(R_E \parallel \frac{r_{be}}{\beta} \right) \right) C_w}$
f_{2out}	$f_{2out} = \frac{1}{2\pi (R_C \parallel (R_L \parallel r_o)) (C_w + C_{para})}$	$f_{2out} \gg f_{2in}$	\mathcal{X} $f_{2out} = \frac{1}{2\pi (R_C \parallel (R_L \parallel r_{ce})) (C_w + C_{para})}$
Just about	$< f_T / \beta$	$< f_T$	$< f_T$

$$f_{2in} = \frac{1}{2\pi (R_G \parallel r_{be}) C_w}$$

$$f_2^{-1} \approx \sqrt{(f_{2in})^{-2} + (f_{2out})^{-2}}$$

$$f_{2out} = \frac{1}{2\pi (r_{ce} \parallel R_L) C_w}$$

NOTICE: in formulas do not included r_{bb} for h.f.

Wrocław University of Technology

Output BJT high frequencies

$$U_{in}^{\tau} = U_{in} \frac{R_2}{R_2 + R_1}$$

$$f_2 = \frac{1}{2\pi (R_1 \parallel R_2) C}$$

Wrocław University of Technology

High frequencies - sum up

f	CE	CC	CB
C_{in}	$C_{in} = C_{bc} + C_{bc}(1 + A_V)$	$C_{bc} + \frac{C_{bc}}{g_m \cdot r_{ce} \parallel R_E \parallel R_L}$	C_{bc}
C_{out}	$C_{bc} + C_{para}$	C_{para} $f_{2out} \gg f_{2in}$	$C_{bc} + C_{para}$
Just about	$-f_T / \beta$	$< f_T$	$-f_T$

$$f_{2in} = \frac{1}{2\pi (R_1 \parallel r_{in}) C_{in}}$$

$$f_{2out} = \frac{1}{2\pi (r_{out} \parallel R_L) C_{out}}$$

$$f_2^{-1} \approx \sqrt{(f_{2in})^{-2} + (f_{2out})^{-2}}$$

$C_{in} + C_{out} = \frac{2}{\beta} \cdot f_T$
 $g_m = \frac{I_{CQ}}{V_T}$

Uwaga: tabela nie uwzględnia r_{bb} , istotną przy dużych częstotliwościach

Wrocław University of Technology

CE-CC-CB comparison

$R_B = R_{B1} \parallel R_{B2}$ $r_{be} / \beta = 1 / g_m$

Parameter	configuration		
	CE	CC	CB
$A_V = \frac{u_{be}}{u_L}$	$-\beta \frac{R_C \parallel R_L \parallel r_{ce}}{r_{be}}$	$\frac{R_E \parallel R_L \parallel r_{ce}}{R_E \parallel R_L \parallel r_{ce} + r_{be} / \beta}$	$-\beta \frac{R_C \parallel R_L \parallel r_{ce}}{r_{be}}$
$A_I = \frac{i_b}{i_L}$	$\frac{-R_C \parallel r_{ce} - \beta}{R_C \parallel r_{ce} + R_L}$	$\frac{R_E}{R_E + R_L} \beta$	$\frac{-R_C \parallel r_{ce}}{R_C \parallel r_{ce} + R_L}$
$r_{in} = \frac{u_{be}}{i_{b(e)}}$	$R_B \parallel r_{be}$	$(\beta(R_E \parallel R_L) + r_{be}) \parallel R_B$	$\left(\frac{r_{be}}{\beta}\right) \parallel R_E$
$r_{out} = \frac{u_{out}}{i_{c(e)}}$ <small>(e) - for CB</small>	$R_C \parallel r_{ce}$	$\left(\frac{(R_B \parallel R_L) + r_{be}}{\beta}\right) \parallel R_E$	$R_C \parallel r_{ce}$

Wrocław University of Technology

CE-CC-CB general comparison

Parameter	configuration		
	CE	CC	CB
$A_V = \frac{u_{bc}}{u_L}$	High (10-200)	< 1	High (10-200)
$A_I = \frac{i_b}{i_L}$	High (10-200)	High (10-200)	< 1
$r_{in} = \frac{u_{bc}}{i_{b(e)}}$	Medium (0.5k-5k)	High (10k-1M)	Low (10Ω-500Ω)
$r_{out} = \frac{u_{out}}{i_{c(e)}}$ <small>(e) - for CB</small>	Medium (0.5k-5k)	Low (10Ω-500Ω)	Medium (0.5k-5k)

Wrocław University of Technology

Summary of BJT with feedback high frequencies

$\phi_s \approx 26mV$
 $U_T \approx 50 \div 300V$
 U_{CEQ}, I_{CQ} - Q-point
 β
 f_T - data sheet
 c_{bc}
 r_{bc} for $I_E, r_{be} = 0$

$S_{in} = \frac{r_{bc}}{\phi_s}$

$c_{bc} = \frac{S_{in}}{2 \cdot \pi \cdot f_T} - c_{bc}$

$c_{bc} = c_{bc} \frac{r_{bc}}{r_{bc} + (\beta + 1) R_E} + c_{bc} (1 + k)$

$k = \frac{R_C}{R_E}$

$r_{in} = R_{B1} \parallel R_{B2} \parallel [r_{bc} + R_E (\beta + 1)]$

$$f_{2in} = \frac{1}{2\pi C_{in} (r_{in} \parallel R_G)}$$

Wrocław University of Technology

Summary - cutoff frequencies

•RC circuits for high (f2) and low (f1) cutoff frequencies

$$f_{1in} = \frac{1}{2\pi (R_G + r_{in}) C_1}$$

$$f_{2in} = \frac{1}{2\pi (R_G \parallel r_{in}) C_{in}}$$

$$f_{1out} = \frac{1}{2\pi (r_{out} + R_L) C_2}$$

$$f_{2out} = \frac{1}{2\pi (r_{out} \parallel R_L) C_{out}}$$

f1 are limited by capacitors in series with in/out and sum of resistors

f2 are limited by capacitors in parallel with in/out and parallel connection of resistors

Problems

- Draw schematic diagram of BJT amplifier (transistor as model) showing cut-off frequencies elements
- Explain Miller effect.
- Estimate low- and high-cut off frequencies for given RC diagrams.
- Compare high cut-off frequencies for BJT in CE, CC, CB configurations.