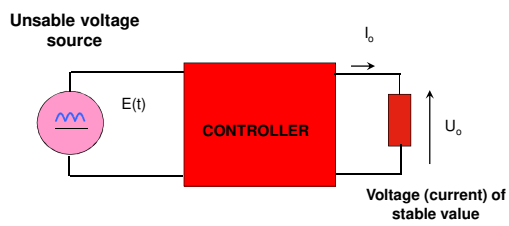


Power supply: - linear voltage (current) controllers.

Voltage controller



Parameters of voltage controllers (current)

- | | |
|---|---|
| <ul style="list-style-type: none"> • Input voltage • Range of input voltage • Nominal and maximum output current • Shortage current • Range of ambient temperature • Efficiency | <ul style="list-style-type: none"> • Output current • Of output voltage • Open voltage • Range of ambient temperature • Efficiency |
|---|---|

Basic parameters of linear voltage controllers

Load regulation
(dynamic output resistivity)

Long-term instability

$$\Delta U_o = \frac{\partial U_o}{\partial E} \Delta E + \frac{\partial U_o}{\partial I_o} \Delta I_o + \frac{\partial U_o}{\partial T} \Delta T + \frac{\partial U_o}{\partial t} \Delta t$$

Line regulation & ripple rejection

Output voltage temp. coefficient

Load regulation (output characteristics of the voltage stabilizer)

$$\frac{\partial U_o}{\partial I} \approx \frac{\Delta U_o}{I_{\max} - I_{\min}} \approx R_{\text{output}}$$

Line regulation (transfer characteristics of the voltage stabilizer)

$$E_{\min} - U_{o\min} \approx U_{\text{DROPOUT}} \quad \frac{\partial U_o}{\partial E} \approx \frac{\Delta U_o}{E_{\max} - E_{\min}}$$

Basic parameters of current controller

Line regulation
(dynamic output conductivity)

Long-term intability

$$\Delta I_o = \frac{\partial I_o}{\partial E} \Delta E + \frac{\partial I_o}{\partial U_o} \Delta U_o + \frac{\partial I_o}{\partial T} \Delta T + \frac{\partial I_o}{\partial t} \Delta t$$

Line rgulation & ripple rejtion


Output current temp coefficient

Parametric voltage controller

(outpu voltage depends of a „parameter” of the device)


Varistor
metal-oxide varistor (MOV) ZnO
Multi-layer varistor (MLV)

$$U = CI^{0.14 \div 0.5}$$

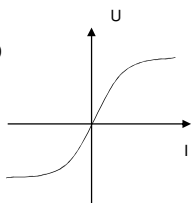


Parametric controller

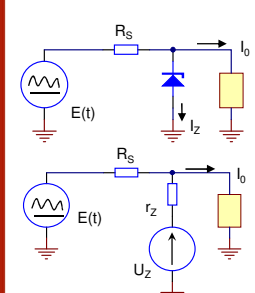(output voltage depends on a „parameter” of device - no active device)



Zener Diode

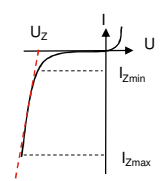

Zener Diode design


$I_z = E/R_s \text{ dla } I_o=0$


Zener Diode design load regulation


$\Delta U_o = \frac{\partial U_o}{\partial I_o} \Delta I_o = r_z \Delta I_o$

Zener Diode design line regulation

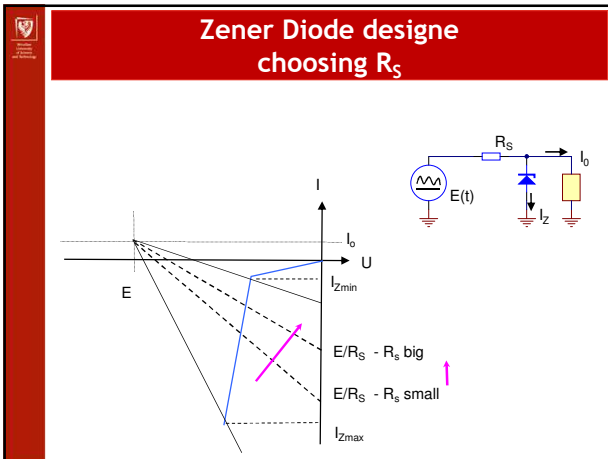$\Delta U_o = \frac{\partial U_o}{\partial E} \Delta E = \frac{r_z}{r_z + R_s} \Delta E$



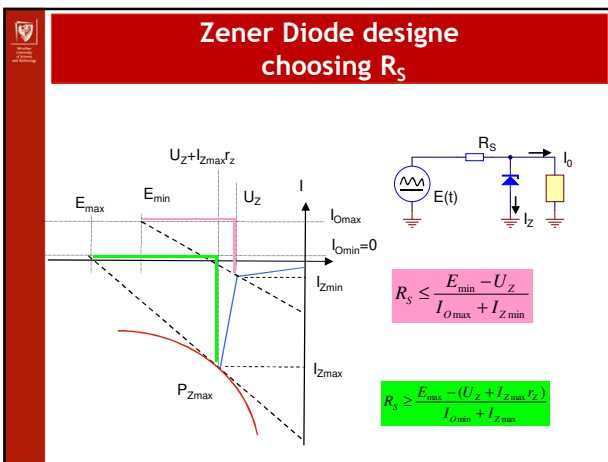

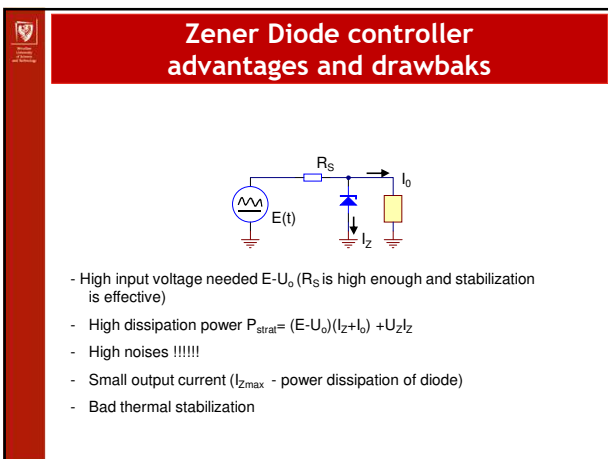

Zener diode parameters



$$\Delta U_o = \frac{\partial U_o}{\partial E} \Delta E + \frac{\partial U_o}{\partial I_o} \Delta I_o + \frac{\partial U_o}{\partial T} \Delta T + \frac{\partial U_o}{\partial t} \Delta t$$

$$\Delta U_o = \frac{r_z}{r_z + R_s} \Delta E + r_z \Delta I_o + (TWU_z) U_z \Delta T + \frac{\partial U_z}{\partial t} \Delta t$$


High R_s needed
So high E- U_o

Long term
stabilization

$$U_z = 10^{-3} + 10^{-5} [1/1000h]$$

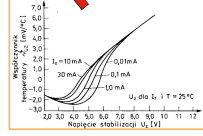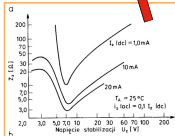

High power Zener diode

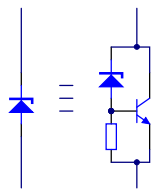


$$U_Z' = U_Z + U_{BE}$$

Follower (CC) as voltage controller

$$\Delta U_o = \frac{r_z}{r_z + R_s} \Delta E + \frac{r_z}{\beta} \Delta I_o + \left((TWU_z) U_z - \frac{\partial U_{BE}}{\partial T} \right) \Delta T + \frac{\partial U_z}{\partial t} \Delta t$$


R_s - can be higher

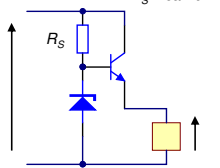


$$U_o = U_z - U_{BE}$$

Series vs parallel controller

$$I_I = I_Z + I_O$$

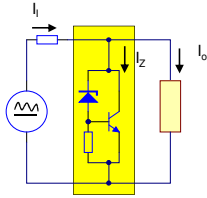


$$I_I \approx I_O$$

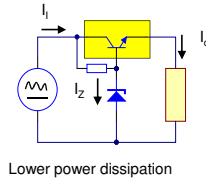

Reference voltage

- Zener Diode
- Compensated Zener Diode
 - Integrated diode
- Band gap („Base-emitter diode thermal compensated”)
- Zener diode with in thermostat

Thermal compensated Zener Diode

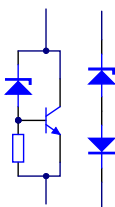

$$(TWU_Z)U_Z = 2mV / K \quad \text{for } U_Z = 6.9V$$

$$\frac{\partial U_Z}{\partial T} = -2mV / K$$




$$TWU_Z \approx 0$$


$$U_Z = 6.9V$$

Constant current required as thermal parameters of Zener Diode depends on current

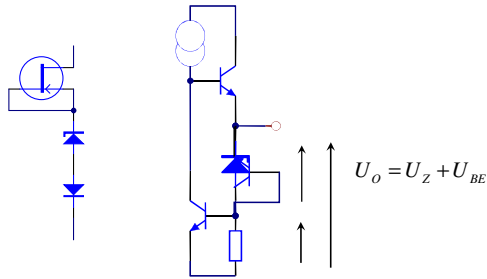
Dioda Zenera kompensowana termicznie przykład



$\frac{dU_D}{dT}$ as function of current

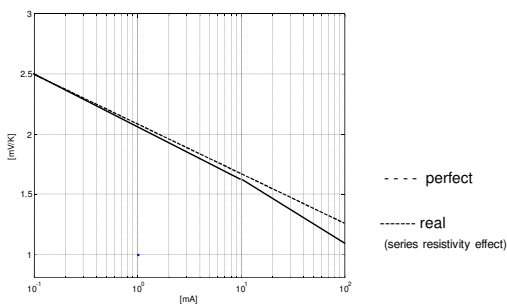

Temperature sensor

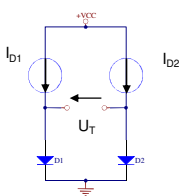

$$I_o = I_s \left(\exp\left(\frac{U_D}{n\phi_T}\right) - 1 \right) \quad \phi_T = \frac{kT}{e}$$

$$U_T = U_{D2} - U_{D1} = n\phi_T \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$

$$\frac{dU_T}{dT} = \frac{nk}{e} \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$

band-gap reference

$$\Delta U_{BE} = U_{BE1} - U_{BE2} = n \frac{kT}{e} \ln \left(\frac{I_2}{I_1} \right)$$

$$U_{REF} = \frac{R_2}{R_3} \Delta U_{BE} + U_{BE3}$$

$$\frac{\partial U_{REF}}{\partial T} = \frac{R_2}{R_3} n \frac{k}{e} \ln \left(\frac{I_2}{I_1} \right) + \frac{U_{BE3} - E_{GG} - 3\phi_T}{T} = 0$$

$$\frac{R_2}{R_3} n \frac{k}{e} \ln \left(\frac{I_2}{I_1} \right) = - \frac{U_{BE3} - E_{GG} - 3\phi_T}{T}$$

$U_{REF} \approx 1,25V$
Or 2,5V

Band-gap 2,5V

$U_{REF} \approx 2,5V$
Other brands possible


Reference voltage

- Zener Diode
- Compensated Zener Diode
 - Integrated diode
- Band gap („Base-emitter diode thermal s-compensated”)
- Zener diode with in thermostat


Voltage references(examples)

typ	U_{ref} [V]	I_{ref} [mA]	TWU [ppm/K]	Long term stab [ppm/1000h]	$\Delta U_{ref}/\Delta U_{ref}$ [% U_{ref} V]	$\Delta U_{ref}/\Delta I_O$ [% U_{ref} 10mA]	noise [μ V pp]
Thermal compensated Zener Diode							
LN821	6,2±5%	7,5	±100	-?			
LN4890	6,2±5%	7,5	±20	100			
Integrated Zener Diode							
μ A723	7,15±3%	1,6	50	1000	0,003	0,03	
LM329	6,9±5%	1	30	20	0,1		
REF08G	-10±0,2%	2	10		0,02	0,2	10
Band-gap							
REF05	5±0,3%	1	3	100	0,006	0,05	10
LM385-1.2	1,235±1%	0,01	30	20		0,8	60
LM385-2.5	2,5±1,5%	0,01	30			0,4	120
Zener Diode with termostate							
LM399	6,95±5%	1,7	0,3	20		0,1	
LIZ1000	7,2±4%	20	0,05	0,3			1,2


Compensated controller

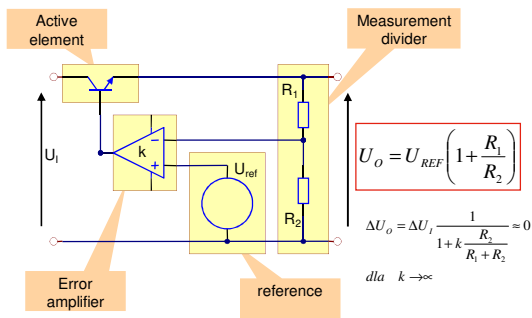

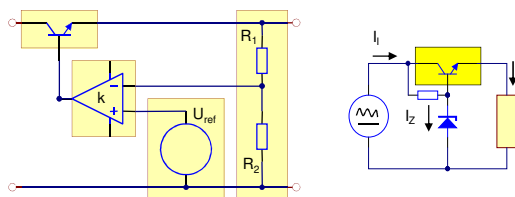
Most simple compensatet and series controller




Compensated controller 1

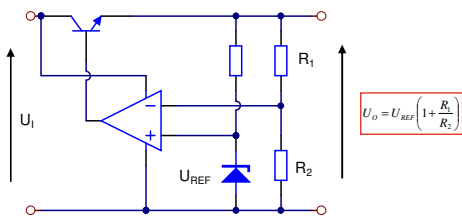

Compensated controller 2

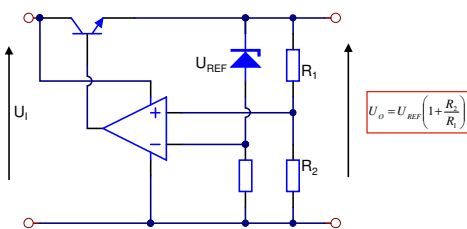

Protection circuits

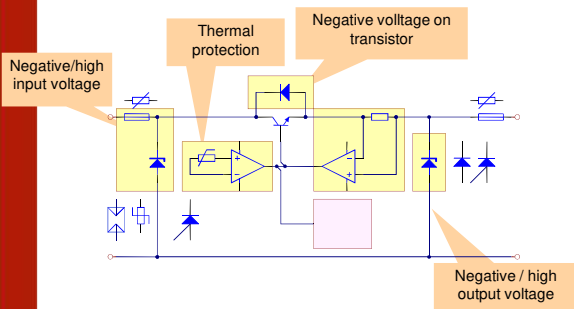


Devices in protection circuits


Protection devices:


- diode,
- Zener diode,
- transistor (uni- bi- directional),
- triac (thyristor),
- arrester,
- Fuse (fast or slow),
- Semiconductor fuse (PTC),
- other.....


Output current limiter (the simplest ?)

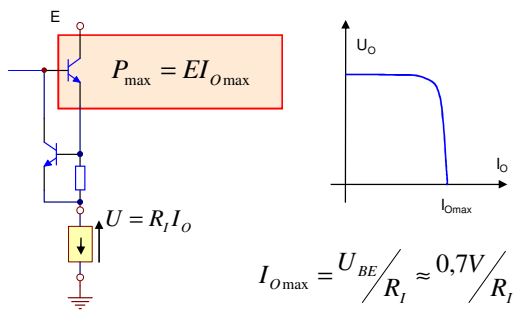


fold-back current limiter

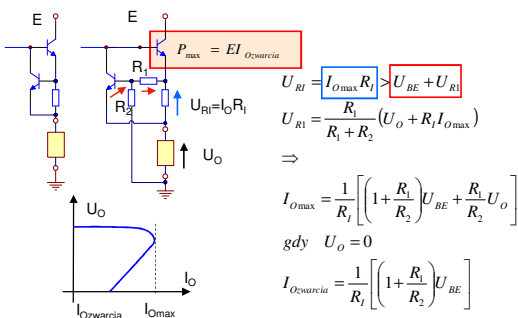

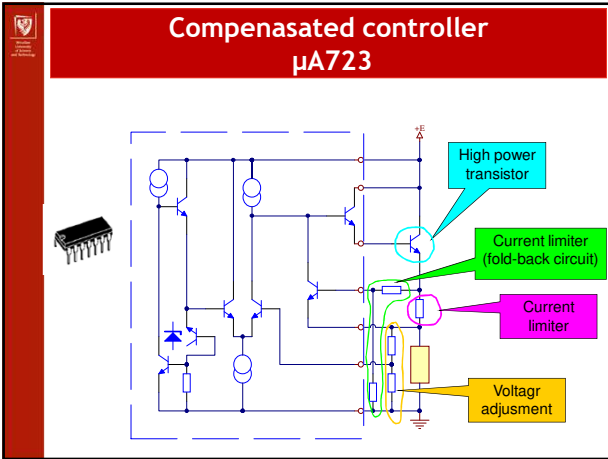

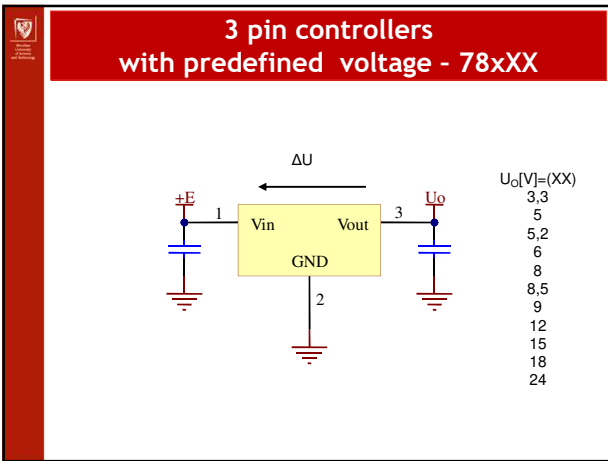

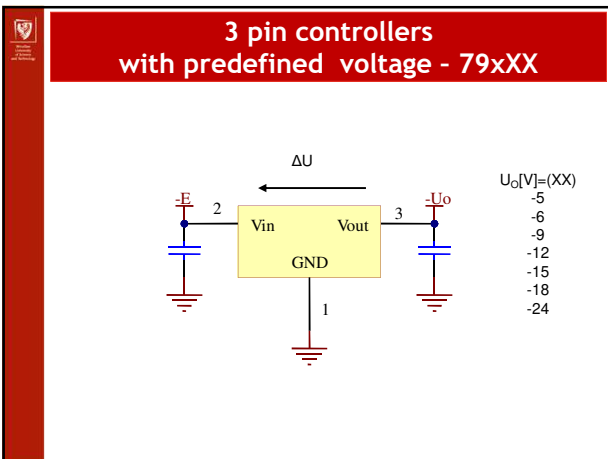


3 pin controllers with predefined voltage - 78XX


Main features:

- Input voltage- 35V(40V)
- Current limiter
0,1A/1A/3A (TO-92/TO-220/TO-3)
- Drop out voltage $\Delta U \approx 2V$
- Line / load regulation, thermal prop.
 - (not excellent)
- Temperature protection


Integrated circuits (examples)

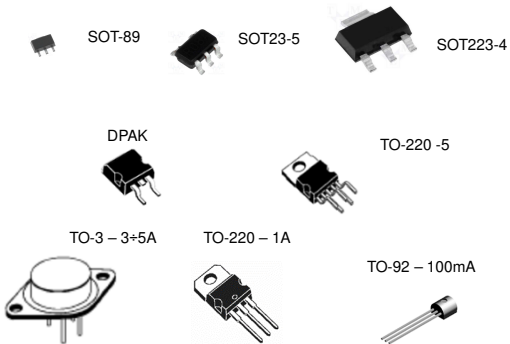

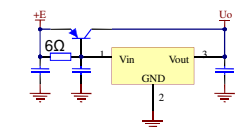3-pin controllers - extension possibilities




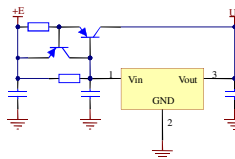Increased maximum current
-no current limiter
-higher dropout voltage




increased maximum current and current limiter
-higher dropout voltage

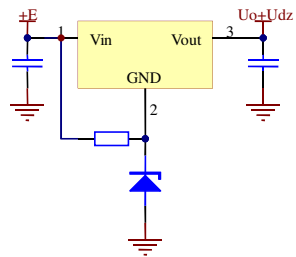Stabilizatory napięcia stałego - możliwości rozszerzenia zakresu zastosowań




Higher output voltage
- control parameters are like for Zener diode controller

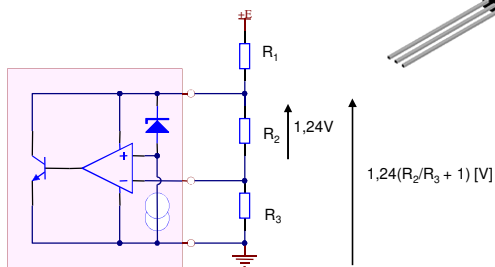
Adjusted reference voltage (parallel controller) LM385-ADJ



IC - adjustable controllers

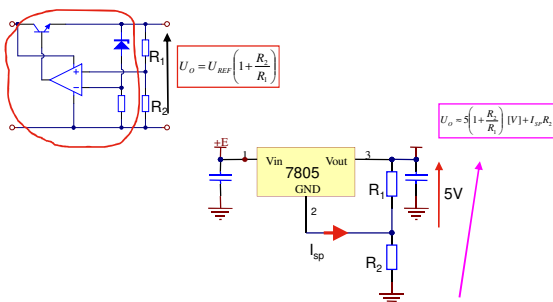


IC LM317 (positive voltage)

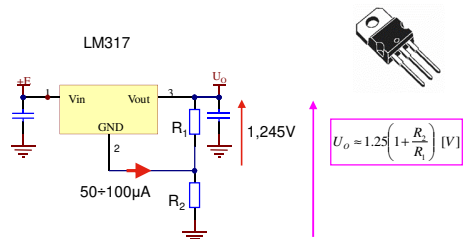


$$U_o = 1.25 \left(1 + \frac{R_2}{R_1} \right) [V]$$

IC LM337 (negative voltage)

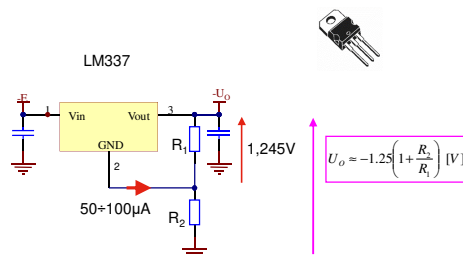

$$U_o = -1.25 \left(1 + \frac{R_2}{R_1} \right) [V]$$

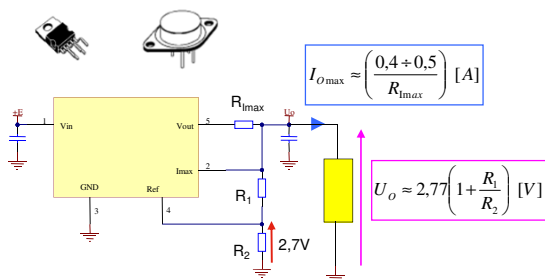
Integrated controller with adjustable voltage and maximum current - L200



$$I_{o\max} \approx \left(\frac{0.4 + 0.5}{R_{l\max}} \right) [A]$$

$$U_o \approx 2.77 \left(1 + \frac{R_1}{R_2} \right) [V]$$

Low DropOut (LDO) controllers

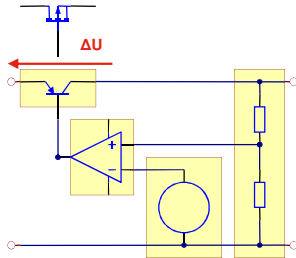


In typical controller $\Delta U > 2V$
 In LDO controller $\Delta U > 0,2 \div 0,5V$

IC controllers


typ	U_{max} [V]	U_O [V]	ΔU_{load} [V]	I_{Omax} [A]	$I_{quidmax}$ [mA]	TWU [ppm/K]	Long term stab [%/1000h]	$U_O/\Delta U_{in}$ [%/V]	$\Delta U_O/\Delta U_O$ [Ω]
Universal controllers									
μA723	40	2.36	2	0,065A	±100	20	0,001	0,003	0,04
L300	40	2.8-3.6	2	3,6A	4.3	10	-	0,001	0,002
LM317/337T	40	1.2-3.7	2	1.5		600	0.3	0.01	0.003
Constant voltage									
LM78L05	35	5±4%	2	0.1	4	300	0.4	0.09	0.01
LM7812	35	12±4%	2	1	4	300	0.4	0.06	0.01
LM7815CT	35	15±4%	2	2	4	300	0.4	0.03	0.01
Negative voltage									
LM7905	-35	-5±4%	2	1	4	300	0.4	0.09	0.01
LDO controllers									
LM2340-05	35	5±4%	0.5	1	4	300	0.4	0.09	0.01


a)- no external transistor and no current limiter


Some „tips” „dual tracking regulator”

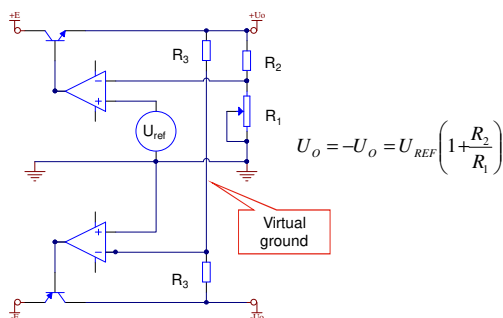

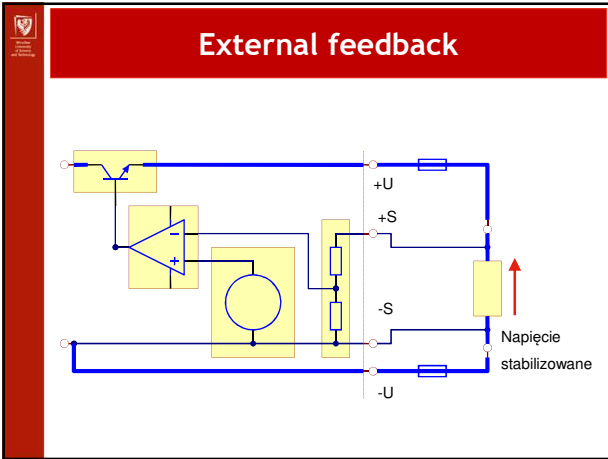
$$U_O = -U_O = U_{REF} \left(1 + \frac{R_2}{R_1} \right)$$



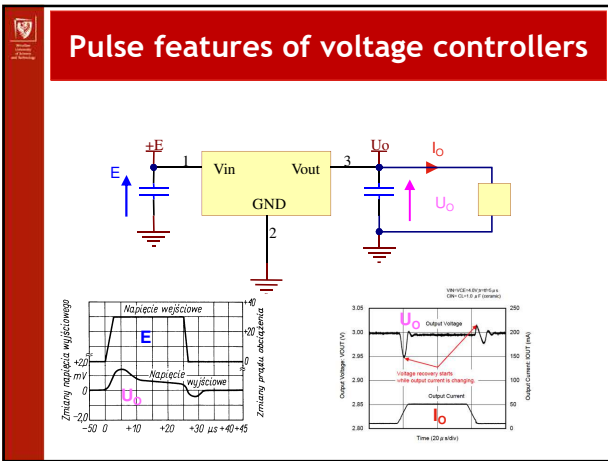

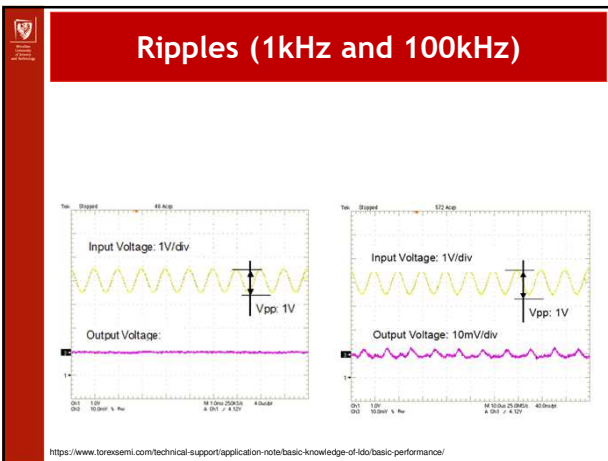

Pulse features of voltage controllers

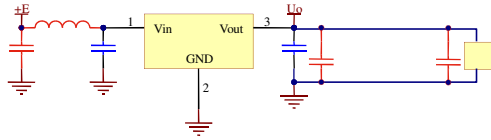


Minimizing the effects of input voltage ripples:

- additional filter (C, L etc.)
- other dumping elements (e.g. transistor)
- additional voltage controller


Minimizing the effects of load current jumps:

- reduction of the output impedance by adding capacitors with low impedance for high frequencies
- capacitors in parallel with elements that sink pulsed current


Current controllers

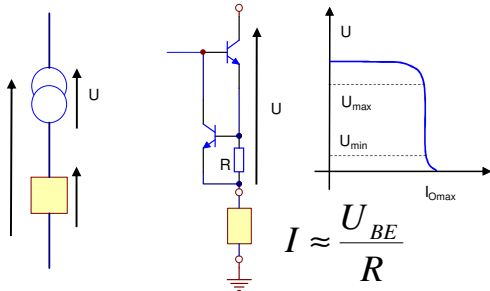

Current controllers

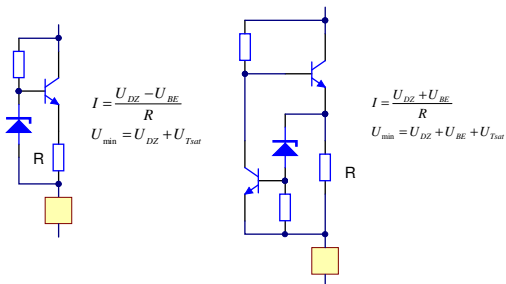

Current controllers

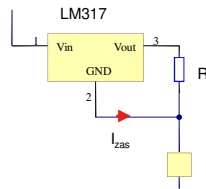

$$I \approx \frac{1,25V}{R} + I_{zas}$$
$$U_{\min} \approx 1,25 + 2 = 3,25V$$

summary

- Parameters of voltage controllers (line, load regulation - characteristics)
- Parametric controllers with Zener Diodes
- Reference voltage sources
- Idea of compensated controller
- Protection methods in voltage controllers
- Parameters of integrated voltage controllers
- Current controllers

Final test problems

- Idea of series and parallel controller.
- Idea of a simple current limiter (with transistor).
- Idea of „fold-back” current limiter.
- Line and Load regulation curves. What kind of parameters can be read from these graphs ?
