



Wrocław
University
of Science
and Technology

DC-DC converters DC-DC controllers

Jerzy Wroblewski






Serial & parallel controller

$$I_I = I_Z + I_o$$

$$P_{loses} = I_Z U_o + I_I (E - U_o)$$

$$I_I \approx I_o$$

$$P_{loses} = I_I (E - U_o)$$

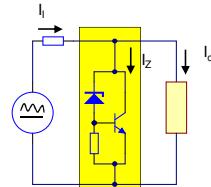


Smaller dissipation power
Better efficiency






Linear vs. Pulse (switching) controller

$$P_{strat} \approx (E - U_o) I_o$$

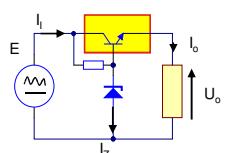

Smaller dissipation power
Better efficiency

$$P_{strat} \approx U_{sat} I_{max}$$

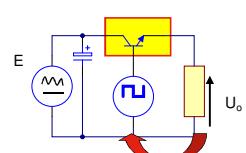


$$U_o = U_{AV} = \frac{t_{on}}{t_{on} + t_{off}} E$$

Even smaller dissipation power
Even better efficiency






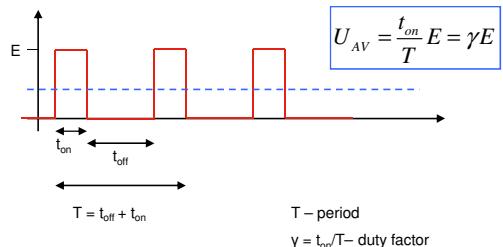The average value of the impulse waveform




Step down converter

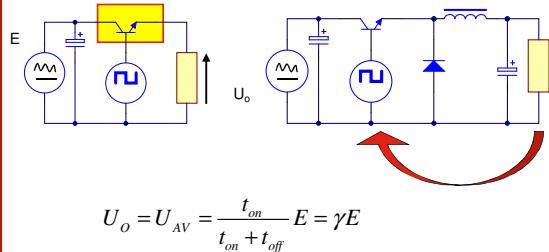

$$U_o = U_{AV} = \frac{t_{on}}{t_{on} + t_{off}} E = \gamma E$$



Choke

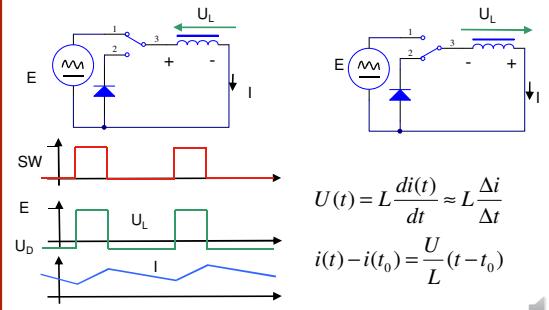


$$U(t) = L \frac{di(t)}{dt} \approx L \frac{\Delta i}{\Delta t}$$


$$i(t) - i(t_0) = \frac{U}{L} (t - t_0)$$



Choke

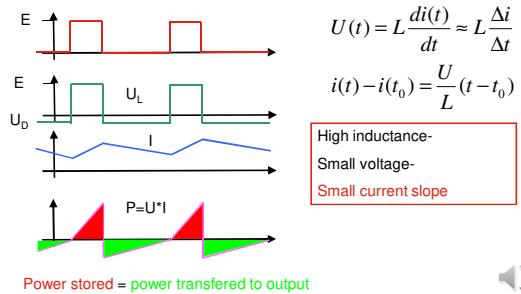

Choke - some parameters

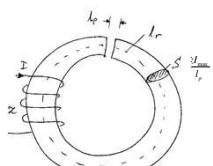

$B_{\max} = 0.05 \dots 0.1 \dots 0.2 \dots 0.3$ [T] for ferrites
and frequencies 200...20..10[kHz]..2[MHz]

when $\mu_r / l_p \gg 1$

$$\frac{BSz}{I} = L = \mu_0 \mu_r \frac{z^2 S}{l_r \left(1 + \mu_r \frac{l_p}{l_r} \right)} = A_t z^2 \approx \mu_0 \frac{z^2 S}{l_p}$$

For sine waveforms:


$$\frac{U_{\max}}{z} = 2\pi f B_{\max} S = \frac{\sqrt{2} U_{\text{skew}}}{z}$$

For square wave:

$$\frac{U_{\max}}{z} = \frac{1}{\gamma} f B_{\max} S = \frac{1}{t_{on}} B_{\max} S$$



Step down (buck) converter

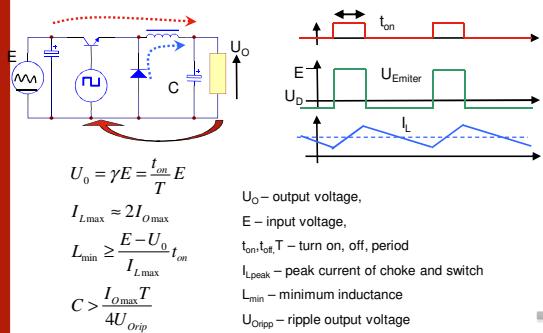




simplified way of deriving equation of the output voltage of the step-down converter

chalk board or separate video





Step down converter (discontinous mode)

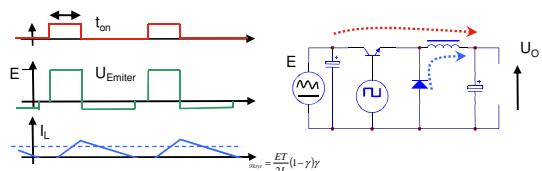


Output voltage can reach the value E !!!






self-excited step-down controller

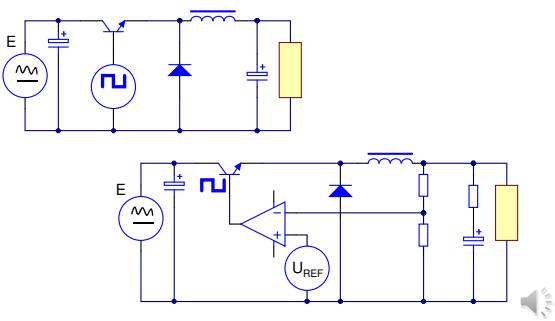


Step up (boost) converter

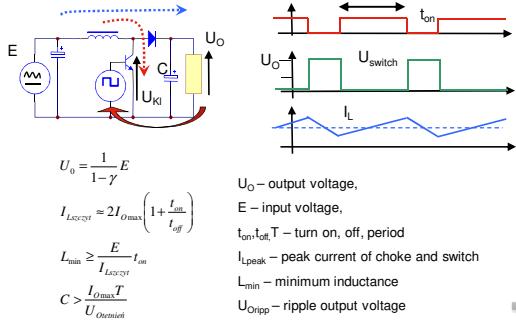

**simplified way of deriving equation
of the output voltage of the step-up
converter**

chalk board or separate video

Inverter
(buck-boost)

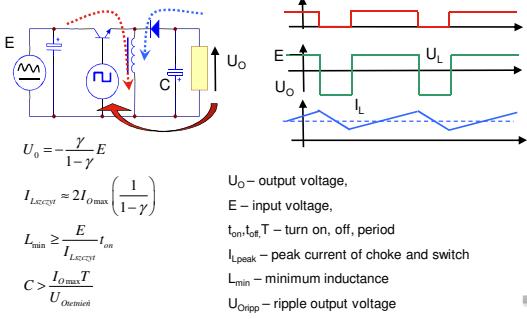




simplified way of deriving equation of the output voltage of the inverter

chalk board or separate video






Inverter

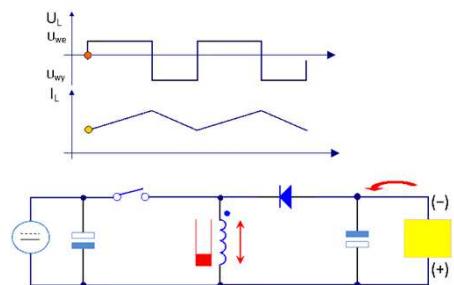



Inverter (discontinuous mode)

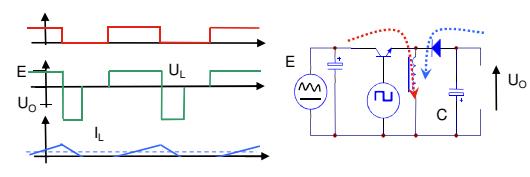


$$I_o < I_{okryt} = \frac{E\gamma}{2L}(1-\gamma)T$$


Output voltage can ??? ∞ !!!




Step up MC34063

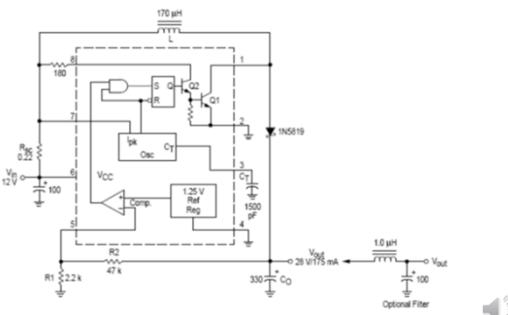

Inverting MC34063

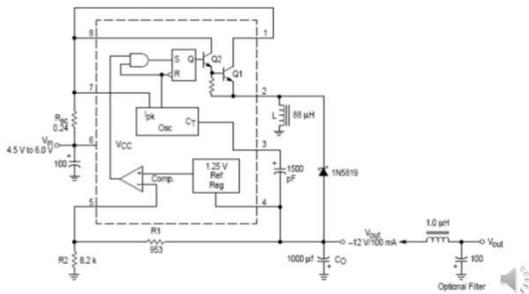

Step down MC34063

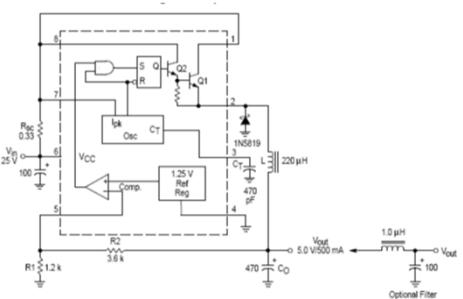



MC34063 data sheet expressions

Calculation	Step-Up	Step-Down	Voltage-Inverting
$t_{on}+t_{off}$	$\frac{V_{out}-V_F-V_{(min)}}{V_{(min)}-V_{sat}}$	$\frac{V_{out}-V_F}{V_{(min)}-V_{sat}-V_{out}}$	$\frac{V_{out}+V_F}{V_{in}-V_{sat}}$
$(t_{on}+t_{off})$	$\frac{1}{f}$	$\frac{1}{f}$	$\frac{1}{f}$
t_{off}	$\frac{t_{on}+t_{off}}{t_{on}+1}$	$\frac{t_{on}+t_{off}}{t_{on}+1}$	$\frac{t_{on}+t_{off}}{t_{on}+1}$
t_{on}	$(t_{on}+t_{off})-t_{off}$	$(t_{on}+t_{off})-t_{off}$	$(t_{on}+t_{off})-t_{off}$
C_T	$4.0 \times 10^{-5} t_{on}$	$4.0 \times 10^{-5} t_{on}$	$4.0 \times 10^{-5} t_{on}$
$I_{pk(\text{switch})}$	$2I_{\text{out(max)}} \left(\frac{t_{on}}{t_{off}} + 1 \right)$	$2I_{\text{out(max)}} \left(\frac{t_{on}}{t_{off}} + 1 \right)$	$2I_{\text{out(max)}} \left(\frac{t_{on}}{t_{off}} + 1 \right)$
R_{SC}	$0.3 I_{pk(\text{switch})}$	$0.3 I_{pk(\text{switch})}$	$0.3 I_{pk(\text{switch})}$
$L_{(min)}$	$\left(\frac{(V_{(min)} - V_{sat})}{I_{pk(\text{switch})}} \right) t_{on(\max)}$	$\left(\frac{(V_{(min)} - V_{sat} - V_{out})}{I_{pk(\text{switch})}} \right) t_{on(\max)}$	$\left(\frac{(V_{(min)} - V_{sat})}{I_{pk(\text{switch})}} \right) t_{on(\max)}$
C_O	$9 \frac{I_{pk(\text{switch})} t_{on}}{V_{\text{ripple(pp)}}}$	$I_{pk(\text{switch})} (t_{on} + t_{off})$	$9 \frac{I_{pk(\text{switch})} t_{on}}{V_{\text{ripple(pp)}}}$

V_{sat} = Saturation voltage of the output switch.

V_F = Forward voltage drop of the output diode.

The following power supply characteristics must be chosen:

$V_{in} = \text{Desired output voltage}, V_{in} = 1.25 \left(1 + \frac{R_L}{R_{load}} \right)$


$I_{out} = \text{Desired output current}$

$f_{switch} = \text{Output switching frequency at the selected values of } V_{in} \text{ and } I_{out}$


$V_{\text{ripple(pp)}} = \text{Desired peak-to-peak output ripple voltage. In practice, the calculated capacitor value will need to be increased due to the equivalent series resistance and board spread. The ripple voltage should be kept to a low value since it will directly affect the line and load regulation.}$



Choke converter (flyback)


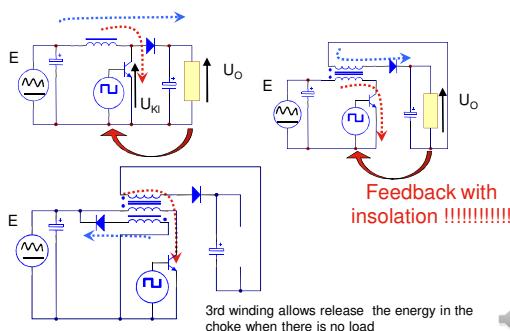


Flyback vs. Forward converter


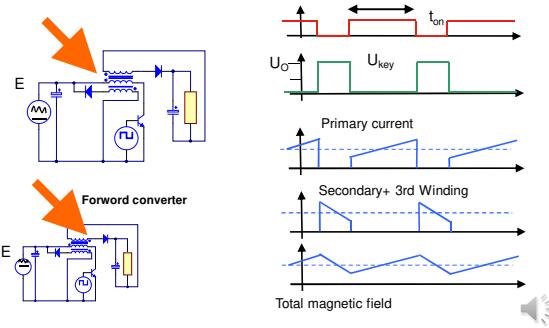


forward converter

Flyback converter

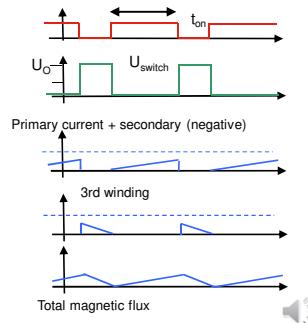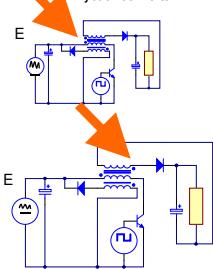

Choke vs. transformer

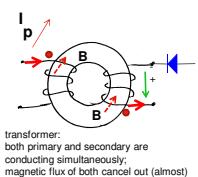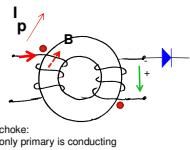


Foreword converter

- In foreword converters:
- Energy is „transformed” (is not stored in magnetic field)
- Magnetization current is small
- Instead of choke a smaller transformer is used
- In symmetrical (push-pull, half-bridge, full-bridge, foreword converters average magnetization current is zero !





High power converters (foreword)

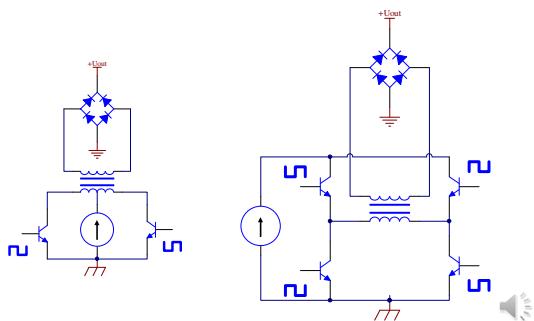



Converters - problems to overcome

High frequency (10-200kHz-2MHz) and short switching times (10-200ns):

- fast diodes and transistors
- distortions - noises
- voltage spikes
- parasitic capacitances (resonances)
- skin effect

Additional reference:
I. Pressman, Switching Power Supply Design 3/e, McGraw-Hill Education Ltd.





Summary

Advantages:

- High efficiency
- Small dimensions

Drawbacks:

- Worse line and load regulation
- Interferences
- More expensive

Capacitive converters (charge pump) - for self studies (n. ICL7660)





Test problems

- simplified derivation of the output voltages for:
 - Step down (buck) converter
 - Step up (boost) converter
 - Inverter (buck-boost)
- Drawbacks and advantages of DC-DC converters