




Wrocław University of Technology

Sin -wave oscillators



Wrocław University of Technology

Loop gain and phase

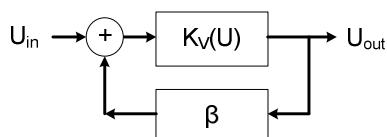


$$(U_{in} + \beta U_{out})K_V(U) = U_{out}$$

$$U_{out} = \frac{K_V(U)}{1 - K_V(U)\beta} U_{in}$$



Wrocław University of Technology

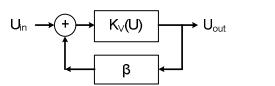Oscillations - positive feedback (Barkhausen's criterion)



$$U_{out} = \frac{K_V(U)}{1 - K_V(U)\beta} U_{in}$$

$$1 = K_V(U)\beta = |K_V(U)\beta|e^{j(\varphi_K + \varphi_\beta)}$$

$$|K_V(U)\beta| = 1 \quad \text{AMPLITUDE condition}$$

$$\varphi_K + \varphi_\beta = n \cdot 360^\circ \quad \text{PHASE condition } (n=0,1,2..)$$





Phase and Amplitude conditions

$$|K_V(U)\beta|=1$$

usually $|K_V(U)\beta| > 1$
U increases $\rightarrow K_V(U)$ decreases
so:
amplitude of oscillation is limited


$$\varphi_K + \varphi_\beta(f) = n \cdot 360^\circ$$

so:
frequency of oscillation is adjusted






Wien-bridge oscillator

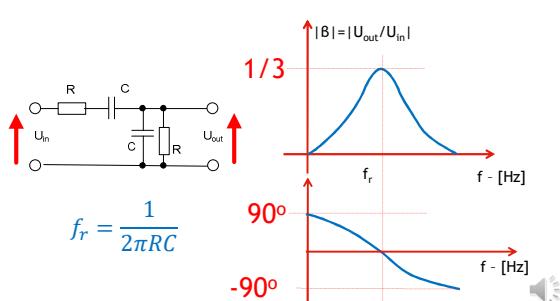




Wien oscillator

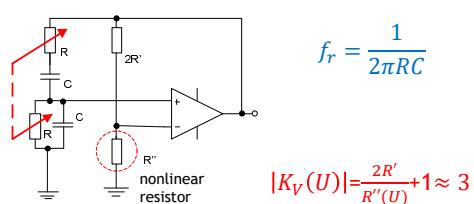




Wien oscillator - automatic gain control

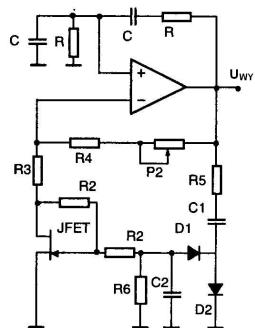




Twin-T filter

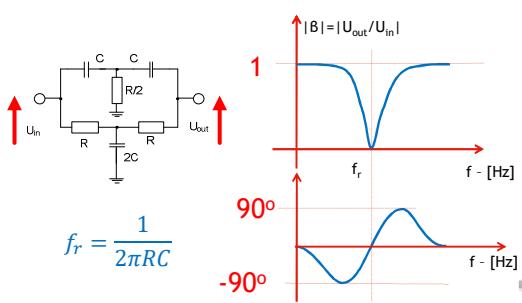



Twin- T oscillator

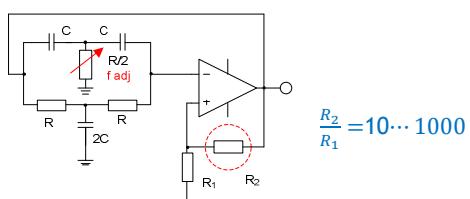


$$\frac{R_2}{R_1} = 10 \dots 1000$$





Phase-Shift oscillators

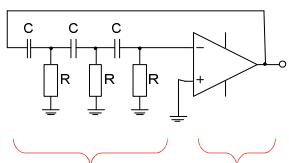


$$f_r = \frac{1}{2\pi RC\sqrt{6}}$$

$\varphi_B = 180^\circ$ $K_v > 30$





Phase-Shift oscillators

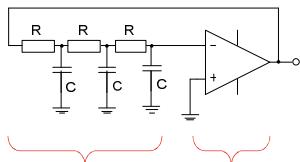


$$f_r = \frac{1}{2\pi RC\sqrt{6}}$$

$\varphi_B = 180^\circ$ $K_v > 30$






LC oscillators resonant circuit (serial)

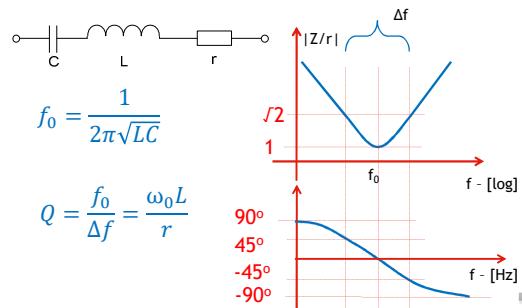


LC oscillators resonant circuit (serial)

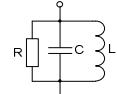


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
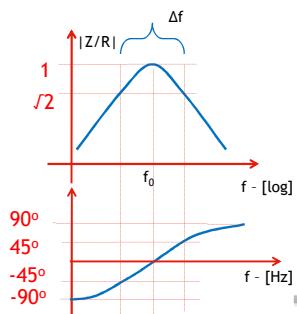
$$Q = \frac{f_0}{\Delta f} = \frac{R}{1/\omega_0 C}$$



Meissner (Armstrong) oscillator

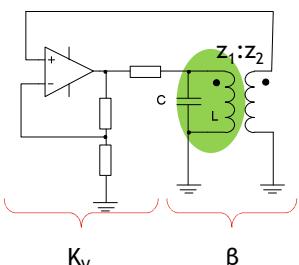


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\beta(f_0) = \frac{z_1}{z_2}$$

$$K_{Vmin} = \frac{z_2}{z_1}$$

MEISSNER

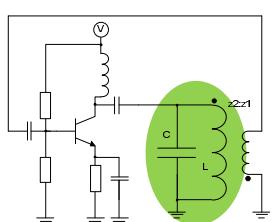


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\beta(f_0) = \frac{z_1}{z_2}$$

$$K_{Vmin} = \frac{z_2}{z_1}$$



Hartley oscillator

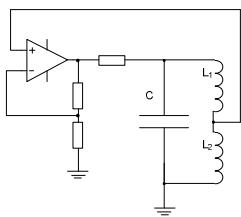


$$f_0 = \frac{1}{2\pi\sqrt{(L_1+L_2)C}}$$

$$\beta(f_0) = \frac{L_2}{L_1 + L_2}$$

$$K_{Vmin} = \frac{L_1 + L_2}{L_2}$$



Hartley oscillator

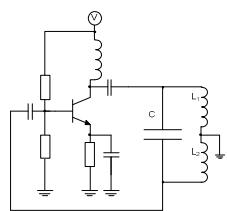


$$f_0 = \frac{1}{2\pi\sqrt{(L_1+L_2)C}}$$

$$\beta(f_0) = \frac{L_2}{L_1 + L_2}$$

$$K_{Vmin} = \frac{L_1 + L_2}{L_2}$$



Colpitts oscillator

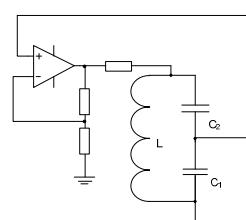

$$f_0 = \frac{1}{2\pi\sqrt{L\frac{C_1C_2}{C_1+C_2}}}$$


$$\beta(f_0) = \frac{C_2}{C_2 + C_1}$$

$$K_{Vmin} = \frac{C_2 + C_1}{C_2}$$





Colpitts oscillator

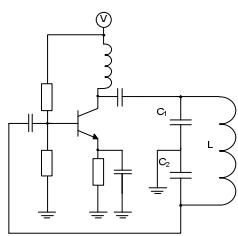

$$f_0 = \frac{1}{2\pi\sqrt{L\frac{C_1C_2}{C_1+C_2}}}$$


$$\beta(f_0) = \frac{C_2}{C_2 + C_1}$$

$$K_{Vmin} = \frac{C_2 + C_1}{C_2}$$






Colpitts oscillator

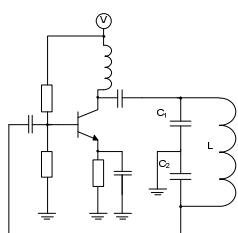

CE

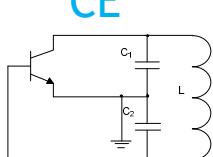



CE, CC, CB amps in oscillators

CE




Grounded E

CB

Grounded B




CC

Grounded C

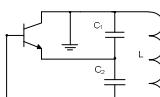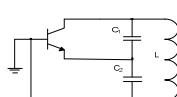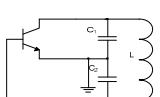




FET amps as oscillators CG, CD, CS

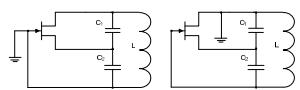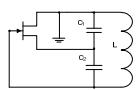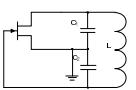CG**CD****CS**

Clapp oscillator

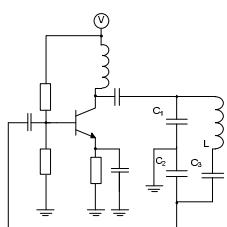

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$



$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\beta(f_0) = \frac{C_2}{C_2 + C_1}$$

$$K_{Vmin} = \frac{C_2 + C_1}{C_2}$$




Quartz (crystal) oscillator Clapp

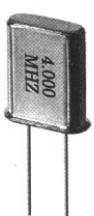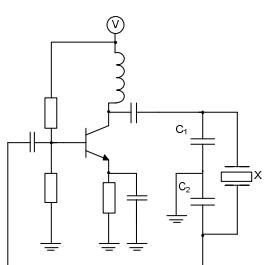





Crystal equivalent circuit


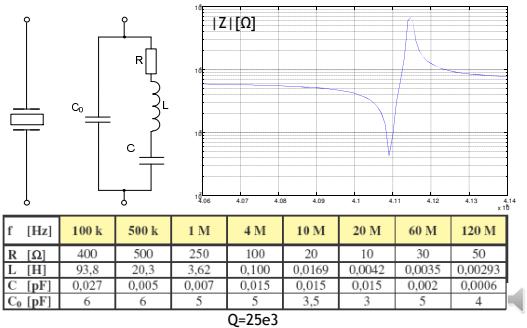


$|Z(f)|$

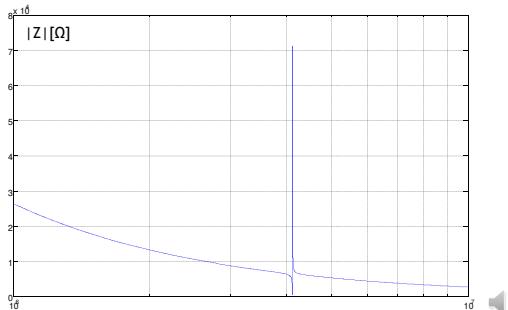

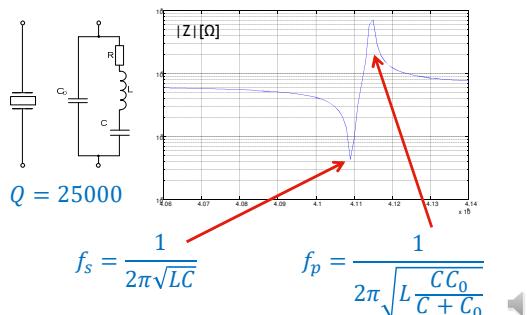
Series and Parallel resonance of a crystal resonator of 4MHz



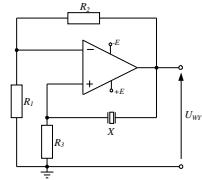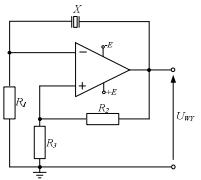fs - $|z| = \text{min}$ fp - $|z| = \text{max}$ 




series resonans

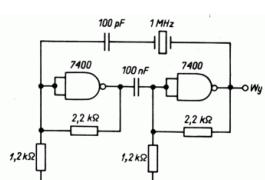



Pirce oscillator - an example

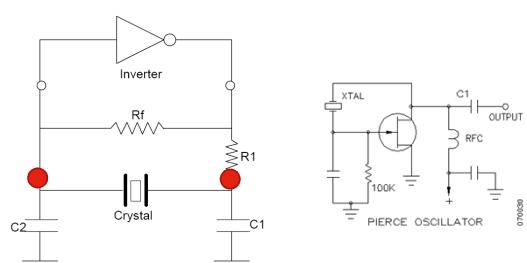



Frequency stability

$$f_0(t) = f_0 \pm \Delta f_0$$

$$S = \frac{\Delta f_0}{f_0} / 24h$$

Type of oscillator	Stability
RC	10e-2 - 10e-3
LC	10e-3 - 10e-4
Crystal	10e-6 - 10e-7
Crystal (temp. stab.)	(10e-8 - 10e-10)
Atomic references	10e-12 - 10e-14





Features of oscillators

- frequency stability
- harmonics (THD)
- frequency range
- amplitude and phase noise (jitter)





Summary

- amplitude and phase conditions of oscillation
 - Wien bridge generator
 - Twin - T filter and oscillator
 - RC phase shifter oscillators
- Meissner, Hartley, Colpits oscillators - topologies
- crystal (quartz) - parallel and series resonances, model, $|Z(f)|$ -graph
- frequency stability and other parameters of generators







Flip-Flops and multivibrators



BJ-Transistor as a switch

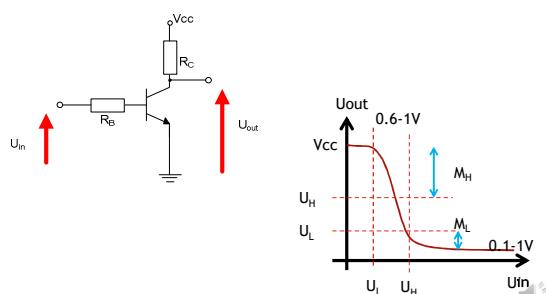


MOSFE-Transistor as a switch

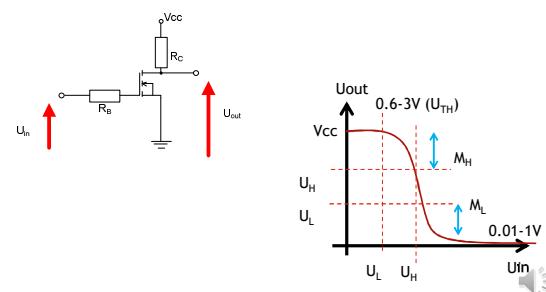




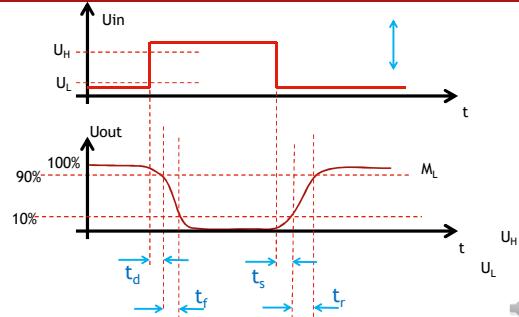Dynamic features delay-, fall-, storage-, rise-time






Dynamic features propagation delay time

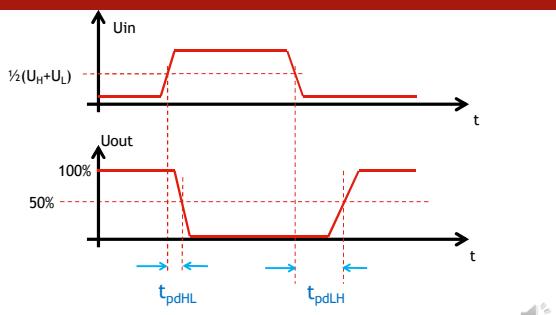





RS flip-flop


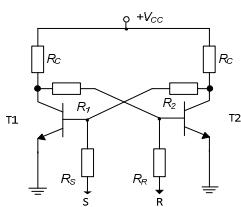






Astable Flip-Flop

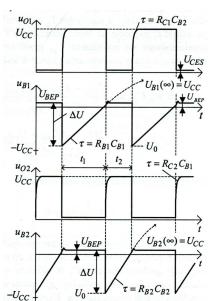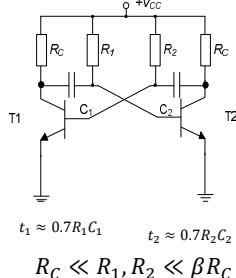

OpAmp(Comparator) Flip-Flop

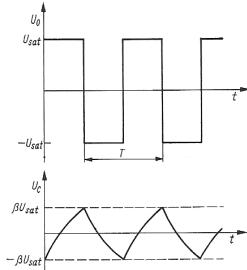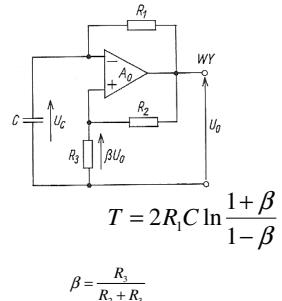


Astable Flip-Flop with NAND Gate

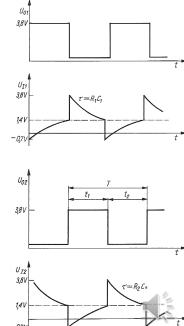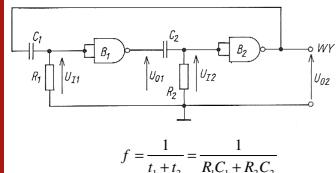




Timer „555” - monostable mode

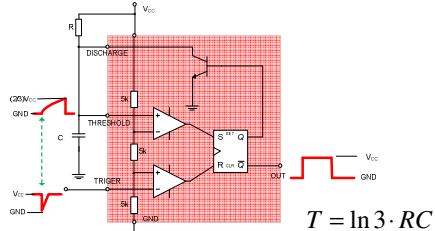




Timer „555” - astable mode

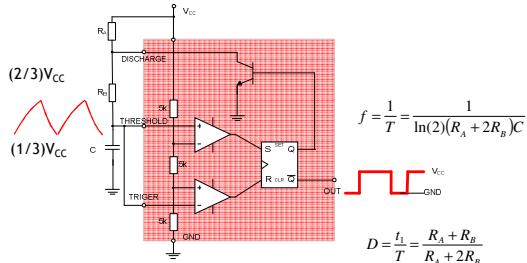



VCO F-F - Emitter coupling

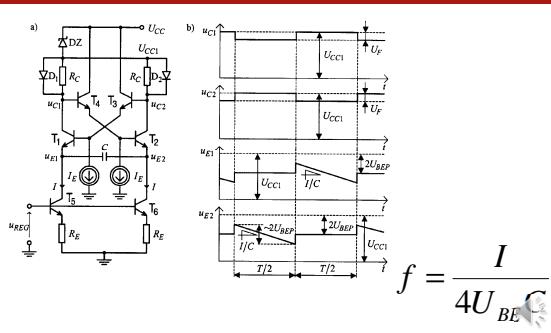




Wrocław University of Technology


Emitter coupled Voltage-controlled multivibrator MC4024

CIRCUIT SCHEMATIC

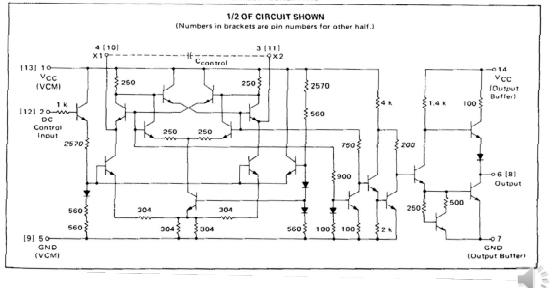1/2 OF CIRCUIT SHOWN
(Numbers in brackets are pin numbers for other half.)


Wrocław University of Technology

Sine, Triangle, Square generator

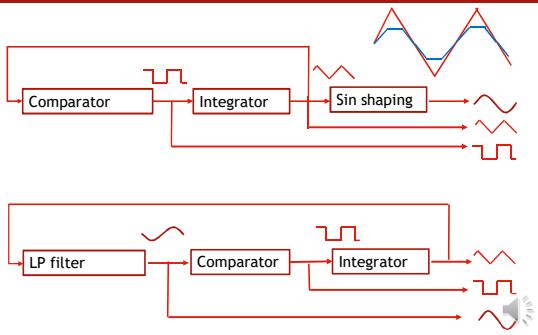

Wrocław University of Technology


Sine, Triangle, Square generator -IC

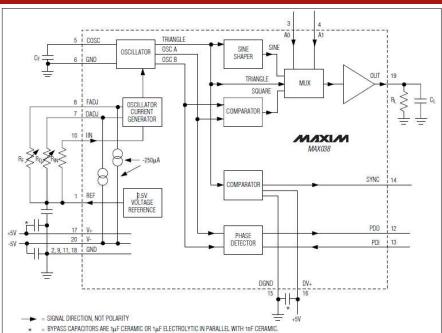




Wrocław University of Technology

Sine, Triangle, Square generator -IC

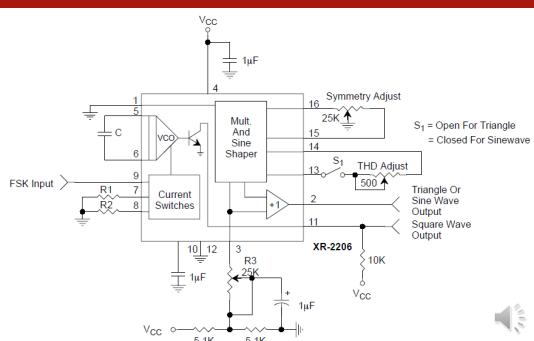


Wrocław University of Technology


Sine, Triangle, Square generator -IC

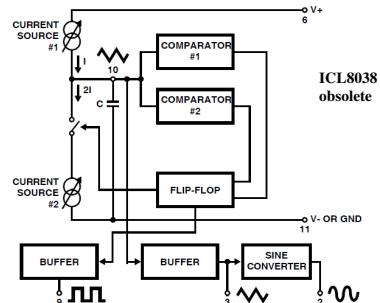

Wrocław University of Technology

DDS - Direct Digital Synthesis

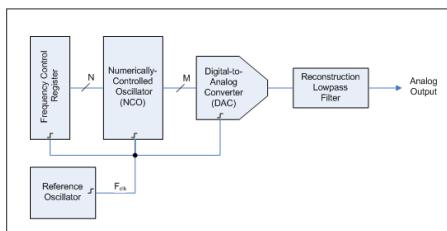

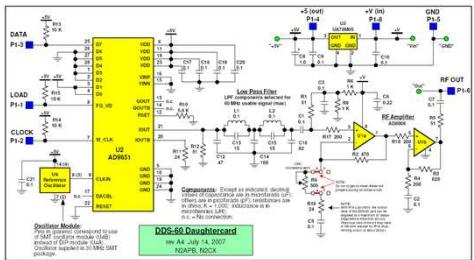

Summary

- Flip-Flop as a-stable and mono-stable
 - Timer 555
 - Function generator
 - DDS, arbitrary generator

