



Wrocław
University
of Science
and Technology

Analog multipliers



General

$$u_{out} = k_m u_x u_y = \frac{u_x u_y}{E_R}$$

u_x, u_y – input voltages,
 $k_m = 1/E_R$ – scale constant,
 E_R – standarization voltage e.g. +10V, -10V.



General types of input ranges

- one-quadrant – u_x and $u_y > 0$,
- two-quadrant – $u_x > 0$ and $u_y >= 0$,
- four-quadrant – u_x and $u_y >= 0$,



Types - principles

- Modulation (+voltage variable resistors),
- logarithmic amplifiers,
- squarer,
- transconductance.



Errors

$$u_{out} = \frac{u_x u_y}{E_R} + \Delta = \frac{u_x u_y}{E_R} (1 + \delta_0)$$


Δ, δ_0 – absolute and relative error.

Parameters:

- f_{3dB} – cut off frequency ????,
- f_a – 1% error frequency of amplitude,
- f_ϕ – 1% error of phase,
- SR – slew rate




Pulse with modulation multiplier

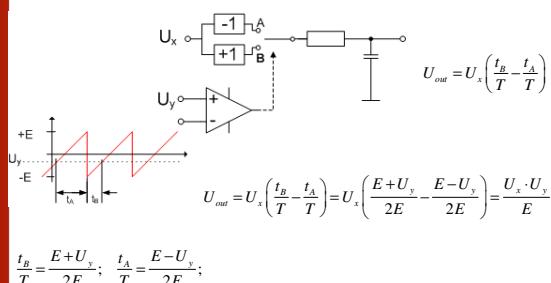



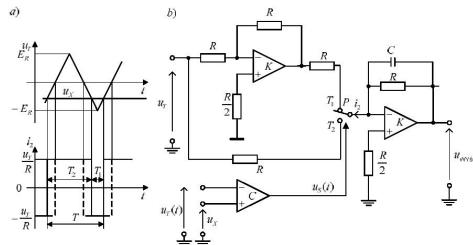Pulse with modulation multiplier practical example



Pulse with modulation multiplier

$$u_s(t) = \begin{cases} U_{s\max} & \text{dla } u_x > u_T \\ U_{s\min} & \text{dla } u_x < u_T \end{cases}$$

$$\frac{u_x}{E_R} = \frac{2T_1}{T} - 1$$

$$u_{out} = \left(\frac{2T_1}{T} - 1 \right) u_y = \frac{u_x u_y}{E_R}$$



Pulse with modulation multiplier properties

High accuracy: $\delta_0 = (0.01 \dots 0.1 \%)$, $f_{3dB} = 1\text{kHz}$, $SR < 0.7\text{V/ms}$.

Limitations:

- Turn on and off of the switch should be much smaller than the period,
- frequency of low-pass filter much smaller than the working frequency.

General:

- High accuracy
- Small bandwidth
- Complicated - expensive




Logarithmic - exponential amplifiers

$$u_{wy} = E_R e^{\left(\ln \frac{u_x}{E_R} + \ln \frac{u_y}{E_R} \right)} = e^{\left(\frac{\ln u_x u_y}{k_E E_R} \right)} = \frac{u_x u_y}{E_R}$$

dla $u_x, u_y > 0$




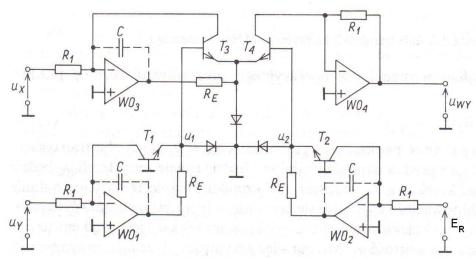Logarithmic - exponential amplifiers example





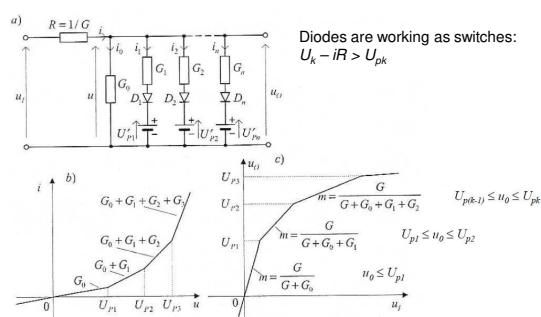Logarithmic - exponential amplifiers arbitrary function amplifier






Multipier with logarithmic - exponential amplifiers

$$u_{wy} = \exp(\ln u_x + \ln u_y - \ln E_R) = \frac{u_x u_y}{E_R} \quad \text{dla } u_x, u_y, E_R > 0$$

One-quadrant multiplier.



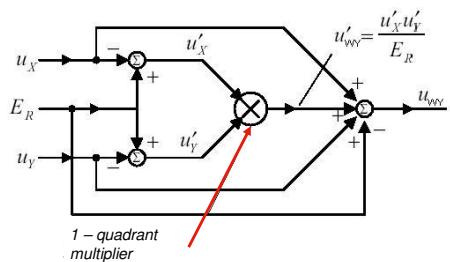Logarithmic - exponential amplifiers 4- quadrant extention





Logarithmic - exponential amplifiers 4- quadrant extention

$$\text{for } E_R > 0, \quad \dot{u}_{out} = \frac{\dot{u}_x \dot{u}_y}{E_R}$$

where:

$$\dot{u}_x = E_R - u_x > 0$$

$$\dot{u}_y = E_R - u_y > 0$$

$$\dot{u}_{out} = \frac{(E_R - u_x)(E_R - u_y)}{E_R} = E_R - u_x - u_y + \frac{u_x u_y}{E_R}$$

finally:

$$u_{out} = \dot{u}_{out} - E_R + u_x + u_y = \frac{u_x u_y}{E_R}$$



Układy mnożące wykorzystujące operacje: logarytmiczną i wykładniczą

Input voltage range: $\pm 10V$


Accuracy ($\delta_0 = 0.1 \dots 0.5\%$),

Bandwidth up to 250kHz

SR < 0.5 V/ μ s.



Multiplier with squarer

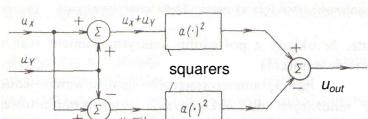

$$u_{out} = a(u_x + u_y)^2 - a(u_x - u_y)^2 = 4au_xu_y$$



Multiplier with squarer


Squarer:

- arbitrary function amplifier (linear approximation),
- FET or MOSFET (input characteristic)

Properties:

- Error 0.5%,
- SR<3V/ μ s
- f_{3dB} <2 MHz

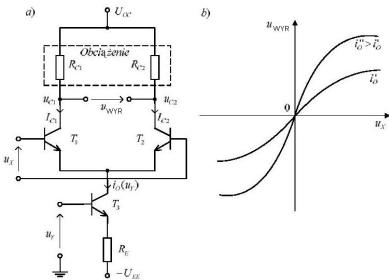Transconductance multiplier - two-quadrant



Transconductance multiplier


$$i_0(u_y) = I_0 + g_m u_y$$

$$u_{out} = i_0 R_C \operatorname{tgh} \frac{u_x}{2\varphi_T}$$


$$\operatorname{tgh} \frac{u_x}{2\varphi_T} \approx \frac{u_x}{2\varphi_T} \quad \text{for} \quad |u_x| \ll 2\varphi_T$$

$$u_{out} = (I_0 + g_m u_y) R_C \operatorname{tgh} \frac{u_x}{2\varphi_T} \approx I_0 R_C \frac{u_x}{2\varphi_T} + g_m R_C \frac{u_x u_y}{2\varphi_T}$$


Linear range of input voltage

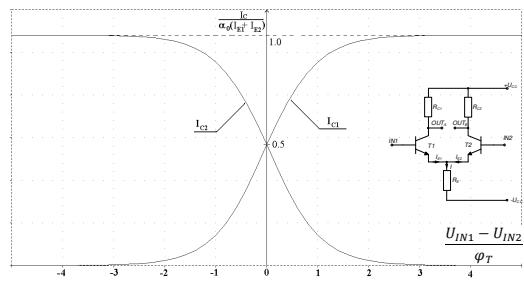


4-quadrant multiplier

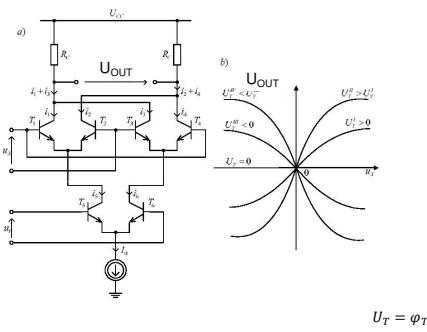


4-quadrant multiplier

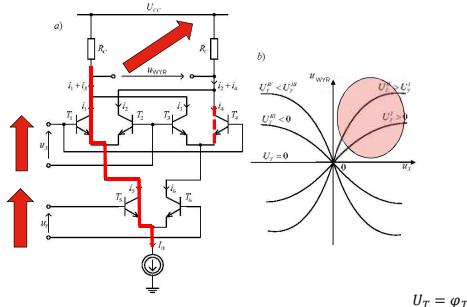

4-quadrant multiplier

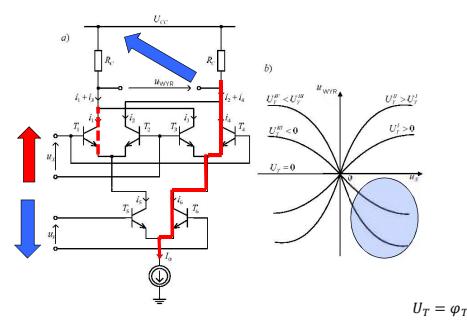


4-quadrant multiplier

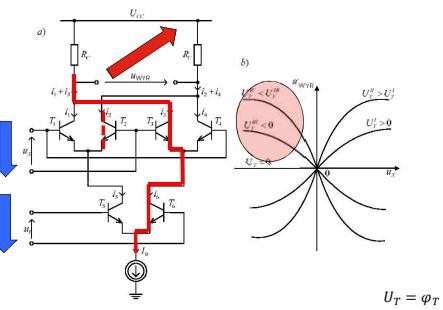

$$U_T = \varphi_T$$

4-quadrant multiplier

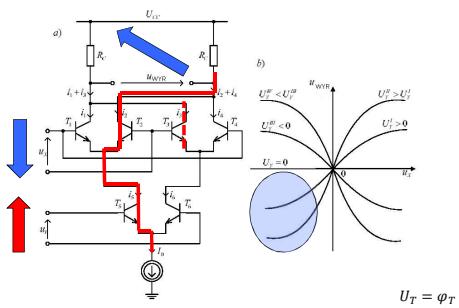

$$U_T = \varphi_T$$

4-quadrant multiplier

$$\begin{aligned} i_{out} &= i_5 \operatorname{tgh} \left(\frac{u_x}{2\varphi_T} \right) - i_6 \operatorname{tgh} \left(\frac{u_x}{2\varphi_T} \right) = (i_5 - i_6) \operatorname{tgh} \left(\frac{u_x}{2\varphi_T} \right) = \\ &= I_0 \left(\frac{u_y}{2\varphi_T} \right) \left(\frac{u_x}{2\varphi_T} \right) \approx \frac{I_0}{4\varphi_T^2} u_x u_y \end{aligned}$$

for: $|u_x|, |u_y| \ll \varphi_T$

Napięcie wyjściowe układu dane jest zależnością:



4-quadrant multiplier linearization


Very small input voltage range

Can be eliminated by:

- Gilbert cell,
- additional R_E




4-quadrant multiplier with Gilbert cell

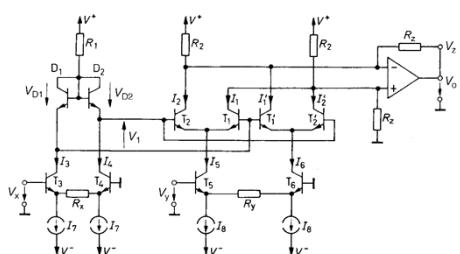


Tietze, Schenk



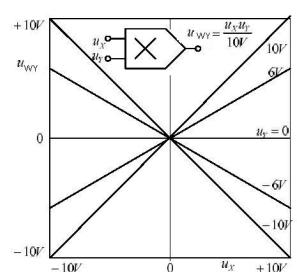4-quadrant multiplier after linearisation



4-quadrant multiplier analog IC examples

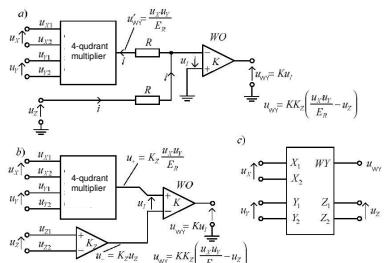


Analog IC multipliers

IC Type	Manufacturer	Accuracy		Bandwidth	
		without adjustment	with adjustment	1%	3 dB
MPY 100	Burr Brown	0.5 %	0.35%	35 kHz	0.5 MHz
MPY 600	Burr Brown	1 %	0.5 %	60 kHz	1 MHz
AD 534	Analog Dev.	0.25%	0.1 %	70 kHz	1 MHz
AD 633	Analog Dev.	1 %	0.1 %	100 kHz	1 MHz
AD 734	Analog Dev.	0.1 %		1000 kHz	10 MHz
AD 834	Analog Dev.	2 %		500 MHz	
AD 835	Analog Dev.			15 MHz	250 MHz
MLT 04*	Analog Dev.	2 %	0.1 %		8 MHz

* 4 multipliers on 1 chip


Tietze, Schenk

Analog divider

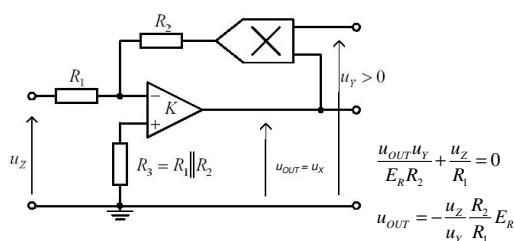




Analog squarer

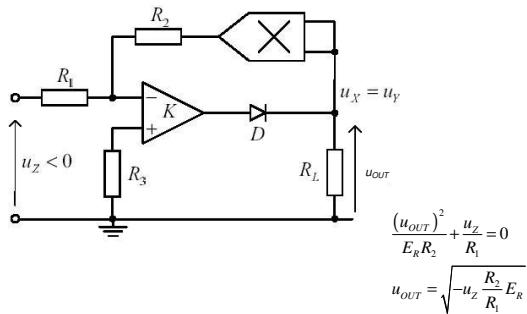


Abs function („perfect” rectifier)

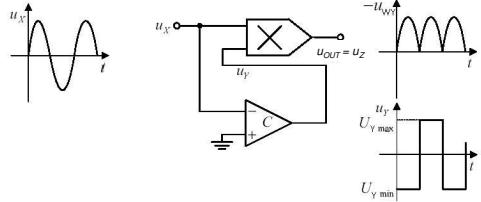

$$u_{OUT} = u_x \operatorname{sgn}(u_x)$$



Analog true RMS transducer

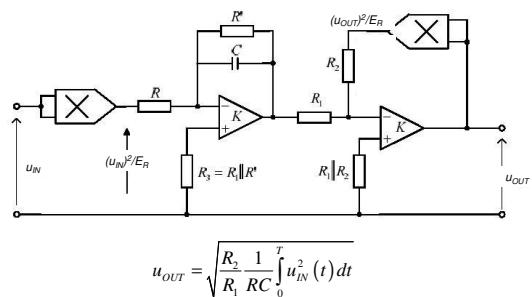



Triangle - sin transducer

Triangle:

$$u_T(t) = (-1)^k \frac{2U_r}{\pi} (\omega t - k\pi)_{\text{dia}} \quad \frac{(2k-1)\pi}{2} \leq \omega t \leq \frac{(2k+1)\pi}{2}$$


SIN Polynomial approximation:

$$U_m \sin \omega t = U_m \left[\omega t - \frac{(\omega t)^3}{3!} + \frac{(\omega t)^5}{5!} - \dots \right]$$


$$u_{OUT} = U_m \sin \omega t \approx U_m \left[\omega t - \frac{(\omega t)^3}{6.81} \right]$$



Triangle - sin transducer

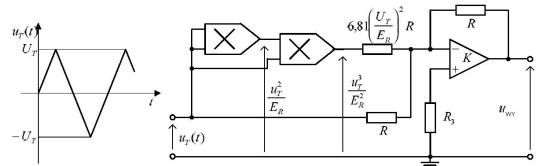


Phase detector

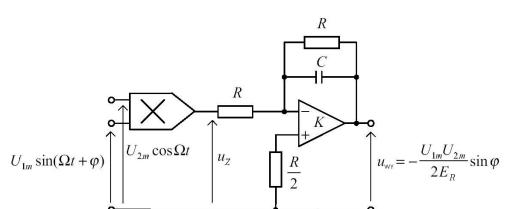




Small signal phase detector

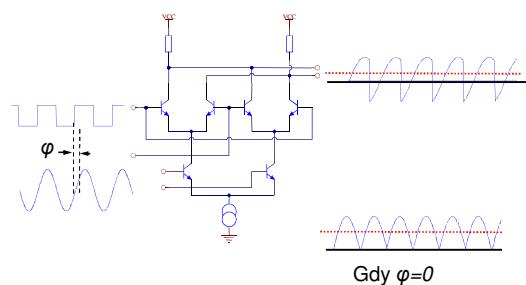




AM synchronous demodulator

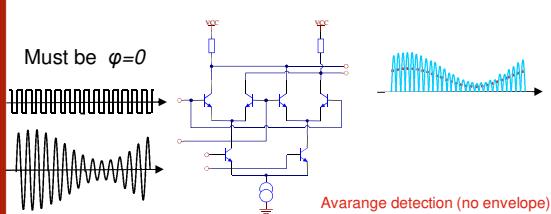



Synchronous detection lock-in-amplifier

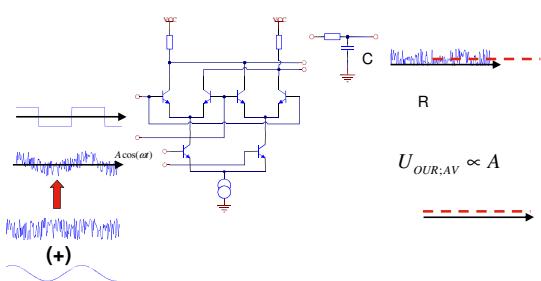



Summary

1. Types of analog multipliers
 - Pulse modulation
 - Log/Exp circuits
 - With squarer
 - Transconductance (2-quadrant; 4-quadrant)
2. Applications
 - divider
 - Square root
 - Rectifier (abs)
 - RMS transducer
 - Triangle – sin transducer
 - Phase detector (to be continued)



Wroclaw
University
of Science
and Technology


Synchronous detection & PLL



Synchronous detection


For

$U_1 \cos(\omega_1 t)$ and $U_2 \cos(\omega_2 t + \phi)$ and $U_2 \gg U_1$
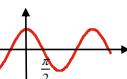
$$U_{OUT,AV} = \begin{cases} U_1 \cos \phi & \text{dla } \omega_1 = \omega_2 \\ 0 & \text{dla } \omega_1 \neq \omega_2 \end{cases}$$

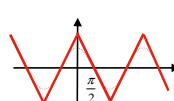
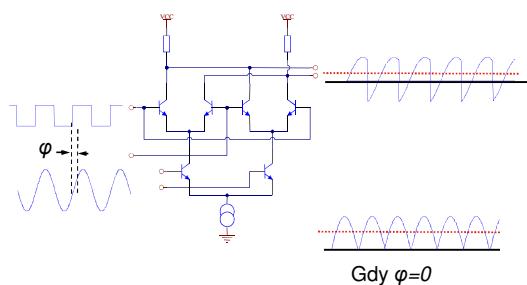
For

$U_1 \cos(\omega_1 t)$ and $U_2 \cos(\omega_2 t + \phi)$

$$U_{OUT,AV} = \begin{cases} U_1 (\phi - \pi/2) & \text{dla } \omega_1 = \omega_2 \\ 0 & \text{dla } \omega_1 \neq \omega_2 \end{cases}$$


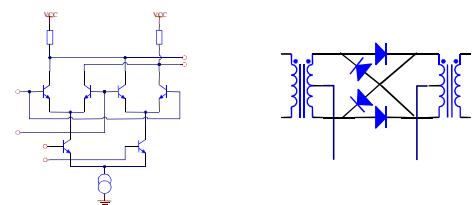


Small signal phase detector






Analog multiplier = phase detector







2-quadrant multiplication

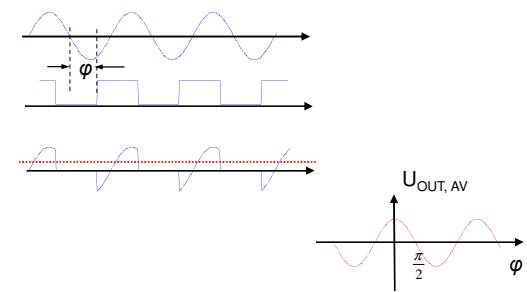


4-quadrant multiplication

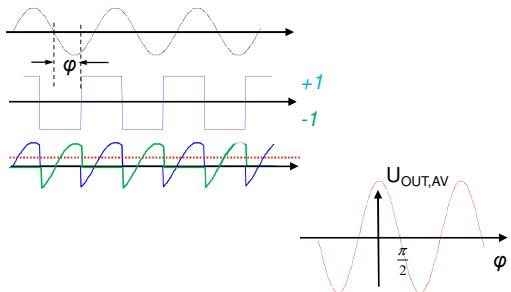

Digital multiplexing - analog output

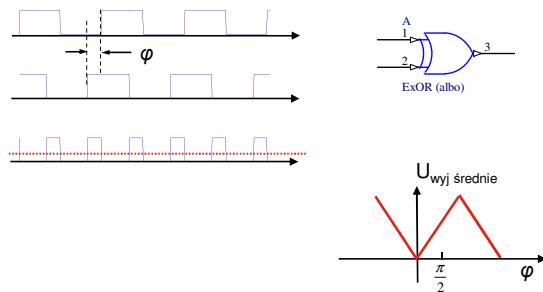


Synchronous detection

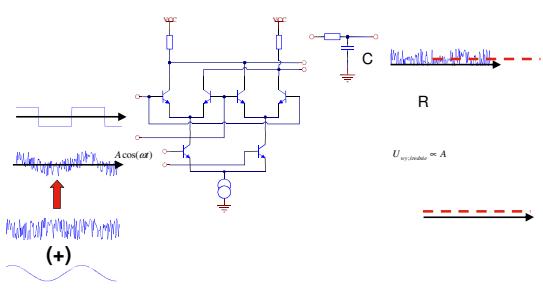



Synchronous detection

Multiplier == synchronous detection

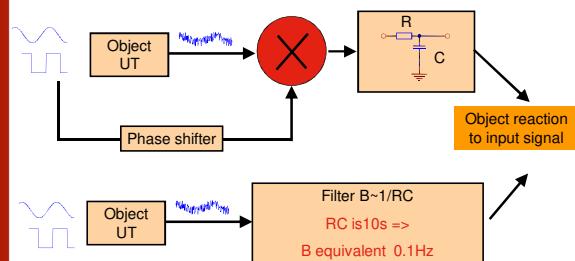






Synchronous detection

- Synchronous detection
- Homodyne detection
- Lock-in amplifier



Lock-in amplifier example




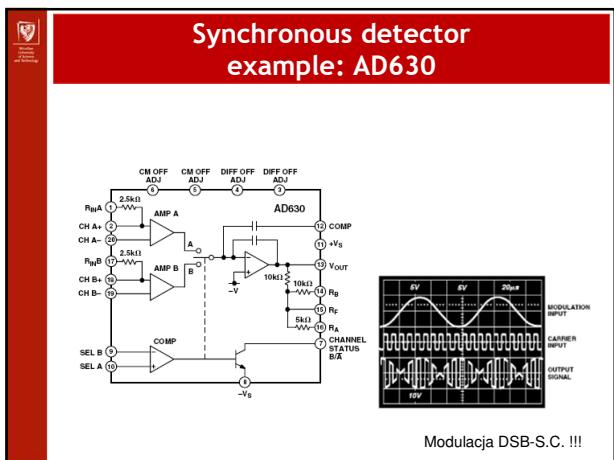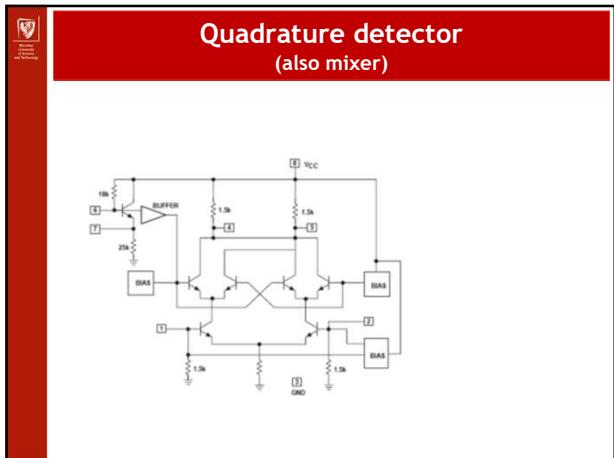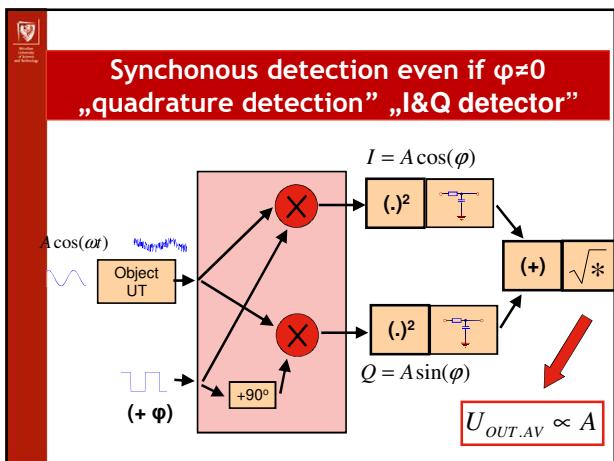



PLL (Phase Locked-Loop)

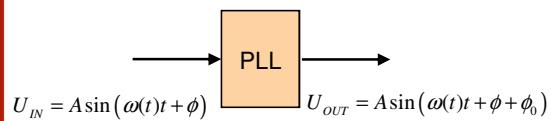Regenerate signal of „exactly” same frequency and phase (shift) !!!!!






PLL

- Synchronize to fundamental frequency or (not always) to harmonics,
- Is able to keep generation even if input signal disappear,
- Input signal can be disturbed(in phase or amplitude),
- Can extract signal from noise (like selective filter)



PLL - block diagram

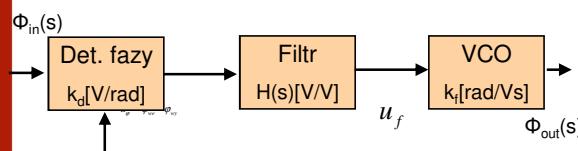



„Phase signal”

$$U_{in} = A \sin(\omega t + \Phi_{in}(t))$$

$$\Phi_{in}(t) \succ \Phi_{in}(s)$$

$$U_{out} = A \sin(\omega t + \Phi_{out}(t))$$

$$\Phi_{out}(t) \succ \Phi_{out}(s)$$



VCO as integrator

$$A \sin(\omega_0 t + \varphi(t)) = A \sin(\Phi(t))$$

$$\omega(t) \equiv \frac{d\Phi(t)}{dt} \quad z \text{ definicji}$$

$$\omega(t) \equiv \omega_0 + k_f u(t) \quad z \text{ "potrzeby"}$$

$$\frac{d\Phi(t)}{dt} = \omega_0 + k_f u(t)$$

$$\Phi(t) = \int_0^t (\omega_0 + k_f u(t)) dt = \omega_0 t + k_f \int_0^t u(t) dt$$


$$\varphi(t) \succ \frac{k_f}{s} U(s)$$

In Laplace transformation
integration corresponds to
division by **s**



PLL - diagram
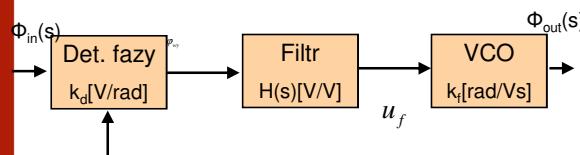
$$G_{owl}(s) \equiv \frac{\Phi_{out}(s)}{\Phi_{in}(s)} = k_d H(s) \frac{k_f}{s}$$






Typ of PLL system

$$G_{OpenLoop}(s) \equiv \frac{\Phi_{out}}{\Phi_{in}} = k_d \frac{k_f}{s} H(s) = \frac{\text{numerator}(s)}{s^{\text{Type}} (\text{polynomial}(s))}$$

Type = the multiplicity of zero pole of transfrerr function with open loop



PLL - block diagram

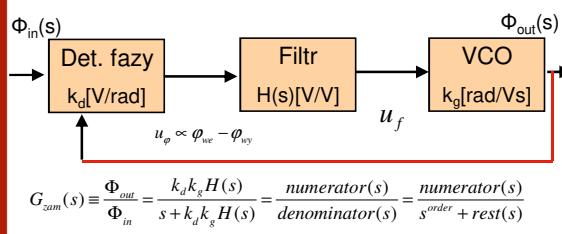


$$G_{zam}(s) \equiv \frac{\Phi_{out}}{\Phi_{in}} = \frac{k_d k_g H(s)}{s + k_d k_g H(s)} = \frac{\text{numerator}(s)}{\text{denominator}(s)} = \frac{\text{numerator}(s)}{s^{\text{order}} + \text{rest}(s)}$$

Order of PLL=

Order of denominator of tr.fuc. with closed loop






Phase detector sample-hold circuit

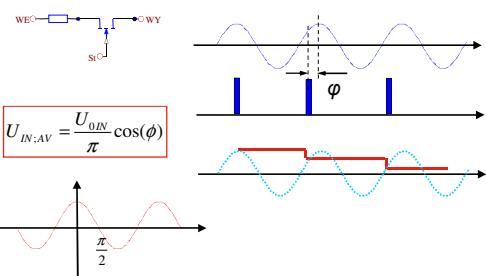



Phase detector EXOR gate

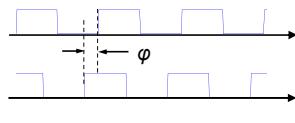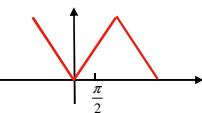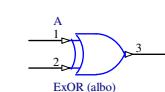





Phase detector switch (multiplier)





$$U_{IN} = U_{0IN} \sin(\omega t)$$
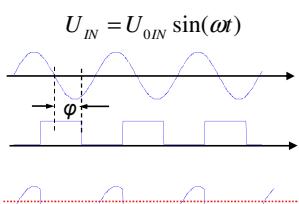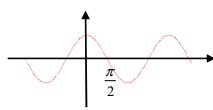
$$U_{OUT,AV} = \frac{U_{0IN}}{\pi} \cos(\phi)$$






Phase detektor switch (multiplier)

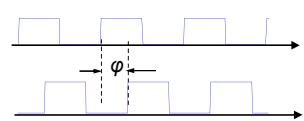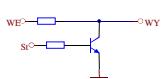


$$U_{OUT,AV} = U_{0IN} \phi / 2$$


Phase detektor analog multiplier

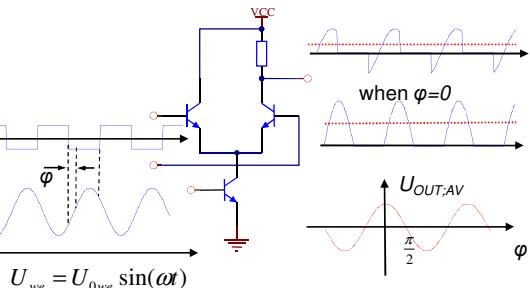

Double-balanced mixer


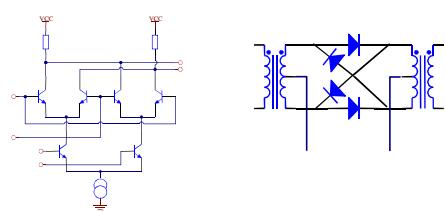


Phase and frequency detector D flip-flop

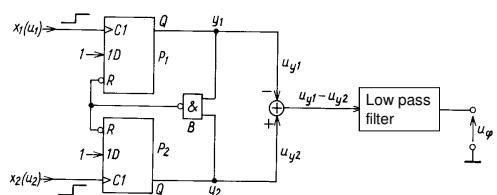





Phase and frequency detector D flip-flop

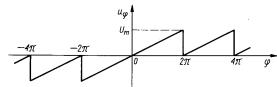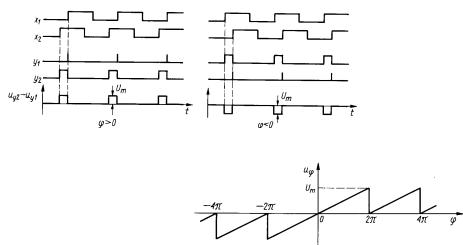

VCO - integrator + flip-flop

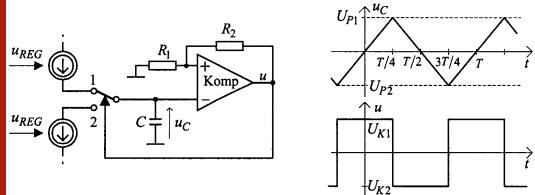


VCO - emitter coupled multivibrator

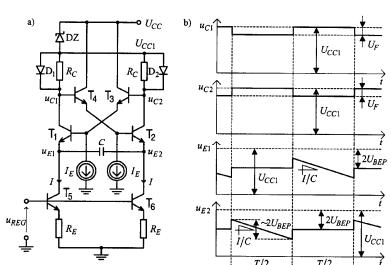



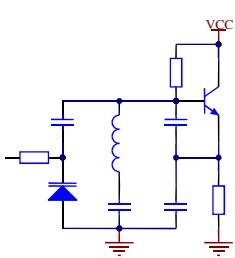Direct modulation VCO- Voltage Controlled Oscillator



$$\Omega = \frac{1}{2\pi\sqrt{LC}}$$


$$C = \frac{C_o}{\sqrt{1-u/V}}$$

$$\Omega = \Omega_0 + f(m(t))$$


Nonlinear function !!!!!



PLL = LP filter

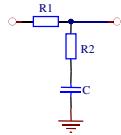

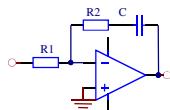
$$H(s) = \frac{1 + R_2 C s}{1 + (R_1 + R_2) C s}$$



$$H(s) = \frac{1 + R_2 C s}{R_1 C s}$$




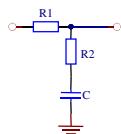PLL funkcja przenoszenia układu z pętlą otwartą



$$G_{ow}(s) = \frac{1 + R_2 C s}{1 + (R_1 + R_2) C s} \cdot \frac{k_d k_f}{s}$$

Type one

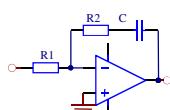


$$G_{ow}(s) = \frac{1 + R_2 C s}{R_1 C s} \cdot \frac{k_g k_f}{s}$$

Type second



PLL close loop transfer function

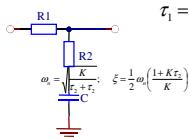

$$\tau_1 = R_1 C \quad \tau_2 = R_2 C \quad K = k_d k_f$$

$$\omega_n = \frac{K}{R_1 + R_2} \quad \xi = \frac{1}{2} \omega_n \left(\frac{1 + K \tau_2}{K} \right)$$

$$G_{zam}(s) = \frac{\omega_n \left(2\xi - \frac{\omega_n}{K} \right) s + \omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

Second order


$$\Delta\omega_L = 2\xi\omega_n$$

$$\Delta\omega_C = \frac{8}{\pi} \sqrt{K\xi\omega_n - \omega_n^2}$$

$$t_C = \frac{(\Delta\omega)^2}{2\xi\omega_n^2}$$



PLL PLL close loop transfer function

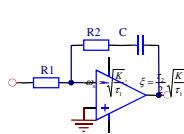

$$\tau_1 = R_1 C \quad \tau_2 = R_2 C \quad K = k_d k_f$$

$$G_{zam}(s) = \frac{2\xi\omega_n s + \omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

Second order

$$\Delta\omega_L = 2\xi\omega_n$$

$$\Delta\omega_C = \frac{8}{\pi} \sqrt{K\xi\omega_n - \omega_n^2}$$

$$t_C = \frac{(\Delta\omega)^2}{2\xi\omega_n^2}$$



PLL - response to input changes

$$\Phi_{out}(s) = G_{zam}(s)\Phi_{in}(s)$$

$$\Phi_{out}(t) > \Phi_{out}(s)$$


$$\omega(t) = \frac{d\Phi_{out}(t)}{dt}$$

$$\begin{aligned} \text{Skokowa zmiana fazy} &\quad \Phi_{in}(t) = \Delta\varphi & \Phi_{in}(s) = \frac{\Delta\varphi}{s} \\ (\text{np.. PSK impulsowa modulacja fazy}) && \end{aligned}$$


$$\begin{aligned} \text{Skokowa zmiana częstotliwości} &\quad \Phi_{in}(t) = \Delta\omega t & \Phi_{in}(s) = \frac{\Delta\omega}{s^2} \\ (\text{np.. FSK impulsowa modulacja częstotliwości}) && \end{aligned}$$

$$\begin{aligned} \text{Liniowa zmiana częstotliwości} &\quad \Phi_{in}(t) = \Delta\omega t^2 & \Phi_{in}(s) = \frac{V}{s^3} \\ (\text{np.. modulacja „chirp”}) && \end{aligned}$$

PLL capture and lock ranges

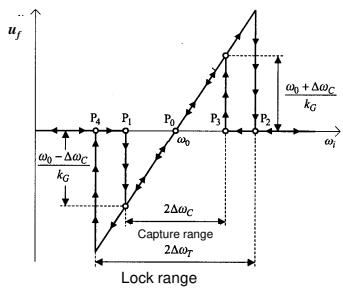

PLL synchronization process

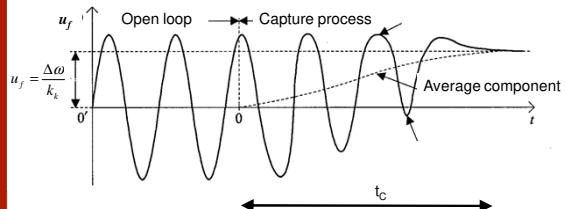


PLL applications


- AM demodulation
- Modulation and demodulation of FM i PM
- Frequency synthesis
- Synchronous detection (reference clock regeneration)
- Telecommunication (clock regeneration)




IC 4046

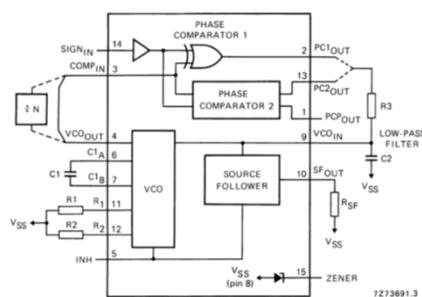

4046 Phase detector I

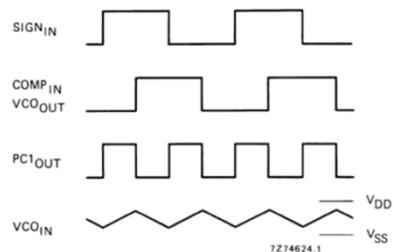

4046 phase detector II

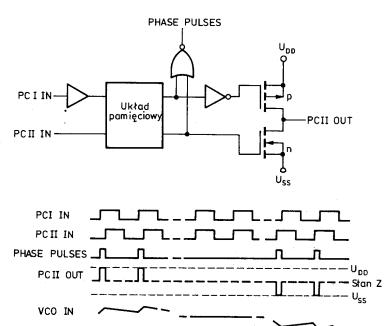



4046 features

Characteristic	Using Phase Comparator 1	Using Phase Comparator 2
No signal on input PCA_{in} .	VCO in PLL system adjusts to center frequency (f_c).	VCO in PLL system adjusts to minimum frequency (f_{min}).
Phase angle between PCA_{in} and PCB_{in} .	90° at center frequency (f_c), approaching 0° and 180° at ends of lock range ($2f_L$)	Always 0° in lock (positive rising edges).
Locks on harmonics of center frequency.	Yes	No
Signal input noise rejection.	High	Low
Lock frequency range ($2f_L$).	The frequency range of the input signal on which the loop will stay locked if it was initially in lock. $2f_L$ = full VCO frequency range = $f_{max} - f_{min}$.	
Capture frequency range ($2f_C$).	The frequency range of the input signal on which the loop will lock if it was initially out of lock. Depends on low-pass filter characteristics (see Figure 3). $f_C \leq f_L$	$f_C = f_L$




4046 features

Charakterystyka	Detektor I (efor)	Detektor II
Brak sygnału na wejściu	$f_{wif} = f_0$	$f_{wif} = f_{min}$
Przesunięcie fazy wej/wy	90deg dla f_c 0 do 180 na granicach $2f_L$	0deg
Syn. Do harmonicznych	synchronizuje	Nie synchronizuje
Odporność na szum	duża	mala
$2f_T$ (trzymanie)		$f_{max} - f_{min}$
$2f_C$ (chwytywanie)	$f_C < f_T$ (zależy od filtra)	$f_C = f_T$




FM demodulator

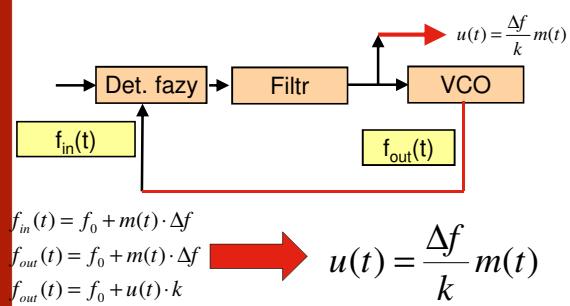





4046 demodulator FM

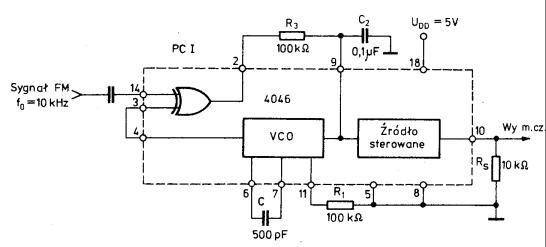

AM synchronous detection

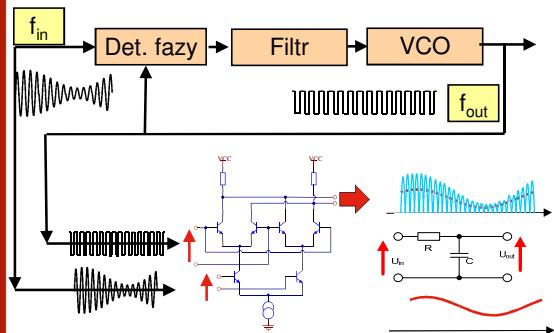


4046 AM demodulator

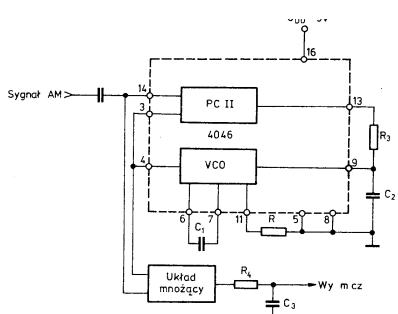





PLL IC LM565 (do 500kHz)

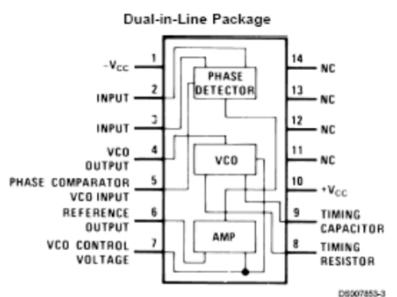

LM565

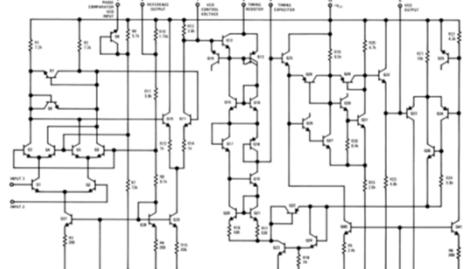


NE564

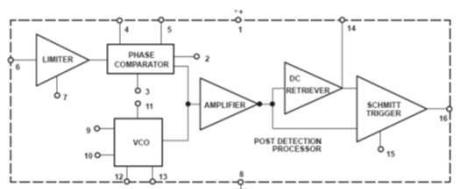





NE564 (up to 50MHz)



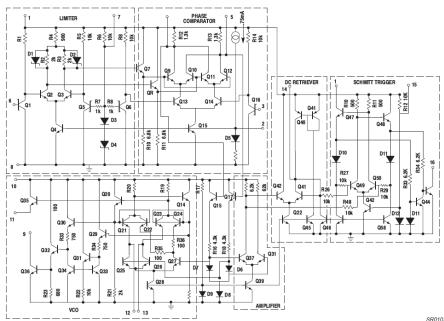


NE567

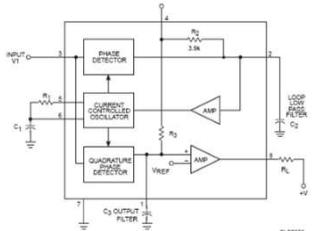


NE567

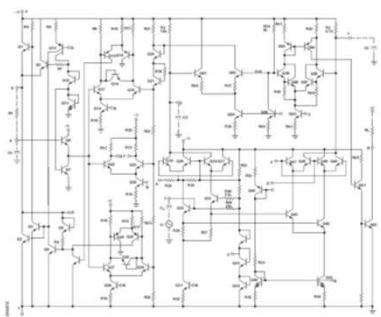

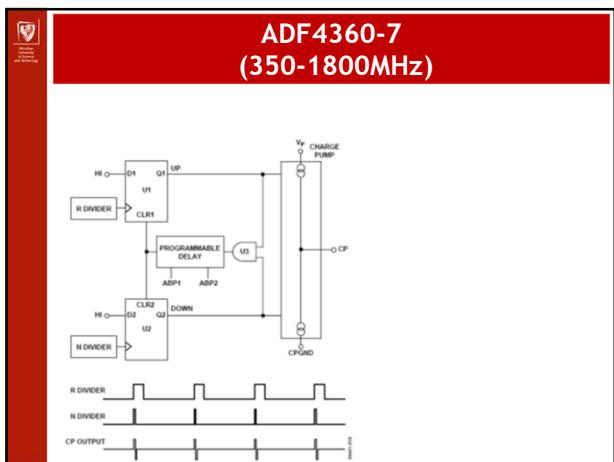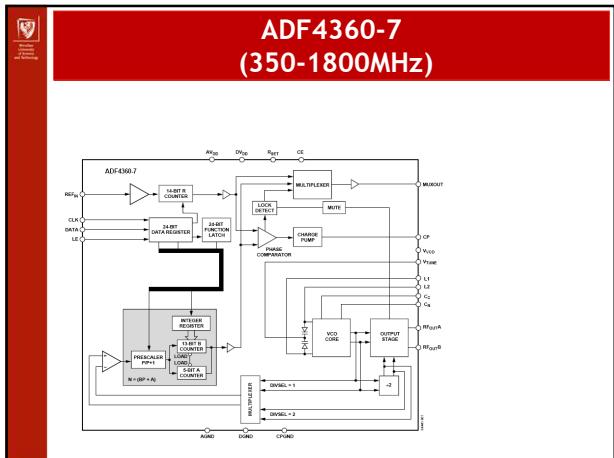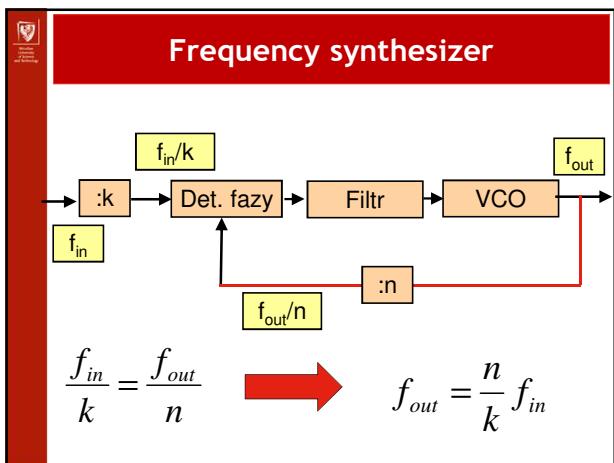



ADF4360-7 generator 500MHz

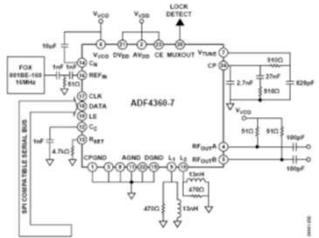

Summary synchronous detection and PLL

- Idea of synchronous detection
- Double balanced mixer
- I & Q detector
- Examples of (phase detector, VCO, filter)
- PLL principle
- What are lock and capture frequency ranges ?
- Applications (AM detector, FM detector, frequency synthesizer)