



Wrocław University of Science and Technology

## Analog to Digital Converters (ADC)

Lecture 7

---

---

---


---

---

---

---

---



## References

- U. Tietze, Ch.Schenk, Electronics Circuits - Handbook for Design and Applications, Springer,2010
- W. Kester, Analog\_Digital conversion, Analog Devices Inc. 2012 ([http://www.analog.com/library/analogDialogue/archives/39/analog\\_conversion\\_handbook.html](http://www.analog.com/library/analogDialogue/archives/39/analog_conversion_handbook.html))
- Advertisement materials and Application notes of:
  - Linear Technology,
  - Analog Device,
  - Texas Instruments,
  - National Semiconductors
  - NEV Corporation

---

---

---


---

---

---

---

---



## Types of AD converters

- **Direct (voltage comparison)**
  - parallel „flash” converter,
  - serial or „pipeline” (2-step, 3-step,.....),
  - successive approximation.
- **Indirect (voltage - time - counter)**
  - tracking converter,
  - compensation converters (single-, dual-, four-slop converter),
  - oversampling converter ( $\Delta$ - $\Sigma$  converters),
  - U/F converters.

---

---

---

---


---

---

---

---

## AC - direct, parallel, „flash”

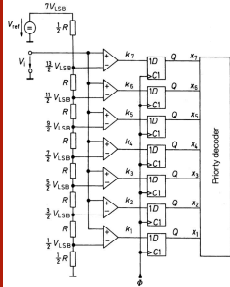

### Features:

- sampling frequency (>100MHz to 10GHz),
- low resolution (4,6,8,10 bits),
- high number of comparators –  $2^n - 1$
- high power dissipation,
- technology: bipolar or ECL,

---

---

---

---


---

---

---

---
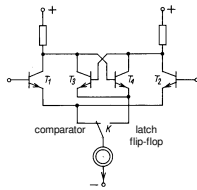
## Comparator and storage flip-flop - a simplified example




---

---

---

---

---

---

---

---


## Example of a „flash” converter AD9054A

### FEATURES

- 200 MSPS Guaranteed Conversion Rate
- 135 MSPS Low Cost Version Available
- 350 MHz Analog Bandwidth
- 1 V p-p Analog Input Range
- Internal 2.5 V Reference and T/H
- Low Power: 500 mW
- 5 V Single Supply Operation
- TTL Output Interface
- Single or Demultiplexed Output Ports
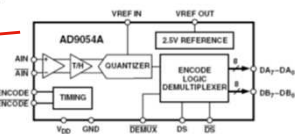
### APPLICATIONS

- RGB Graphics Processing
- High Resolution Video
- Digital Data Storage Read Channels
- Digital Communications
- Digital Instrumentation
- Medical Imaging




---

---

---

---

---

---

---

---


## Example of a „flash” converter AD9054A - cont.

Parameter	Temp	Test Level	AD9054ABST-200			AD9054ABST-135			Unit
			Min	Typ	Max	Min	Typ	Max	
RESOLUTION			8			8			Bits
DC ACCURACY	25°C	I	±0.9	+1.5/-1.0		±0.9	+1.5/-1.0		LSB
	Full	VI	±1.0	+2.0/-1.0		±1.0	+2.0/-1.0		LSB
Integral Nonlinearity	25°C	I	±0.6	±1.5		±0.6	±1.5		LSB
	Full	VI	±0.9	±2.0		±0.9	±2.0		LSB
No Missing Codes	Full	VI	Guaranteed			Guaranteed			
Gain Error <sup>1</sup>	25°C	I	±2	±7		±2	±7		% FS
Gain Tempo <sup>1</sup>	Full	V	160			160			ppm/°C

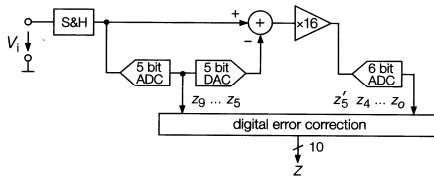
## 2-step converter (direct, serial, pipeline)

**Features** (compared to „flash”):

- lower number comparators
- higher conversion time
- more popular (cheaper)
- higher resolution



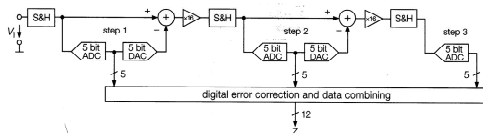
## 3-step converter (direct, serial, pipeline)




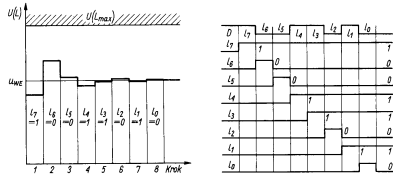
## Successive approximation AD converters - principle of operation




---

---

---

---

---

---

---

---

---

---

## Example of successive approximation converter - AD7854

### FEATURES

Specified for  $V_{DD}$  of 3 V to 5.5 V

Read-Only Operation

AD7854-200 kSPS; AD7854L-100 kSPS

System and Self-Calibration

Low Power

Normal Operation

AD7854: 15 mW ( $V_{DD} = 3$  V)

AD7854L: 5.5 mW ( $V_{DD} = 3$  V)

Automatic Power-Down After Conversion (25  $\mu$ W)

AD7854: 1.3 mW 10 kSPS

AD7854L: 650  $\mu$ W 10 kSPS

Flexible Parallel Interface

12-Bit Parallel/8-Bit Parallel (AD7854)

28-Lead DIP, SOIC and SSOP Packages (AD7854)

### APPLICATIONS

Battery-Powered Systems (Personal Digital Assistants, . . .

Medical Instruments, Mobile Communications)

Pen Computers

Instrumentation and Control Systems

High Speed Modems

Compare with  
„flash“

**FEATURES**  
 200 MSPS Guaranteed Conversion Rate  
 135 MSPS Low Cost Version Available  
 350 MHz Analog Bandwidth  
 1 V p-p Analog Input Range  
 Internal 2.5 V Reference and T/H  
 Low Power: 500 mW  
 5-V Single Supply Operation  
 TTL Output Interface  
 Single or Demultiplexed Output Ports

**APPLICATIONS**  
 RGB Graphics Processing  
 High Resolution Video  
 Digital Data Storage Read Channels  
 Digital Communications  
 Digital Instrumentation  
 Medical Imaging

---

---

---

---

---

---


---

---

---

---
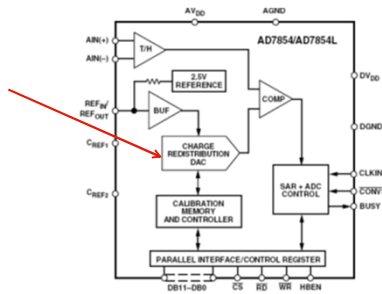
## Example of successive approximation AD converter - AD7854 (cont.)




---

---

---

---

---

---

---


---

---

---


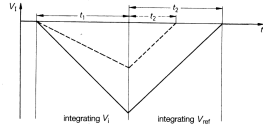
## Compensation converter (indirect) - dual slop converter (cont.)



### Advantages:

- result does not depend on:
  - linearity of the integrator,
  - time constant,
  - clock frequency,
  - comparator offset,
  - some noise is suppressed.

$$U_{in} = \frac{t_2}{t_1} U_{REF}$$

---

---

---

---

---

---


---

---

---

---
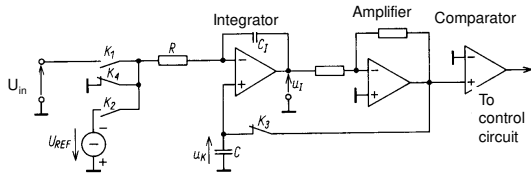
## Auto-zero conversion (auto zero amplifier)



1. For K4 and K3 on, the capacitor C is charged to a voltage  $U_k$  equal to the integrator offset.
2. When K4 and K3 off the voltage  $U_k$  cancels the integrator offset.

---

---

---

---

---

---

---

---

---

---

## Dual slope with auto-zero example ICL7106/7107

### Features

- Guaranteed Zero Reading for 0V Input on All Scales ←
- True Polarity at Zero for Precise Null Detection ←
- 1pA Typical Input Current ←
- True Differential Input and Reference, Direct Display Drive
  - LCD ICL7106, LED ICL7107
- Low Noise - Less Than  $15\mu V_{p,p}$
- On Chip Clock and Reference
- Low Power Dissipation - Typically Less Than 10mW ←
- No Additional Active Circuits Required
- Enhanced Display Stability
- Pb-Free Plus Anneal Available (RoHS Compliant)

---

---

---

---

---

---

---

---


---

---

## Dual slope with auto-zero example ICL7106/7107 (cont.)


PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
<b>SYSTEM PERFORMANCE</b>					
Zero Input Reading	$V_{IN} = 0\text{V}$ , Full Scale = 200mV	-000.0	+000.0	+000.0	Digital Reading
Stability (Last Digit) (ICL7106, ICL7107 Only)	Fixed Input Voltage (Note 6)	-000.0	+000.0	+000.0	Digital Reading
Ratometric Reading	$V_{IN} = V_{REF}$ , $V_{REF} = 100\text{mV}$	999	999.10	1000	Digital Reading
Rollover Error	$V_{IN} = +V_{FS} \pm 200\text{mV}$ (Difference in Reading for Equal Positive and Negative Inputs Near Full Scale)	-	$\pm 0.2$	$\pm 1$	Counts
Linearity	Full Scale = 200mV or Full Scale = 2V Maximum Deviation from Best Straight Line (4 Note 5)	-	$\pm 0.2$	$\pm 1$	Counts
Common Mode Rejection Ratio	$V_{CM} = 1\text{V}$ , $V_{IN} = 0\text{V}$ , Full Scale = 200mV (Note 5)	-	50	-	$\mu\text{V/V}$
Noise	$V_{IN} = 0\text{V}$ , Full Scale = 200mV (Peak-to-Peak Value Not Exceeded 95% of Time)	-	15	-	$\mu\text{V}$
Leakage Current Input	$V_{IN} = 0$ (Note 5)	-	1	10	$\mu\text{A}$
Zero Reading Drift	$V_{IN} = 0$ , 0°C To 75°C (Note 5)	-	0.2	1	$\mu\text{V}/^\circ\text{C}$
Scale Factor Temperature Coefficient	$V_{IN} = 199\text{mV}$ (0°C To 75°C (Ext. Ref. Approx. $^\circ\text{C}$ )) (Note 5)	-	1	5	ppm/°C
End Power Supply Character $V^+$ -Supply Current	$V_{IN} = 0$ (Does Not Include LED Current for ICL7107)	-	1.0	1.6	mA
End Power Supply Character $V^-$ -Supply Current	ICL7107 Only	-	0.0	1.6	mA
COMMON Pin Analog Common Voltage	25kΩ Between Common and Positive Supply (With Respect to + Supply)	2.4	3.0	3.2	V
Temperature Coefficient of Analog Common	25kΩ Between Common and Positive Supply (With Respect to + Supply)	-	80	-	ppm/°C
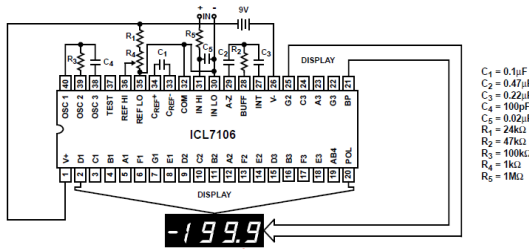
## Dual slope with auto-zero example ICL7106/7107 (cont.)




- $C_1 = 0.1\mu\text{F}$
- $C_2 = 0.47\mu\text{F}$
- $C_3 = 0.22\mu\text{F}$
- $C_4 = 100\mu\text{F}$
- $C_5 = 0.02\mu\text{F}$
- $R_1 = 24\text{k}\Omega$
- $R_2 = 47\text{k}\Omega$
- $R_3 = 100\text{k}\Omega$
- $R_4 = 1\text{k}\Omega$
- $R_5 = 1\text{M}\Omega$
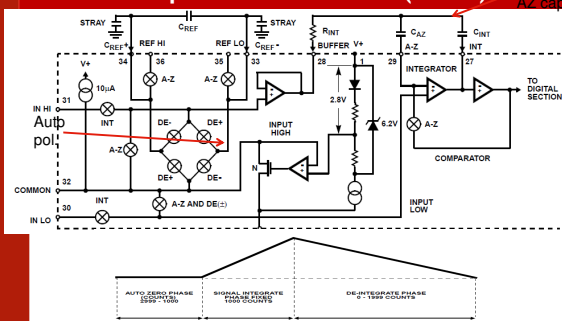
## Dual slope with auto-zero example ICL7106/7107 (cont.)





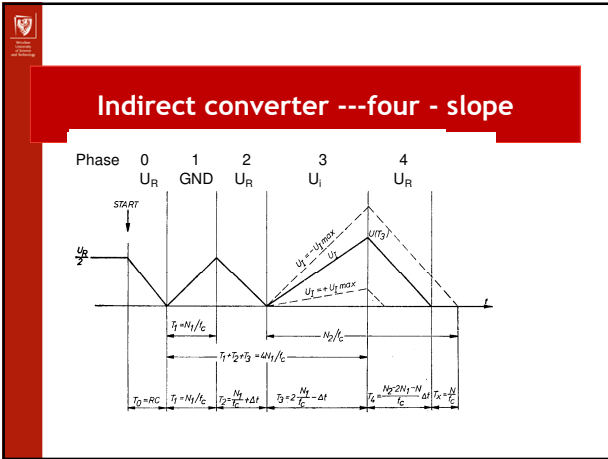


---

---

---


---

---

---

---

---

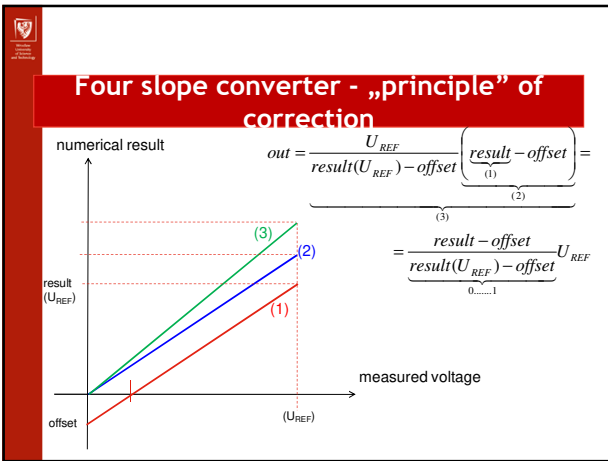


---

---

---

---

---

---

---

---

- ### Indirect, integrating converters - dual and four slope
- Result is independent on:
    - time constant of the integrator
    - integrator nonlinearity,
    - comparator offset
    - (integrate and de-integrate phase)
    - clock frequency (result = ratio of pulse number)
    - high frequency noise (averaging effect)
    - gain error
    - temperature drifts
- }

four slope

}

dual slope

---

---

---

---

---

---

---

---

## Types of AD converters

- Direct (voltage comparison)
  - parallel „flash” converter,
  - serial or „pipeline” (2-step, 3-step,...),
  - successive approximation.
- Indirect (voltage - time - counter)
  - tracking converter,
  - compensation converters (single-, dual-, four-slop converter),
  - oversampling converter ( $\Sigma$ - $\Delta$  converters),
  - U/F converters.

---

---

---

---


---

---

---

---
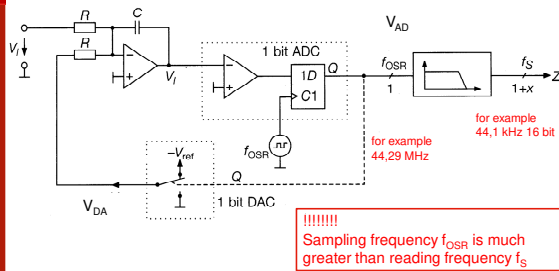
## „ $\Sigma$ - $\Delta$ ” converter oversampling converter




---

---

---

---


---

---

---

---
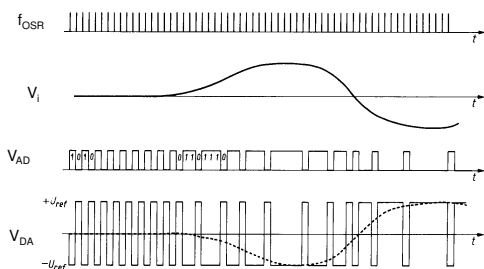
## „ $\Sigma$ - $\Delta$ ” converter - principle of operation




---

---

---

---


---

---

---

---
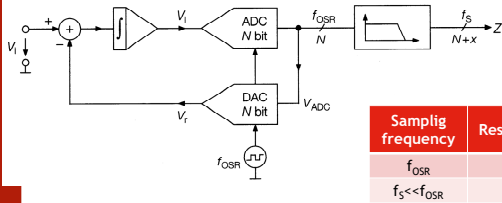
## Oversampling „Σ-Δ” converter - general principle



Sampling frequency	Resolution
$f_{OSR}$	N
$f_s \ll f_{OSR}$	N+x

---

---

---

---

---

---


---

---

---

---

## Noise shaping in „Σ-Δ” converter

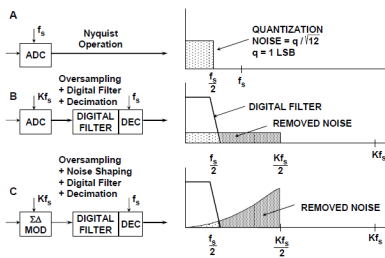


---

---

---

---

---

---


---

---

---

---

## „Σ-Δ” converter - linear model

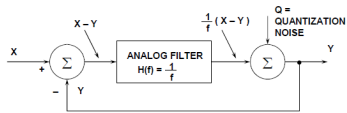

$$Y = \frac{1}{f}(X - Y) + Q$$

REARRANGING, SOLVING FOR Y:

$$Y = \frac{X}{f+1} + \frac{Qf}{f+1}$$

SIGNAL TERM
 NOISE TERM

---

---

---

---

---

---

---

---

---

---

## Conventional converter

$$U_{Nout} \propto \frac{1}{\sqrt{f_{os}/f_s}}$$

$$N_{bits} = \frac{20 \log \sqrt{f_{os}/f_s}}{6dB/bit}$$

$f_{os}/f_s$	bit
2	0.5
4	1
256	4

---

---

---

---


---

---

---

---
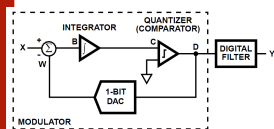
## First order „ $\Delta$ - $\Sigma$ ” converter



$$U_{Nout} \propto \left( \frac{1}{\sqrt{f_{os}/f_s}} \right)^3$$

$$N_{bits} = \frac{20 \log \left( \sqrt{f_{os}/f_s} \right)^3}{6dB/bit}$$

$f_{os}/f_s$	bit
2	1.5
4	3
256	12

---

---

---

---


---

---

---

---
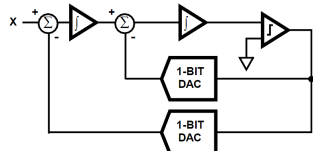
## 3rd order „ $\Delta$ - $\Sigma$ ” converter



$$U_{Nout} \propto \left( \frac{1}{\sqrt{f_{os}/f_s}} \right)^5$$

$$N_{bits} = \frac{20 \log \left( \sqrt{f_{os}/f_s} \right)^5}{6dB/bit}$$

$f_{os}/f_s$	bit
2	2.5
4	5
256	20

---

---

---


---

---

---

---

---

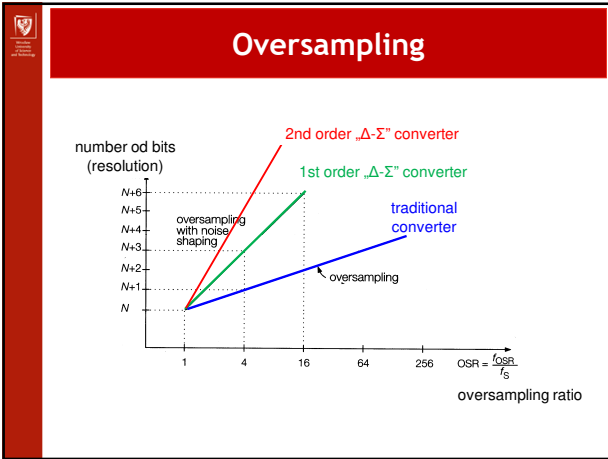


---

---

---

---

---


---

---

---

---

---

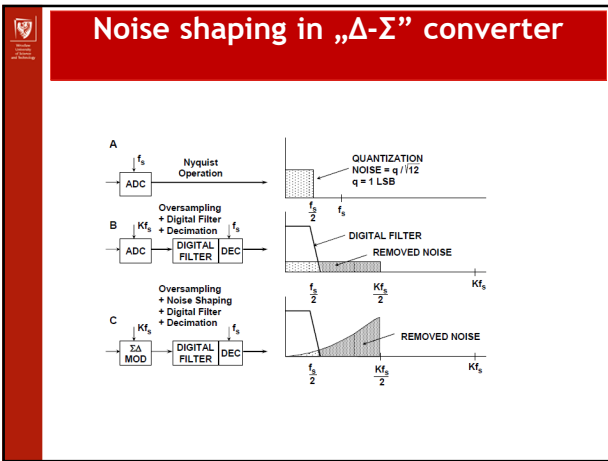


---

---

---

---

---

---

---

---

---

---

## Example of „Δ-Σ” converter ADS1110

**FEATURES**

- COMPLETE DATA ACQUISITION SYSTEM IN A TINY SOT23-6 PACKAGE
- ONBOARD REFERENCE: Accuracy: 2.048V ±0.05%  
Drift: 5ppm/°C
- ONBOARD PGA
- ONBOARD OSCILLATOR
- 16-BITS NO MISSING CODES
- INL: 0.01% of FSR max
- CONTINUOUS SELF-CALIBRATION
- SINGLE-CYCLE CONVERSION
- PROGRAMMABLE DATA RATE: 15SPS TO 240SPS
- I<sup>2</sup>C™ INTERFACE—EIGHT AVAILABLE ADDRESSES
- POWER SUPPLY: 2.7V to 5.5V
- LOW CURRENT CONSUMPTION: 240µA

---

---

---

---

---

---


---

---

---

---

## Lab setup of pressure sensor

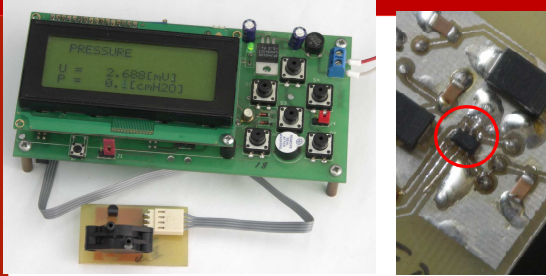


---

---

---

---


---

---

---

---
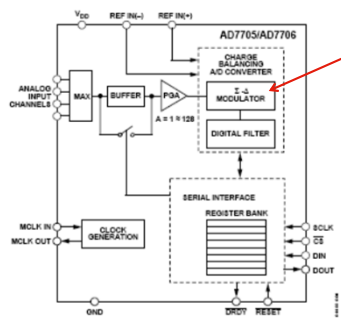
## Example of „ $\Delta$ - $\Sigma$ ” converter AD7705/7706




---

---

---

---

---

---

---

---

## „ $\Delta$ - $\Sigma$ ” summary

- Inherently Excellent Linearity
- High Resolution Possible (24-Bits)
- Oversampling Relaxes Analog Antialiasing Filter Requirements
- Ideal for CMOS Processes, no Trimming
- No SHA Required
- Added Functionality: On-Chip PGAs, Analog Filters, Autocalibration
- On-Chip Programmable Digital Filters (AD7725: Lowpass, Highpass, Bandpass, Bandstop)
- Upper Sampling Rate Currently Limits Applications to Measurement, Voiceband, and Audio, except for Bandpass Sigma-Delta ADCs
- Analog Multiplexer Switching Speed Limited by Internal Filter Settling Time.

---

---

---

---

---

---

---

---

## Example of „ $\Delta$ - $\Sigma$ ” converter AD7705/7706 (cont.)

Parameter	B Version <sup>1</sup>	Unit	Conditions/Comments
<b>STATIC PERFORMANCE</b>			
No Missing Codes	16	Bits min	Guaranteed by design, filter notch < 60 Hz
Output Noise	See Table 5 and Table 7		Depends on filter cutoffs and selected gain
Integral Nonlinearity <sup>2</sup>	$\pm 0.003$	% of FSR max	Filter notch < 60 Hz, typically $\pm 0.0003\%$
Unipolar Offset Error <sup>2</sup>	0.5	$\mu\text{V}/^\circ\text{C}$ typ	
Unipolar Offset Drift <sup>4</sup>	0.5	$\mu\text{V}/^\circ\text{C}$ typ	
Bipolar Zero Error <sup>3</sup>	0.1	$\mu\text{V}/^\circ\text{C}$ typ	For gains 1, 2, and 4
Bipolar Zero Drift <sup>4</sup>	0.1	$\mu\text{V}/^\circ\text{C}$ typ	For gains 8, 16, 32, 64, and 128
Positive Full-Scale Error <sup>3,5</sup>	0.5	$\mu\text{V}/^\circ\text{C}$ typ	
Full-Scale Drift <sup>4,6</sup>	0.5	$\mu\text{V}/^\circ\text{C}$ typ	
Gain Error <sup>3,7</sup>	0.5	ppm of FSR/ $^\circ\text{C}$ typ	
Gain Drift <sup>8,9</sup>	0.5	ppm of FSR/ $^\circ\text{C}$ typ	
Bipolar Negative Full-Scale Error <sup>2</sup>	$\pm 0.003$	% of FSR typ	Typically $\pm 0.001\%$
Bipolar Negative Full-Scale Drift <sup>4</sup>	1	$\mu\text{V}/^\circ\text{C}$ typ	For gains of 1 to 4
	0.6	$\mu\text{V}/^\circ\text{C}$ typ	For gains of 8 to 128

---

---

---

---

---

---


---

---

---

---

## General comparison of AD converters

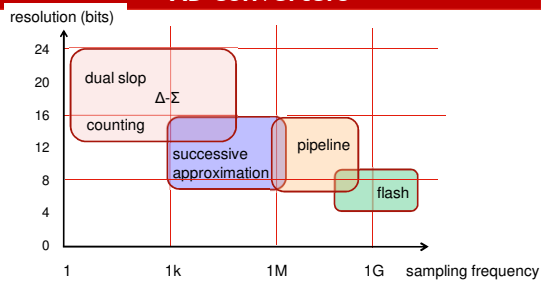


---

---

---

---

---

---


---

---

---

---
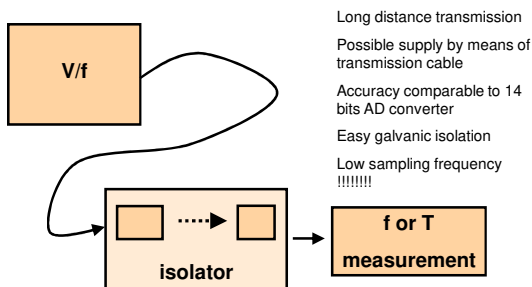
## Voltage-frequency transducers -features




---

---

---

---

---

---

---

---


---

---

## Voltage-frequency transducers AD654
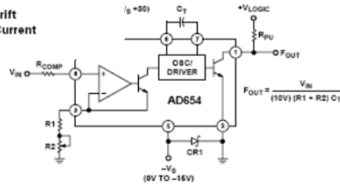
### FEATURES

- Low Cost
- Single or Dual Supply, 5 V to 36 V,  $\pm 5$  V to  $\pm 18$  V
- Full-Scale Frequency Up to 500 kHz
- Minimum Number of External Components Needed
- Versatile Input Amplifier
- Positive or Negative Voltage Modes
- Negative Current Mode
- High Input Impedance, Low Drift
- Low Power: 2.0 mA Quiescent Current
- Low Offset: 1 mV




## Voltage-frequency transducers AD654 (cont.)

Model	Min	AD654JNJR Typ	Max	Units
<b>CURRENT-TO-FREQUENCY CONVERTER</b>				
Frequency Range	0		500	kHz
Nonlinearity		0.06	0.1	%
$f_{max}$ = 250 kHz		0.20	0.4	%
$f_{max}$ = 500 kHz				
Full-Scale Calibration Error	-10		+10	%
C = 390 pF; $I_{CS}$ = 1.000 mA				
vs. Supply ( $f_{max}$ ≤ 250 kHz)		0.20	0.40	%/V
$V_1$ = +4.75 V to +5.25 V		0.05	0.10	%/V
$V_2$ = +5.25 V to +6.5 V				
vs. Temp. (0°C to +70°C)		50		ppm/°C
<b>ANALOG INPUT AMPLIFIER (Voltage-to-Current Converter)</b>				
Voltage Input Range				V
Single Supply	0		(+V <sub>1</sub> - 4)	V
Dual Supply	-V <sub>2</sub>		(+V <sub>1</sub> - 4)	V
Input Bias Current		30	50	nA
(Either Input)		5		nA
Input Offset Current		250		μA
Input Resistance (Noninverting)		0.5	1.0	mV
Input Offset Voltage				mV/V
vs. Supply		0.1	0.25	mV/V
$V_1$ = +4.75 V to +5.25 V		0.05	0.1	mV/V
$V_2$ = +5.25 V to +6.5 V				
vs. Temp. (0°C to +70°C)		4		μV/°C

## Voltage-frequency transducers AD537
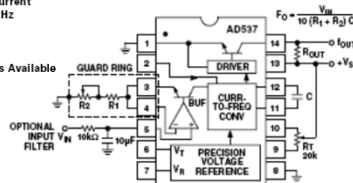
### FEATURES

- Low Cost A-D Conversion
- Versatile Input Amplifier
- Positive or Negative Voltage Modes
- Negative Current Mode
- High Input Impedance, Low Drift
- Single Supply, 5 V to 36 V
- Linearity:  $\pm 0.05\%$  FS
- Low Power: 1.2 mA Quiescent Current
- Full-Scale Frequency up to 100 kHz
- 1.00 V Reference
- Thermometer Output (1 mV/K)
- F-V Applications
- MIL-STD-883 Compliant Versions Available







## Flow rate sampling frequency vs. resolution

$$FR[\text{bits} / \text{s}] \approx \underbrace{\frac{SNR[\text{dB}] \cdot B[\text{Hz}]}{3}}_{\text{flow rate of a channel}} \approx \frac{6n \cdot f_s / 2}{3} = n \cdot f_s$$

high resolution – low sampling rate  
high sampling rate – low resolution

!!!!!!!!!!!!!!!!!!!!

---

---

---

---


---

---

---

---

## General comparison of AD converters

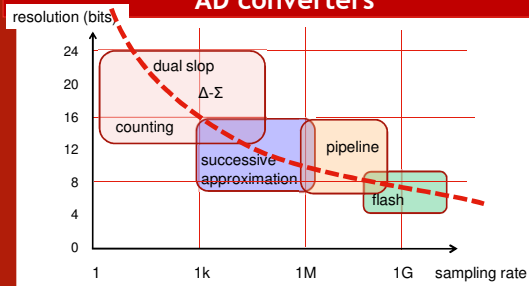


---

---

---

---

---

---

---

---

## References

1. W. Tietze, Ch. Schenk, „*Electronic circuits. Handbook for Design and Applications*“, Springer 2002.
2. P. Horowitz, H. Hill, „*The Art of Electronics*“, Cambridge Univ. Press 1989.
3. Application notes:
  - Analog Device Inc.,
  - Texas Instrument Inc.

---

---

---

---

---

---

---

---



### Test questions:

- Name types of AD converters, describe the typical speed and resolution.
- What is the principle of oversampling ?

---

---

---

---

---

---

---

---