



Wrocław
University
of Science
and Technology

Power suppliers:

- rectifiers,
- filters,
- voltage multipliers



Transformer parameters


- Power (single phase up to 3kW)
- Nominal voltage 230V +10% -10%
- Frequency 50Hz
- Transformer parameters:
 - Turn ratio (secondary voltage and current)
 - Idle current
 - Isolation breakdown voltage
 - Dimensions, weight
 - temperature






Rodzaje transformatorów sieciowych

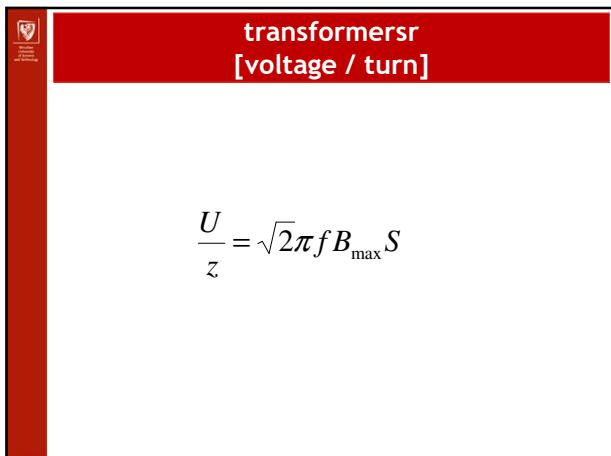
- Rdzenie typu EI, zwijane, toroidalne
- Materiał rdzenia
 - Blachy gorąco walcowane
 - Blachy zimnowalcowane








Transformers - power vs. type		
S[cm ²] [@] P[W]	core	B _{max} [T]
$S \approx 1,25 \cdot \sqrt{P_1}$	Hot rolled steel sheet, EI core	1T
$S \approx 1,1 \cdot \sqrt{P_1}$	Cold rolled steel sheet EI core	1.1T
$S \approx \sqrt{P_1}$	Cold rolled steel sheet wound core	1.5T
$S \approx 0,8 \cdot \sqrt{P_1}$	Cold rolled steel sheet Toroid	1.6T

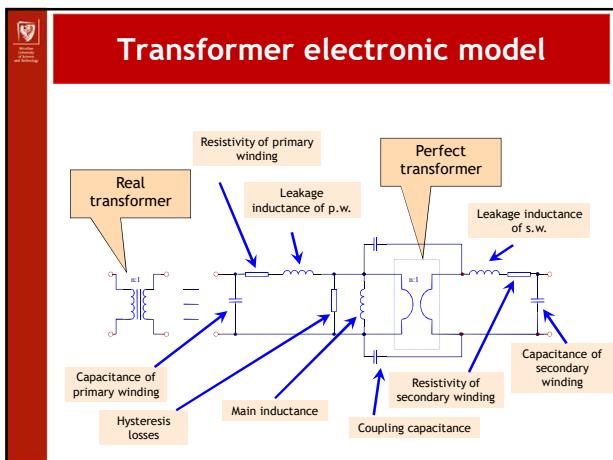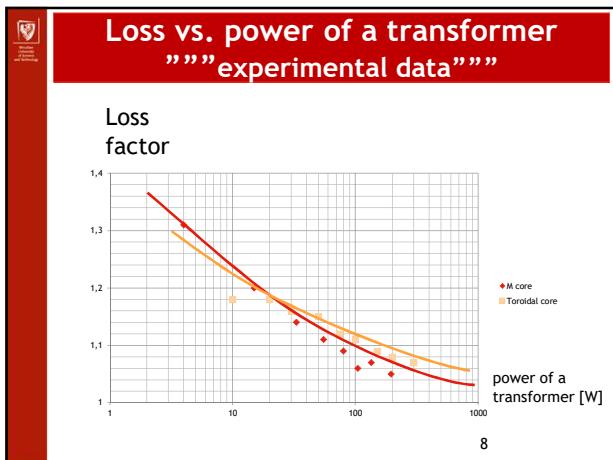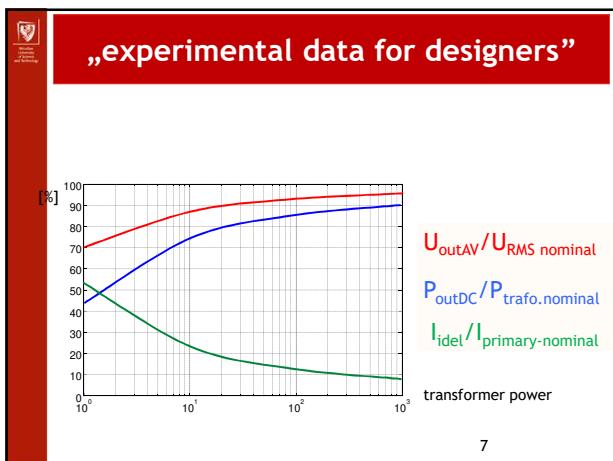


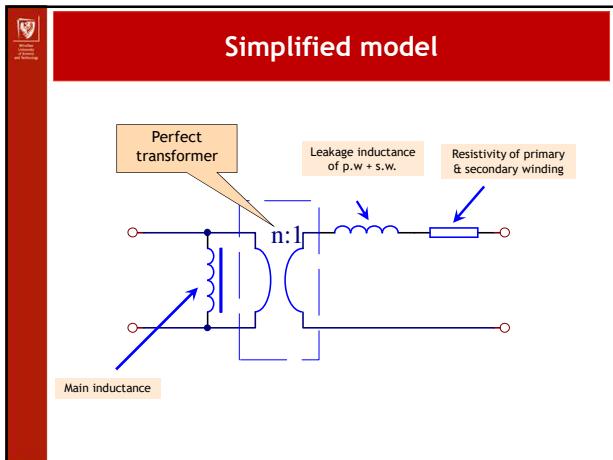




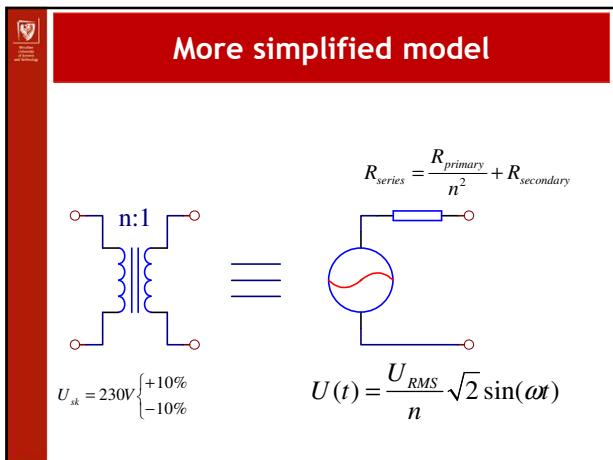


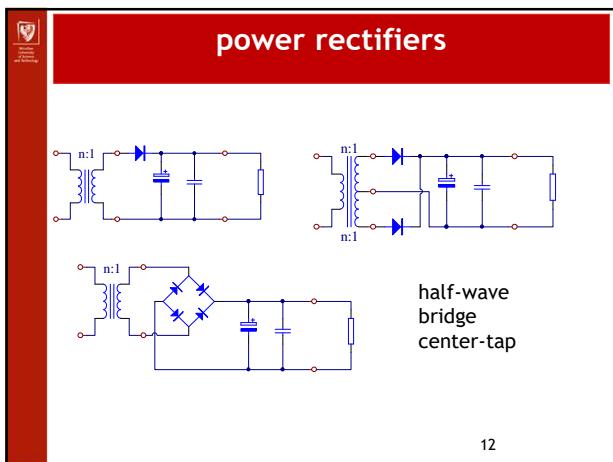

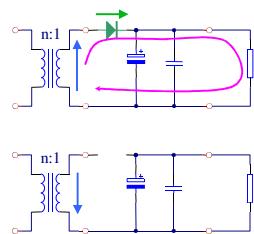half-wave

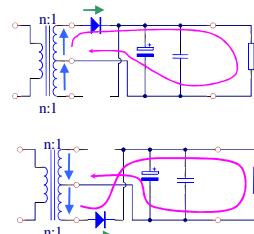Center-tap

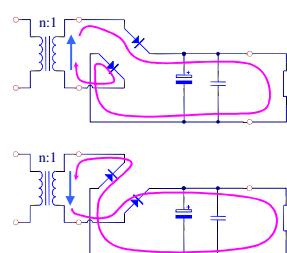bridge

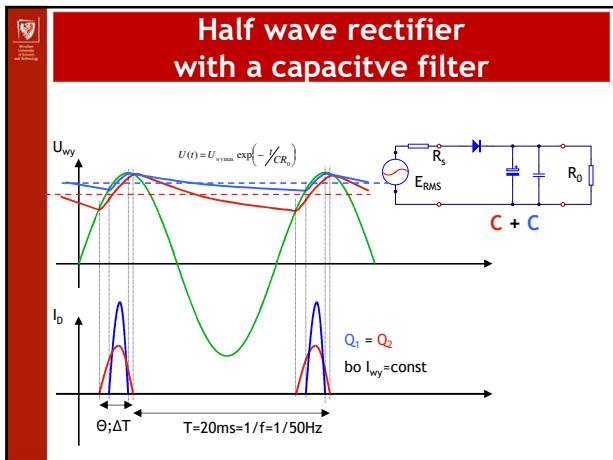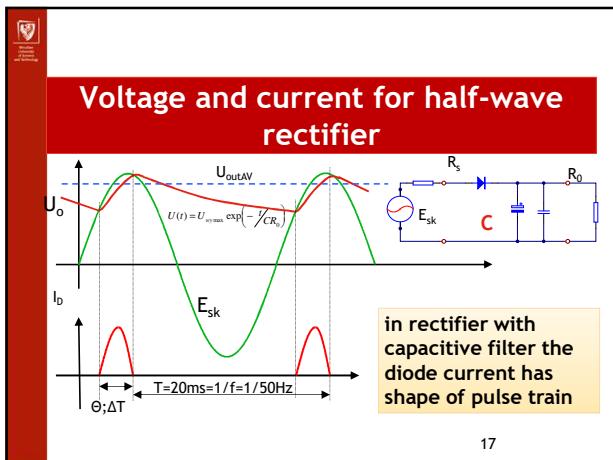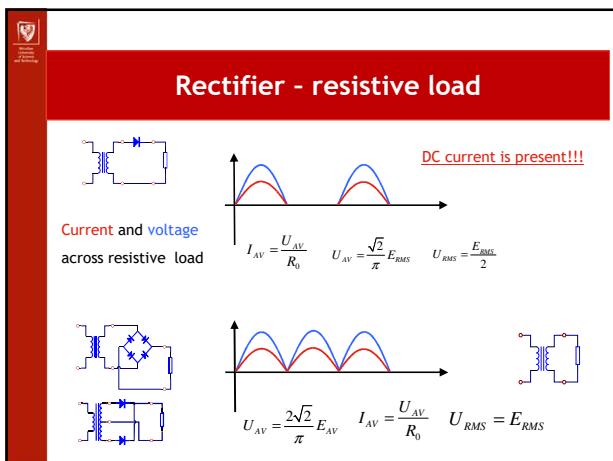



Basic relations

Maximum idle voltage:

$$U_{\max} \approx \sqrt{2}E_{RMS} - U_F \approx \sqrt{2}E_{RMS}$$


ripples:

$$U_{rip,pp} \approx \frac{Q}{C} = \left(\frac{U_{\max}}{R_0} \right) \frac{T}{C} = \frac{U_{\max}}{fR_0 C} \approx \frac{I_{AV}}{fC}$$

How to figure out this relationship!



Full wave rectifier

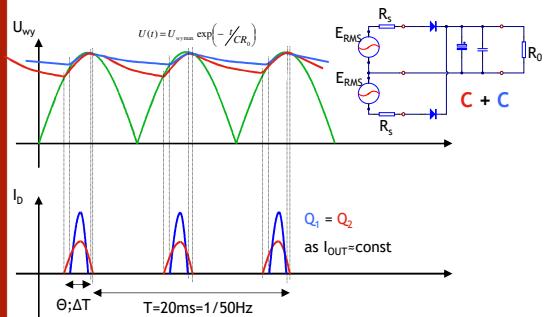



Basic relations

Maximum idle voltage:

$$U_{\max} \approx \sqrt{2}E_{RMS} - U_F$$


bridge:

$$U_{\max} \approx \sqrt{2}E_{RMS} - 2U_F$$

ripples:

$$U_{rip,pp} \approx \frac{Q}{C} = \frac{I_{AV} T / 2}{C} = \frac{I_{AV}}{2fC}$$

How to figure out this relationship!

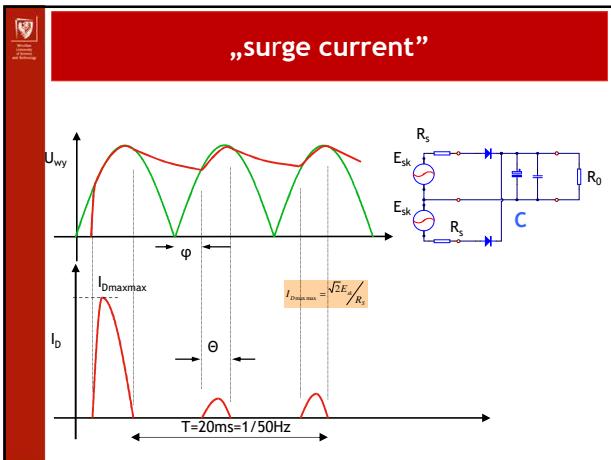

half-wave rectifier
for $U_{rpp}/U_{outAV} < 10\%$

No-load voltage	$U_{outMax} = \sqrt{2}E_{RMS} - U_F$
On-load voltage ($C=\infty$)	$U_{outAV} = U_{outMax} \left(1 - \sqrt{\frac{R_L}{R_s}} \right)$
Peak reverse voltage	$U_{Dmax} = 2\sqrt{2}E_{sk}$
Mean diode current	$I_{Dmean} = I_{outAV}$
Repetitive diode current	$I_{Dmax} = U_{outAV} / \sqrt{R_s R_L}$
Ripple voltage (peak to peak)	$U_{rpp} = \frac{I_{outAV}}{fC} \left(1 - \sqrt{\frac{R_L}{R_s}} \right)$
Minimum output voltage	$U_{outMin} = U_{outAV} - \frac{2}{3}U_{rpp}$

23

bridge rectifier
for $U_{rpp}/U_{outAV} < 10\%$


No-load voltage	$U_{outMax} = \sqrt{2}E_{RMS} - 2U_F$
On-load voltage ($C=\infty$)	$U_{outAV} = U_{outMax} \left(1 - \sqrt{\frac{R_L}{2R_s}} \right)$
Peak reverse voltage	$U_{Dmax} = \sqrt{2}E_{sk}$
Mean diode current	$I_{Dmean} = \frac{1}{2}I_{outAV}$
Repetitive diode current	$I_{Dmax} = U_{outAV} / \sqrt{2R_s R_L}$
Pipple voltage (peak to peak)	$U_{rpp} = \frac{I_{outAV}}{2fC} \left(1 - \sqrt{\frac{R_L}{2R_s}} \right)$
Minimum output voltage	$U_{outMin} = U_{outAV} - \frac{2}{3}U_{rpp}$

24

center-tap rectifier for $U_{rip}/U_{outAV} < 10\%$	
No-load voltage	$U_{outMax} = \sqrt{2}E_{RMS} - U_F$
On-load voltage ($C = \infty$)	$U_{outAV} = U_{outMax} \left(1 - \frac{R_s}{2R_L} \right)$
Peak reverse voltage	$U_{Dmax} = 2\sqrt{2}E_{av}$
Mean diode current	$I_{Dmean} = \frac{1}{2}I_{outAV}$
Repetitive diode current	$I_{Dmax} = U_{outAV} / \sqrt{2R_s R_L}$
Pipple voltage (peak to peak)	$U_{rip} = \frac{I_{outAV}}{2fC} \left(1 - \sqrt{\frac{R_s}{2R_L}} \right)$
Minimum output voltage	$U_{outMin} = U_{outAV} - \frac{2}{3}U_{rip}$

25



Główne parametry	
• Assumed:	- $E_{RMS} = U_{RMS} / n_{turn}$ ratio
	- R_s - series resistivity
	- U_F - forward diode voltage
• calculated	- U_{OUTRMS} ; U_{OUTAV} ; U_{OUTMAX} ; U_{OUTMIN} ; U_{rip}
	- I_{DAV} ; I_{DRMS} ; I_{DMAX} ; I_{OUTAV}
	- θ ; ΔT - flow angle; conducting time
	- $k_t = U_{rip,pp} / U_{OUTAV}$ - ripples coefficient
	- $\eta_u = U_{OUTAV} / E_{RMS}$ - voltage efficiency



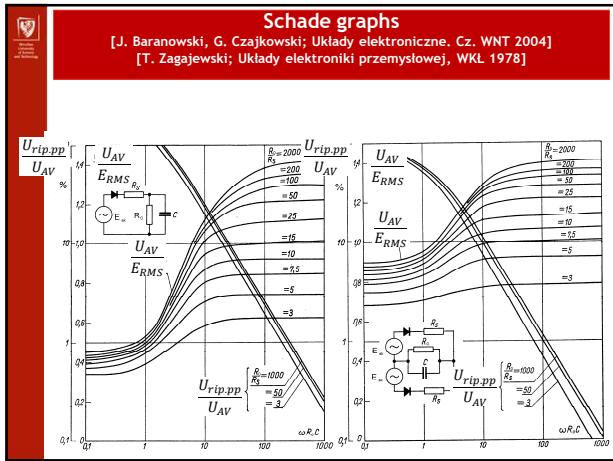


Crest & Wave Form factors

$CF = \frac{I_{MAX}}{I_{RMS}}$ Crest Factor -
For sin = $1,41 = \sqrt{2}$

$FF = \frac{I_{RMS}}{|I|_{AV}}$ waveForm Factor -
For sin = $1,11 = \pi/2/2$

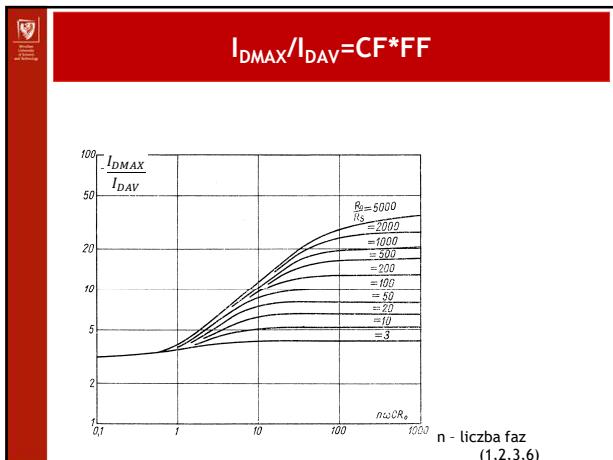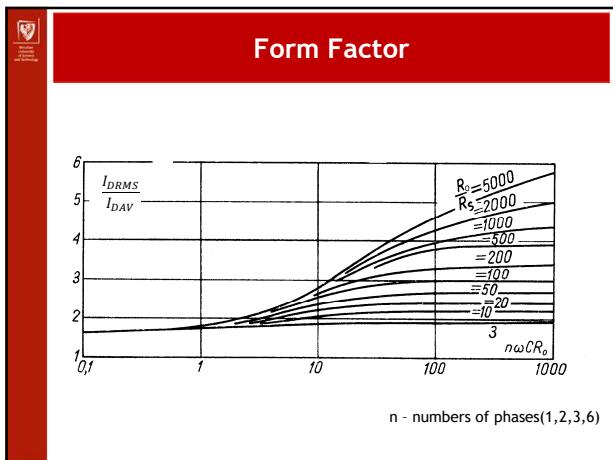

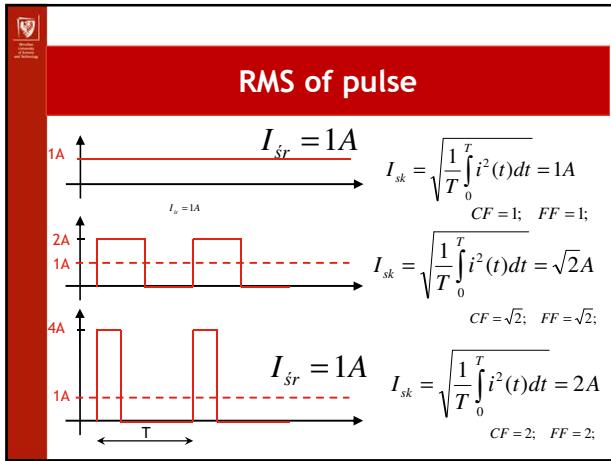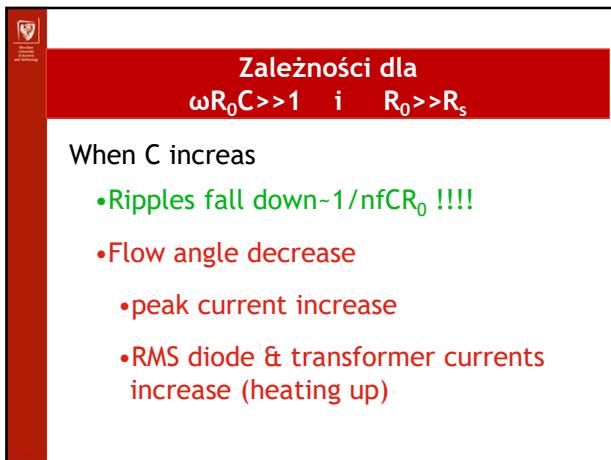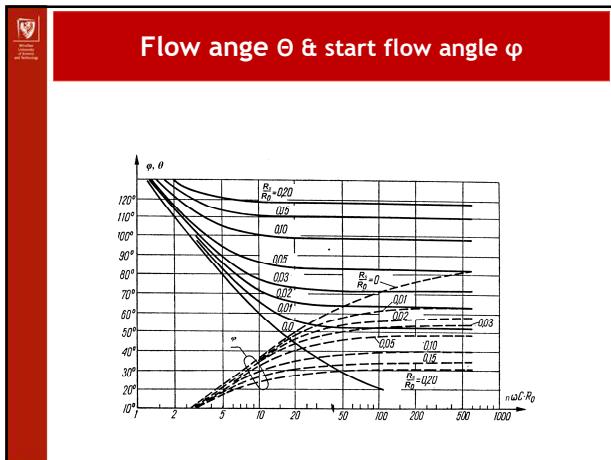



Power dissipated in diode


$$P_{Dreal} = \frac{1}{T} \int_0^T u_D(t) i_D(t) dt + \frac{1}{T} \int_0^T i_D^2(t) R_{D.series} dt =$$

$$= U_D I_{DAV} + I_{DRMS}^2 R_{D.series}$$

$$P_{Dreal} = 0.7V \bullet 1A + (3A)^2 \bullet 0.1\Omega = \\ = 0.7W + 0.9W$$



Form Factor $I_{DRMS}/I_{DAV} = FF$

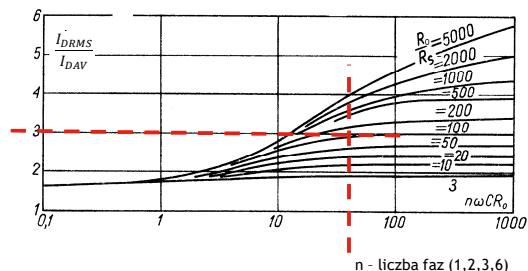



Porównanie zasilaczy

	Half-wave	Center-tap	Bridge
C To reach proper U_{rip}	$C = \frac{U_{OUT,max}}{U_{rip,pp}} \cdot \frac{1}{J\bar{R}_0}$	$\frac{1}{2}(..)$	$\frac{1}{2}(..)$
Maximum and RMS diode current)	high	medium	medium
Diode reverse voltage	$2E_{max}$	$1(..)$	$\frac{1}{2}(..)$
Current Harmonics	All Including DC ???	odd	odd



Współczynnik szczytu i kształtu

$$CF = \frac{I_{MAX}}{I_{RMS}}$$


Crest Factor - współczynnik szczytu
Dla sinusa = $1,41 = \sqrt{2}$

$$FF = \frac{I_{RMS}}{|I|_{AV}}$$

waveForm Factor - współczynnik kształtu
Dla sinusa = $1,11 = \pi/2/2$




„surge current”

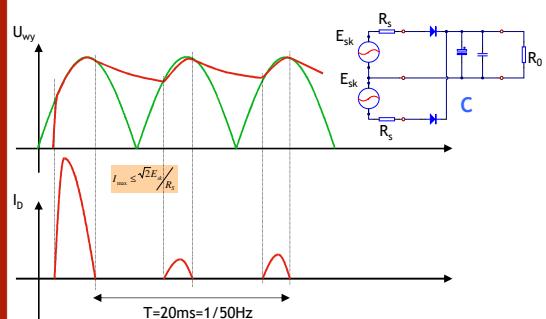





regulation EN61000-3-2 (IEC555)



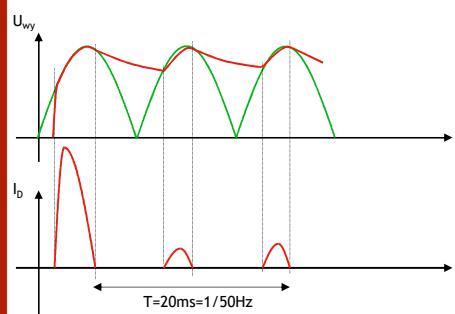




**Supply current distortion - IEC555
EN 61000-3-2**

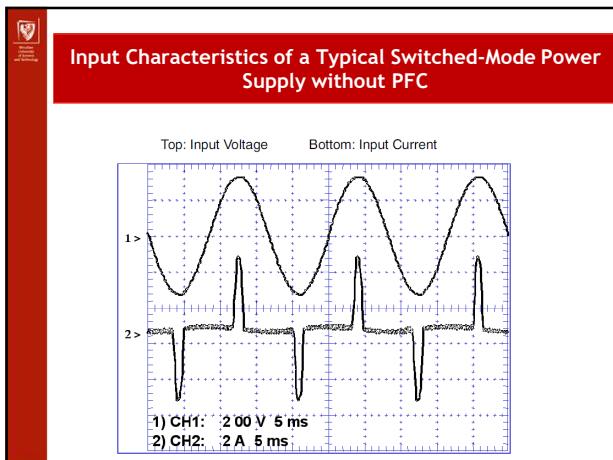- harmonics (up to 40 harmonic)
- current fluctuations of load
- surge current ???



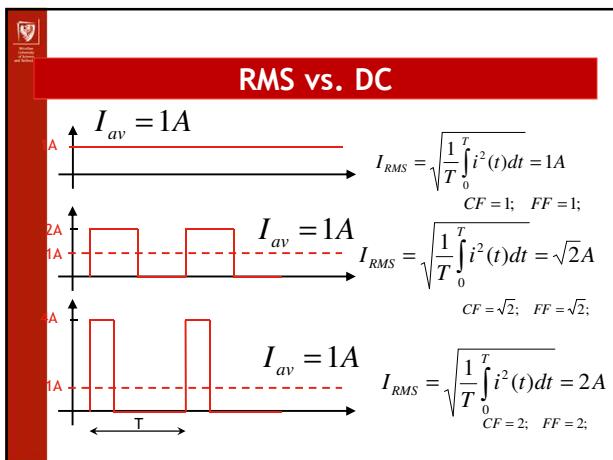

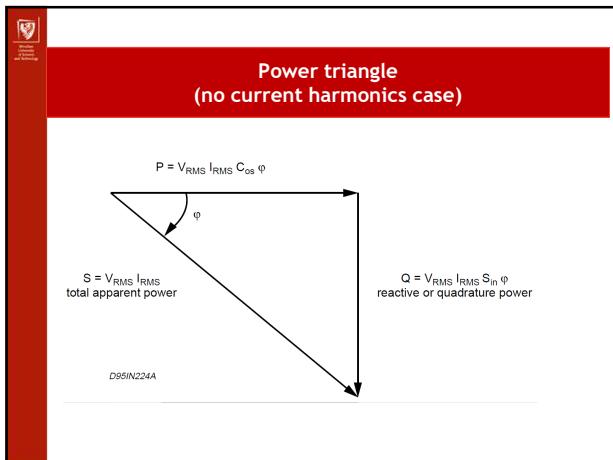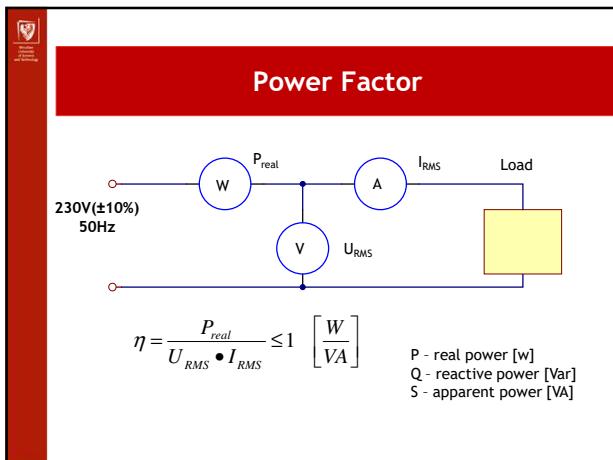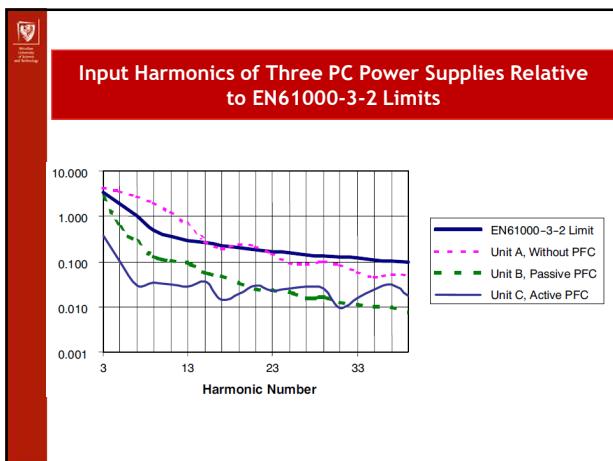

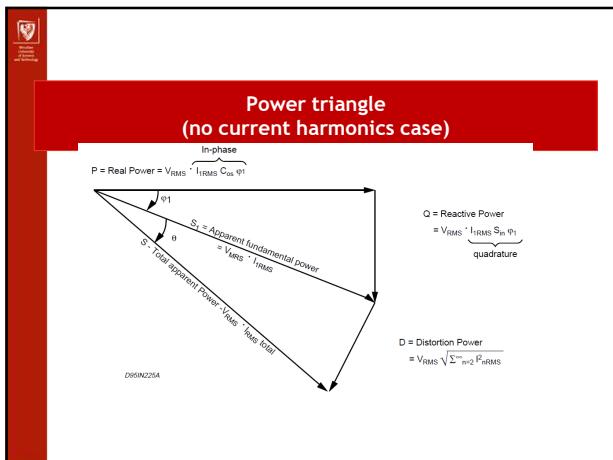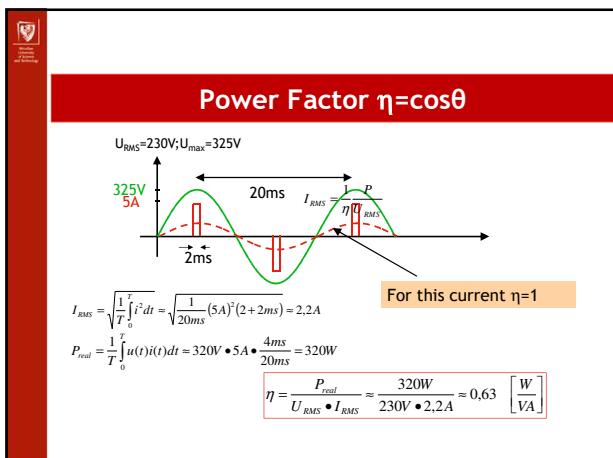

Total P.F. = $\eta = \cos \varphi_1 \cos \theta$

φ_1 is the "conventional" displacement angle (phase lag) between the in-phase fundamental I and V .
 θ is the distortion angle linked to the harmonic content of the current.

Both of reactive (Q) and distortion (D) powers produce extra RMS currents, giving extra losses so that then the mains supply network efficiency is decreased.

Improving P.F. means to improve both of factors i.e.:

$\varphi_1 \rightarrow 0 \quad \cos \varphi_1 \rightarrow 1$ = reduce phase lag between I and V
 $\theta \rightarrow 0 \quad \cos \theta \rightarrow 1$ = reduce harmonic content of I



THD vs. P.F. ($\cos \varphi_1 = 1$)

$$THD(\%) = 100 * \sqrt{\frac{1}{Kd^2} - 1}$$

$$Kd = \frac{1}{\sqrt{1 + \left(\frac{THD(\%)}{100} \right)^2}}$$

$$PF = \frac{1}{\sqrt{1 + \left(\frac{THD(\%)}{100} \right)^2}}$$







THD vs. P.F.




$$P.F. = \frac{\cos(\varphi_1)}{\sqrt{1 + \left(\frac{THD(\%)}{100} \right)^2}} = \cos(\theta) \cdot \cos(\varphi_1)$$





Harmonic Content of the Current Waveform

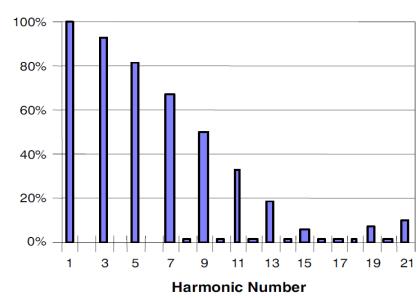


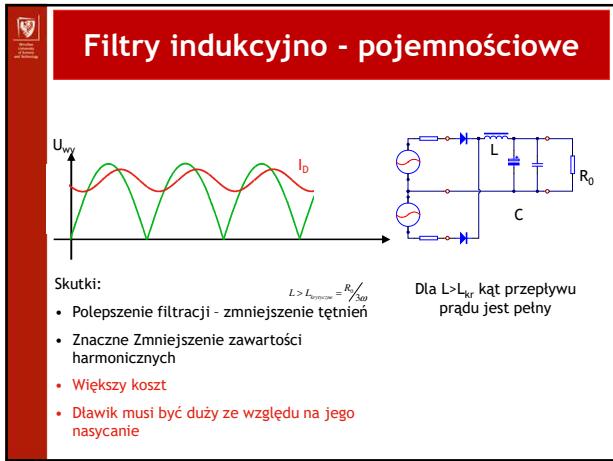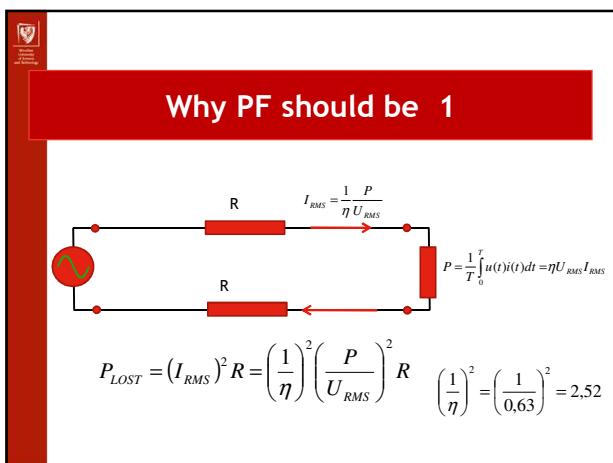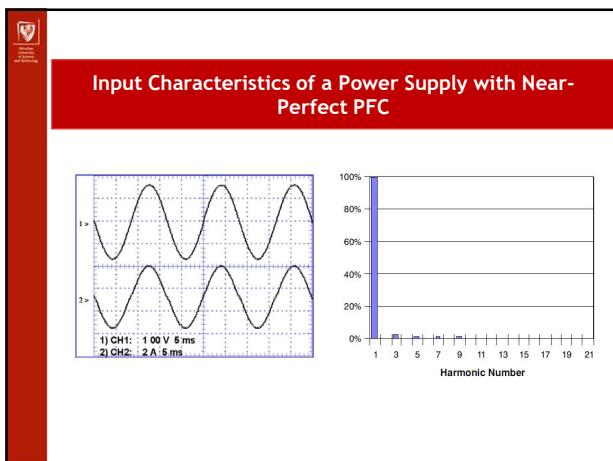


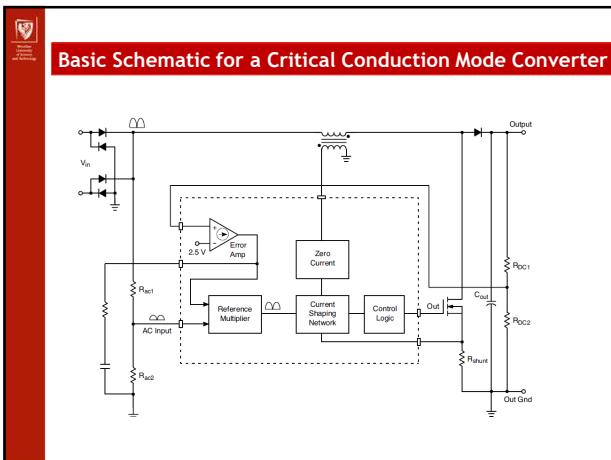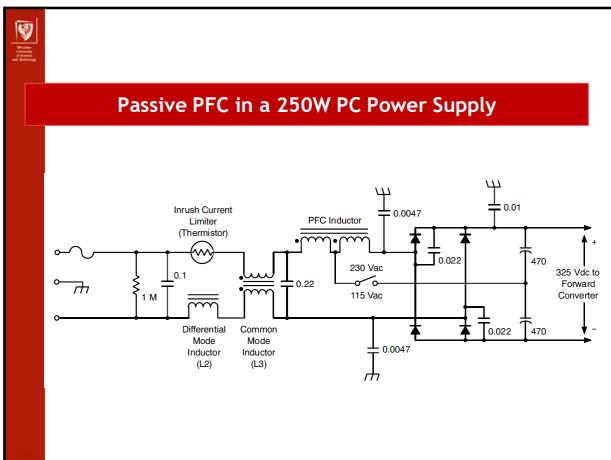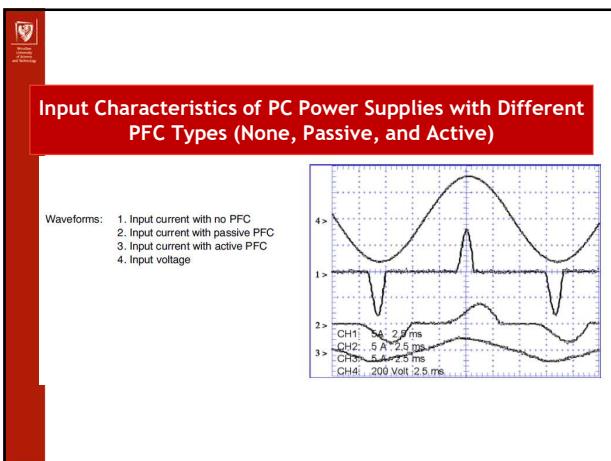


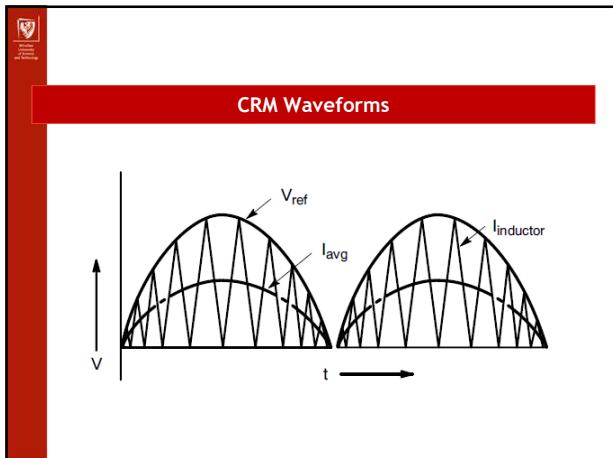




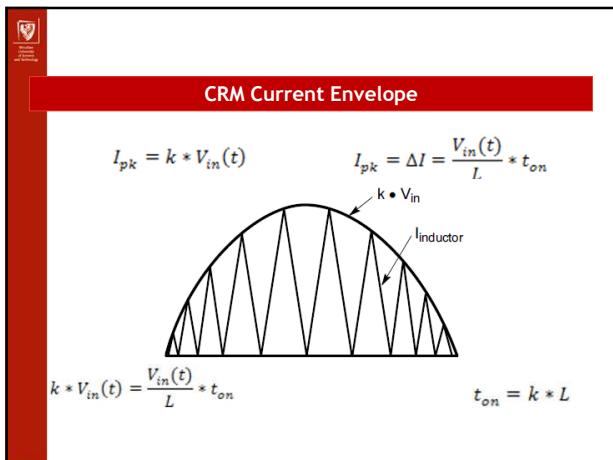


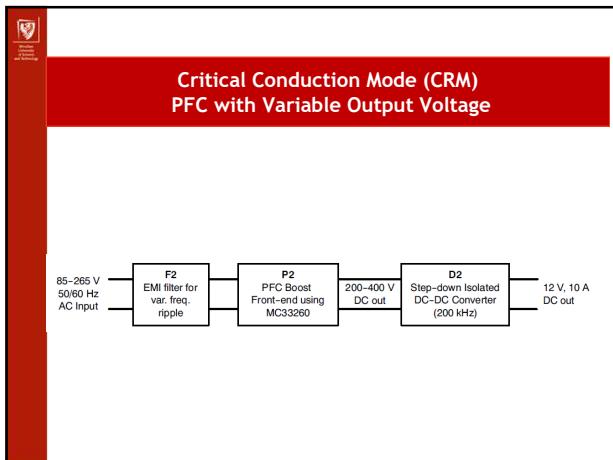

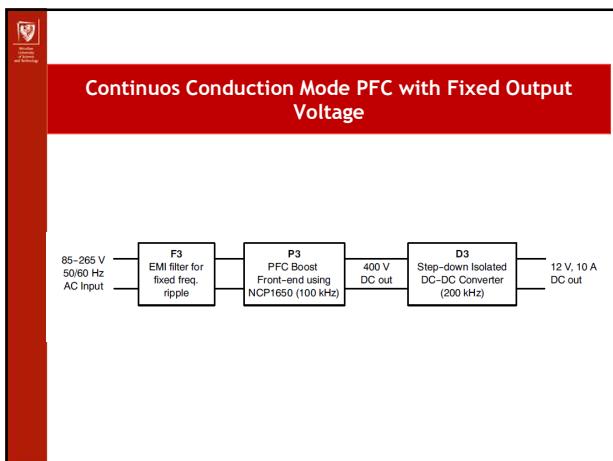

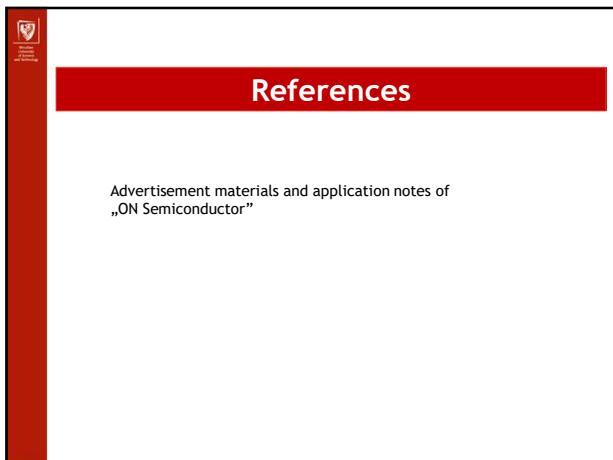

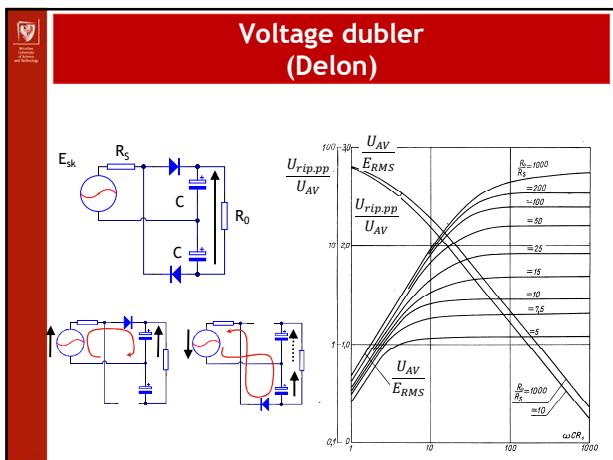

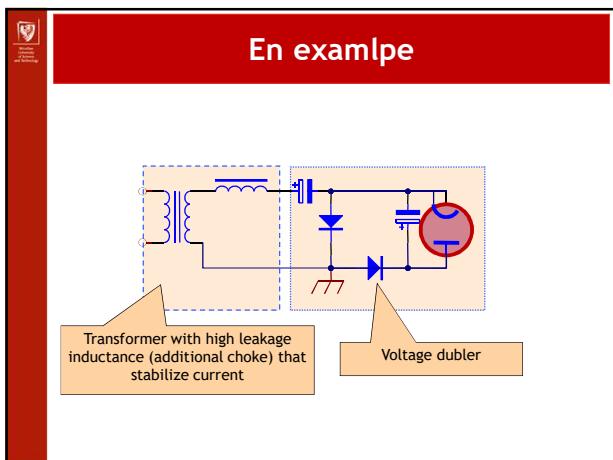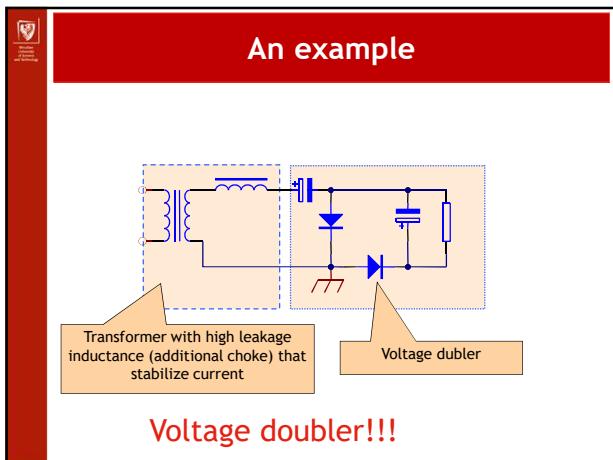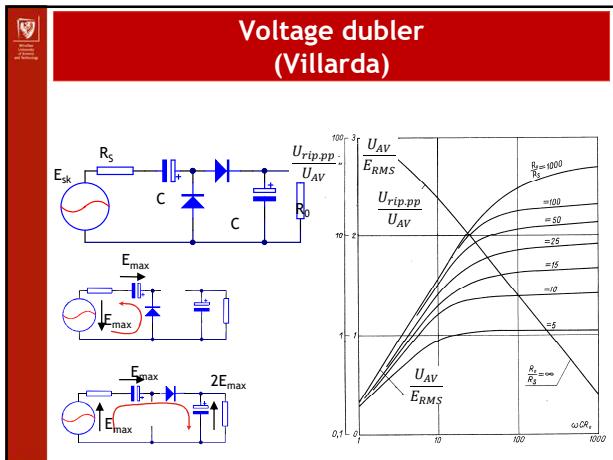

Przykład

Transformer with high leakage inductance (additional choke) that stabilizes current

Voltage doubler

Microwave oven !!!

Voltage multipliers

$$C \geq \frac{2n(n+2)}{fR_0}$$

$$U_{wy,ir} = n\sqrt{2}E_{sk} - U_i$$

$$U_i = \frac{I_{wy,ir}}{fC} \left(\frac{2}{3}n^3 + \frac{1}{2}n^2 - \frac{1}{6}n \right)$$

$$U_i = \frac{I_{wy,ir}}{fC} \left(\frac{1}{6}n^3 + \frac{1}{4}n^2 + \frac{1}{12}n \right)$$

summary

- Transformer (parameters, types, equivalent schematic diagram)
- Types of rectifiers
- Resistive load rectifier (voltage, current waveforms)
- Rectifier with capacitive filter (voltage, current waveforms)
- Power Factor (definition, way of correction)



Pytania kontrolne

- Schematy oraz zasada działania prostownika jedno-/dwupołówkowym/Gretza z filtrem pojemnościowym.
- Przebiegi napięć i prądów w prostownikach jw.
- Co to jest współczynnik mocy ?
- Co to jest napięcie tężnień i od czego zależy ?
- Uproszczony schemat zastępczy transformatora.
