


Electronic Circuits

1. Amplifiers - basics:

- a. Lower and upper frequency limit?
- b. Amplitude and phase characteristics of first order RC circuits.
- c. Compensated divider ?
- d. Bode plots ? (example: - Amplifier of the gain of 10V/V has lower and upper frequency limits of 100Hz and 100kHz respectively. Draw Bode plots for this amp.).
- e. Convert units dB to V/V or W/W ($\pm 3\text{dB}$, $\pm 6\text{dB}$, $\pm 10\text{dB}$, $\pm 20\text{dB}$, $\pm 40\text{dB}$ and other as e.g.. $13=10+3\text{dB}$).
- f. Explain units: dBu, dBm, dBV (be ready to convert units).

2. Operating amplifiers:

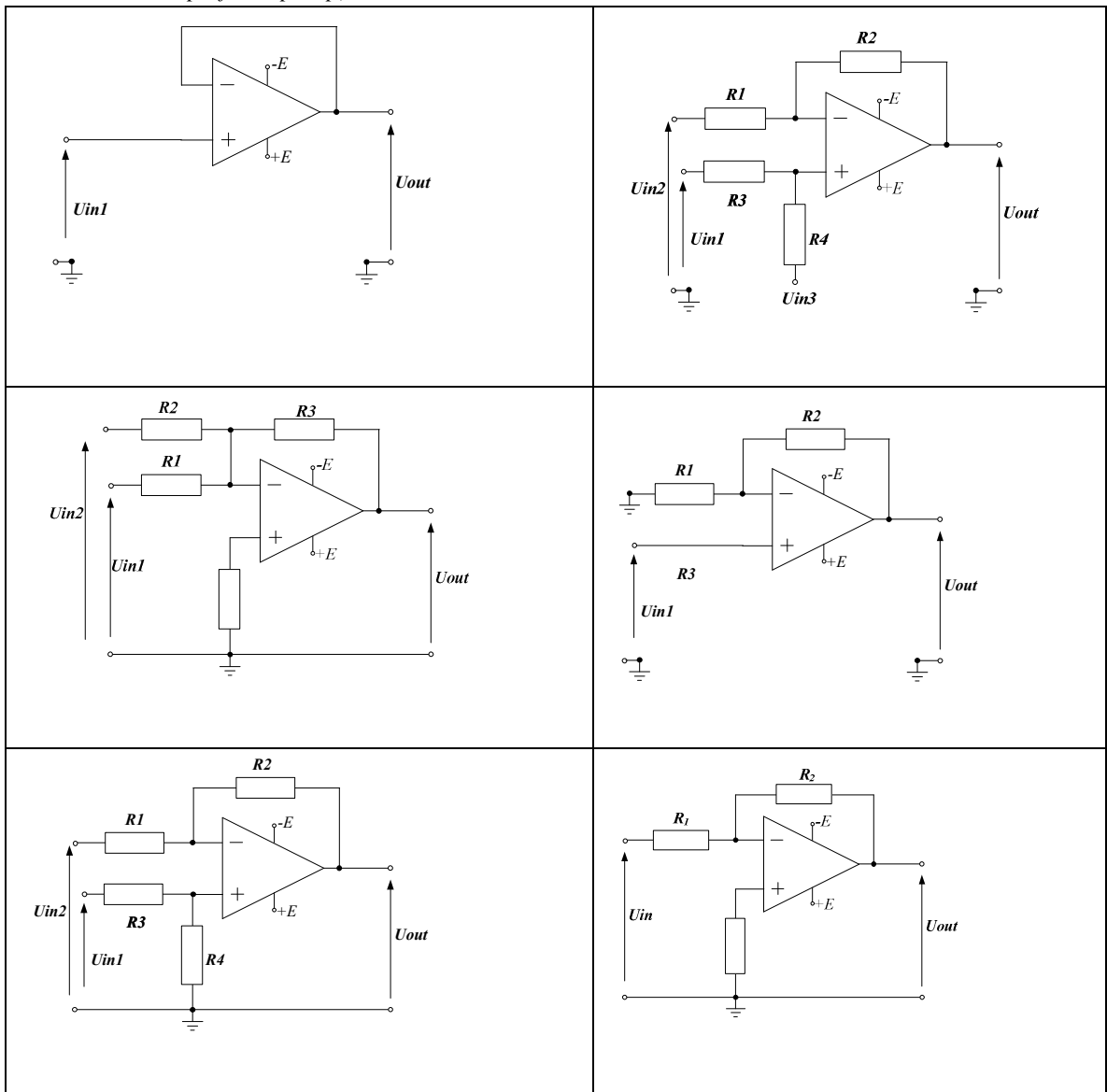- a. What is a differential amplifier ?
- b. Compare a perfect and a real OpAmp (give an order of magnitude of real parameters).
- c. Explain notion of a "offset voltage" ?
- d. Explain notion of CMRR (Common Mode Rejection Ratio) ?
- e. For a given schematic diagram calculate unknown voltage (Ri and other voltages are given, assume perfect OpAmp).



- f. What is an "instrumentation amp" ?
- g. Schematic diagram of differentiator and integrator.

- h. Explain way of operation of auto-zeroing amplifier ?
3. Active filters.
- Name the types of active filters due to the type of frequency response.
 - List the types of active filters due to the method of approximation of the frequency response. Characterize their basic properties in time and frequency domains.
 - What is a biquadratic section of a filter ?
 - How can be realized an active filter of the order higher than 2 ?
 - What is the basic principle of an active filter with switching capacitor ?
4. Amplifier with BJT – operating point:
- Small signal model of BJT.
 - List types of polarization schemes of BJT (draw schematics) ?
 - Establish operating point of BJT (assume all values of resistors , supply voltages, transistor parameters).
 - What is a load line (How to draw it ?) ?
 - What are the effects of changes in the parameters of the polarization (resistors, supply voltage, transistor parameters) on collector current potential of emitter, collector, collector-emitter voltage?
5. Amplifier with BJT – gain:
- Establish gain (and effective gain)of BJT amp for given: $R_G, R_{B1}, R_{B2}, R_C, R_L, \beta, \varphi_T, I_{CQ}, U_{CEQ}$.
 - Compare BJT amp in CE, CB, CC configurations.
 - What if emitter follower, what are specific parameter of it ?
6. Amplifier with BJT – frequency limits:
- What determines the lower and upper frequency of the amplifier with the BJT?
 - Compare upper frequency limits of CE, CB, CC configurations.
 - Explain Miller effect ?
7. Linear voltage controllers:
- What is a serial and parallel voltage regulator - main features ?
 - What is the principle of operation of a simple current limiter (with transistor)?
 - What is a "fold-back" current limiter??
 - Draw a load and line regulation curves of a voltage stabilizer. What parameters of the stabilizer can be read from them these curves ?
8. Oscillators:
- What are the condition of amplitude and the condition of phase of wave generation?
 - Name and draw main LC oscillators.
 - Name and draw basic RC oscillator.
 - Draw the electronic model of a crystal resonator. Draw an absolute value of the impedance of a crystal resonator vs. frequency. What are series and parallel resonance of the resonator?
 - What are the basic (essential) parameters of oscillators ?
 - What is a monostable and astable flip-flop?
 - What is a function generator ?; What is the principle of operation of the DDS generator (Direct Digital Synthesis)?
9. DC-DC converters:
- Draw a basic (simplified) schematic diagram of DCDC converter (step up, step down, inverter). Derive the formula for the output voltage; Sketch basic voltage and current waveforms..
10. Multipliers and PLL.
- List the basic types of analog multipliers - compare their accuracy with the speed of operation.
 - What is the principle of synchronous detection ?
 - What is the I&Q detector ?
 - Draw block diagram of a PLL and explain its operation principle.
 - Draw the examples of functional blocks of PLL (VCO, Filter, phase detector).
 - What is the capture frequency range and the lock frequency range of a PLL ?

- g. Draw the block diagram and explain principle of operation of AM detector, FM detector, frequency synthesizer with a PLL.*

11. AD and DA converters

- a. What is the quantization noise? How can be estimated the signal-to-noise ratio for the n-bit converter?*
- b. List several types of AC converters and arrange them in order from the largest to the smallest resolution and speed.*
- c. What is the difference between "sample and hold" and "track and hold" systems ?*

12. Rectifiers:

- a. Draw schematic diagram of half-wave, center-tap and bridge rectifier with capacitive filter.*
- b. Draw the currents and voltages wave forms in rectifier (HW, CT, Bridge).*
- c. What is the PF (Power Factor) ?*
- d. What is the voltage ripples and what the ripples depends on ?*
- e. Draw a simplified model of real transformer. Describe the components of the model..*